


Introduction to CMOS VLSI Design

Lecture 5: Logical Effort

David Harris



Harvey Mudd College
Spring 2004


Outline

- ❑ Introduction
- ❑ Delay in a Logic Gate
- ❑ Multistage Logic Networks
- ❑ Choosing the Best Number of Stages
- ❑ Example
- ❑ Summary

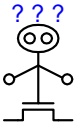5: Logical Effort CMOS VLSI Design Slide 2

Introduction


- ❑ Chip designers face a bewildering array of choices
 - What is the best circuit topology for a function?
 - How many stages of logic give least delay?
 - How wide should the transistors be?
- ❑ Logical effort is a method to make these decisions
 - Uses a simple model of delay
 - Allows back-of-the-envelope calculations
 - Helps make rapid comparisons between alternatives
 - Emphasizes remarkable symmetries



5: Logical Effort CMOS VLSI Design Slide 3

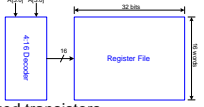Example

- ❑ Ben Bitdiddle is the memory designer for the Motorola 68W86, an embedded automotive processor. Help Ben design the decoder for a register file.
- ❑ Decoder specifications:
 - 16 word register file
 - Each word is 32 bits wide
 - Each bit presents load of 3 unit-sized transistors
 - True and complementary address inputs A[3:0]
 - Each input may drive 10 unit-sized transistors
- ❑ Ben needs to decide:
 - How many stages to use?
 - How large should each gate be?
 - How fast can decoder operate?



5: Logical Effort CMOS VLSI Design Slide 4

Delay in a Logic Gate

- ❑ Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

$\tau = 3RC$
 $\approx 12 \text{ ps in } 180 \text{ nm process}$
 $40 \text{ ps in } 0.6 \mu\text{m process}$

5: Logical Effort CMOS VLSI Design Slide 5

Delay in a Logic Gate

- ❑ Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

- ❑ Delay has two components

$$d = f + p$$

5: Logical Effort CMOS VLSI Design Slide 6

Delay in a Logic Gate

- Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

- Delay has two components

$$d = f + p$$

- Effort delay $f = gh$ (a.k.a. stage effort)
 - Again has two components

5: Logical Effort CMOS VLSI Design Slide 7

Delay in a Logic Gate

- Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

- Delay has two components

$$d = f + p$$

- Effort delay $f = gh$ (a.k.a. stage effort)
 - Again has two components
- g : logical effort
 - Measures relative ability of gate to deliver current
 - $g = 1$ for inverter

5: Logical Effort CMOS VLSI Design Slide 8

Delay in a Logic Gate

- Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

- Delay has two components

$$d = f + p$$

- Effort delay $f = gh$ (a.k.a. stage effort)
 - Again has two components
- h : electrical effort = C_{out} / C_{in}
 - Ratio of output to input capacitance
 - Sometimes called fanout

5: Logical Effort CMOS VLSI Design Slide 9

Delay in a Logic Gate

- Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

- Delay has two components

$$d = f + p$$


- Parasitic delay p
 - Represents delay of gate driving no load
 - Set by internal parasitic capacitance

5: Logical Effort CMOS VLSI Design Slide 10

Delay Plots

$$d = f + p$$

$$= gh + p$$

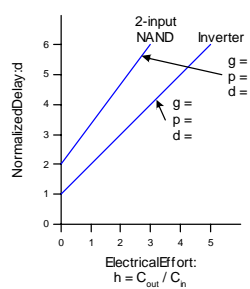


5: Logical Effort CMOS VLSI Design Slide 11

Delay Plots

$$d = f + p$$

$$= gh + p$$


- What about NOR2?

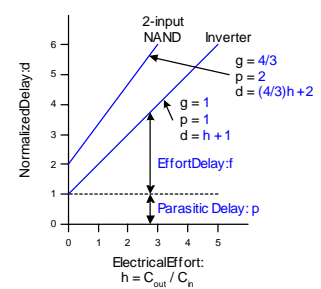

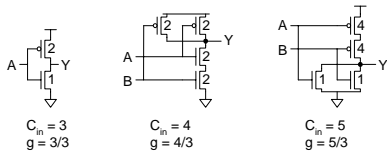5: Logical Effort CMOS VLSI Design Slide 12

Computing Logical Effort

- DEF: *Logical effort is the ratio of the input capacitance of a gate to the input capacitance of an inverter delivering the same output current.*
- Measure from delay vs. fanout plots
- Or estimate by counting transistor widths



5: Logical Effort CMOS VLSI Design Slide 13

Catalog of Gates

- Logical effort of common gates

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		4/3	5/3	6/3	(n+2)/3
NOR		5/3	7/3	9/3	(2n+1)/3
Tristate / mux	2	2	2	2	2
XOR, XNOR		4, 4	6, 12, 6	8, 16, 16, 8	

5: Logical Effort CMOS VLSI Design Slide 14

Catalog of Gates


- Parasitic delay of common gates
– In multiples of $p_{inv} (\approx 1)$

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		2	3	4	n
NOR		2	3	4	n
Tristate / mux	2	4	6	8	2n
XOR, XNOR		4	6	8	

5: Logical Effort CMOS VLSI Design Slide 15

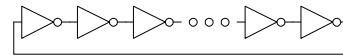Example: Ring Oscillator

- Estimate the frequency of an N-stage ring oscillator




Logical Effort: $g =$
 Electrical Effort: $h =$
 Parasitic Delay: $p =$
 Stage Delay: $d =$
 Frequency: $f_{osc} =$

5: Logical Effort CMOS VLSI Design Slide 16

 Example: Ring Oscillator

- Estimate the frequency of an N-stage ring oscillator




Logical Effort: $g = 1$ 31 stage ring oscillator in
 Electrical Effort: $h = 1$ 0.6 μm process has
 Parasitic Delay: $p = 1$ frequency of ~ 200 MHz
 Stage Delay: $d = 2$
 Frequency: $f_{osc} = 1/(2 \cdot N \cdot d) = 1/4N$

5: Logical Effort CMOS VLSI Design Slide 17

 Example: FO4 Inverter

- Estimate the delay of a fanout-of-4 (FO4) inverter




Logical Effort: $g =$
 Electrical Effort: $h =$
 Parasitic Delay: $p =$
 Stage Delay: $d =$

5: Logical Effort CMOS VLSI Design Slide 18

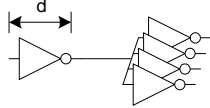Example: FO4 Inverter

- Estimate the delay of a fanout-of-4 (FO4) inverter



Logical Effort: $g = 1$
 Electrical Effort: $h = 4$
 Parasitic Delay: $p = 1$
 Stage Delay: $d = 5$

The FO4 delay is about
 200 ps in 0.6 μm process
 60 ps in a 180 nm process
 $f/3$ ns in an f μm process

5: Logical Effort CMOS VLSI Design Slide 19


Multistage Logic Networks

- Logical effort generalizes to multistage networks

Path Logical Effort $G = \prod g_i$

Path Electrical Effort $H = \frac{C_{\text{out-path}}}{C_{\text{in-path}}}$

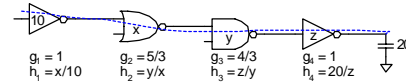Path Effort $F = \prod f_i = \prod g_i h_i$



5: Logical Effort CMOS VLSI Design Slide 20

Multistage Logic Networks

- Logical effort generalizes to multistage networks

Path Logical Effort $G = \prod g_i$

Path Electrical Effort $H = \frac{C_{\text{out-path}}}{C_{\text{in-path}}}$

Path Effort $F = \prod f_i = \prod g_i h_i$


- Can we write $F = GH$?

5: Logical Effort CMOS VLSI Design Slide 21

Paths that Branch

- No! Consider paths that branch:

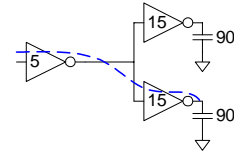$G =$
 $H =$
 $GH =$
 $h_1 =$
 $h_2 =$
 $F = GH?$




5: Logical Effort CMOS VLSI Design Slide 22

Paths that Branch

- No! Consider paths that branch:

 $G = 1$
 $H = 90 / 5 = 18$
 $GH = 18$
 $h_1 = (15 + 15) / 5 = 6$
 $h_2 = 90 / 15 = 6$
 $F = g_1 g_2 h_1 h_2 = 36 = 2GH$



5: Logical Effort CMOS VLSI Design Slide 23

Branching Effort

- Introduce *branching effort*
 - Accounts for branching between stages in path

$$b = \frac{C_{\text{on path}} + C_{\text{off path}}}{C_{\text{on path}}}$$

$$B = \prod b_i$$

Note:

$$\prod h_i = BH$$

- Now we compute the path effort
 - $F = GBH$

5: Logical Effort CMOS VLSI Design Slide 24

Multistage Delays

- Path Effort Delay $D_F = \sum f_i$
- Path Parasitic Delay $P = \sum p_i$
- Path Delay $D = \sum d_i = D_F + P$

5: Logical Effort CMOS VLSI Design Slide 25

Designing Fast Circuits

- $D = \sum d_i = D_F + P$
- Delay is smallest when each stage bears same effort
 - $\hat{f} = g, h_i = F^{\frac{1}{N}}$
- Thus minimum delay of N stage path is
 - $D = NF^{\frac{1}{N}} + P$
- This is a **key** result of logical effort
 - Find fastest possible delay
 - Doesn't require calculating gate sizes

5: Logical Effort CMOS VLSI Design Slide 26

Gate Sizes

- How wide should the gates be for least delay?

$$\hat{f} = gh = g \frac{C_{out}}{C_{in}}$$


$$\Rightarrow C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$

- Working backward, apply capacitance transformation to find input capacitance of each gate given load it drives.
- Check work by verifying input cap spec is met.

5: Logical Effort CMOS VLSI Design Slide 27

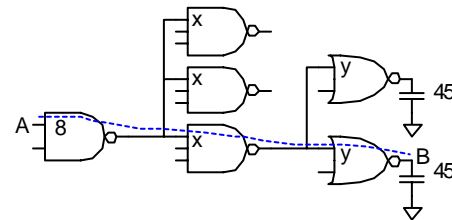
Example: 3-stage path

- Select gate sizes x and y for least delay from A to B



5: Logical Effort CMOS VLSI Design Slide 28


Example: 3-stage path

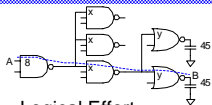

Logical Effort $G =$
 Electrical Effort $H =$
 Branching Effort $B =$
 Path Effort $F =$
 Best Stage Effort $\hat{f} =$
 Parasitic Delay $P =$
 Delay $D =$

5: Logical Effort CMOS VLSI Design Slide 29

Example: 3-stage path

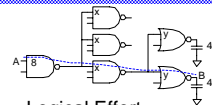

Logical Effort $G = (4/3) * (5/3) * (5/3) = 100/27$
 Electrical Effort $H = 45/8$
 Branching Effort $B = 3 * 2 = 6$
 Path Effort $F = GBH = 125$
 Best Stage Effort $\hat{f} = \sqrt[3]{F} = 5$
 Parasitic Delay $P = 2 + 3 + 2 = 7$
 Delay $D = 3 * 5 + 7 = 22 = 4.4 \text{ FO4}$


5: Logical Effort CMOS VLSI Design Slide 30

Example: 3-stage path

- Work backward for sizes

$$y =$$

$$x =$$

 


5: Logical Effort CMOS VLSI Design Slide 31

Example: 3-stage path

- Work backward for sizes

$$y = 45 * (5/3) / 5 = 15$$

$$x = (15*2) * (5/3) / 5 = 10$$

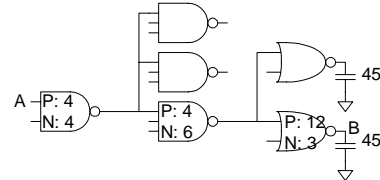


5: Logical Effort CMOS VLSI Design Slide 32

Best Number of Stages

- How many stages should a path use?
 - Minimizing number of stages is not always fastest
- Example: drive 64-bit datapath with unit inverter

$$D =$$

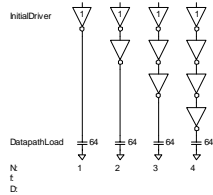


5: Logical Effort CMOS VLSI Design Slide 33

Best Number of Stages

- How many stages should a path use?
 - Minimizing number of stages is not always fastest
- Example: drive 64-bit datapath with unit inverter

$$D = NF^{1/N} + P$$

$$= N(64)^{1/N} + N$$

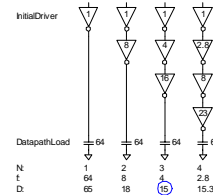

5: Logical Effort CMOS VLSI Design Slide 34

Derivation

- Consider adding inverters to end of path
 - How many give least delay?

$$D = NF^{1/N} + \sum_{i=1}^{n_1} p_i + (N - n_1) p_{inv}$$

$$\frac{\partial D}{\partial N} = -F^{1/N} \ln F^{1/N} + F^{1/N} + p_{inv} = 0$$

- Define best stage effort $\rho = F^{1/N}$

$$p_{inv} + \rho(1 - \ln \rho) = 0$$

5: Logical Effort CMOS VLSI Design Slide 35


Best Stage Effort

- $p_{inv} + \rho(1 - \ln \rho) = 0$ has no closed-form solution
- Neglecting parasitics ($p_{inv} = 0$), we find $\rho = 2.718$ (e)
- For $p_{inv} = 1$, solve numerically for $\rho = 3.59$

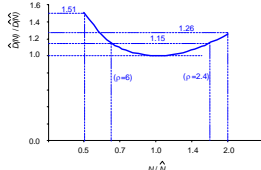5: Logical Effort CMOS VLSI Design Slide 36

Sensitivity Analysis

- How sensitive is delay to using exactly the best number of stages?




- $2.4 < \rho < 6$ gives delay within 15% of optimal
 - We can be sloppy!
 - I like $\rho = 4$

5: Logical Effort CMOS VLSI Design Slide 37

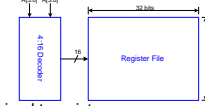Example, Revisited

- Ben Bitdiddle is the memory designer for the Motorola 68W86, an embedded automotive processor. Help Ben design the decoder for a register file.



- Decoder specifications:
 - 16 word register file
 - Each word is 32 bits wide
 - Each bit presents load of 3 unit-sized transistors
 - True and complementary address inputs $A[3:0]$
 - Each input may drive 10 unit-sized transistors
- Ben needs to decide:
 - How many stages to use?
 - How large should each gate be?
 - How fast can decoder operate?

5: Logical Effort CMOS VLSI Design Slide 38

Number of Stages

- Decoder effort is mainly electrical and branching
 - Electrical Effort: $H =$
 - Branching Effort: $B =$

- If we neglect logical effort (assume $G = 1$)
 - Path Effort: $F =$

Number of Stages: $N =$

5: Logical Effort CMOS VLSI Design Slide 39

Number of Stages

- Decoder effort is mainly electrical and branching
 - Electrical Effort: $H = (32 \cdot 3) / 10 = 9.6$
 - Branching Effort: $B = 8$

- If we neglect logical effort (assume $G = 1$)
 - Path Effort: $F = GBH = 76.8$


Number of Stages: $N = \log_4 F = 3.1$

- Try a 3-stage design

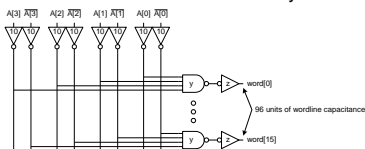5: Logical Effort CMOS VLSI Design Slide 40

Gate Sizes & Delay


- Logical Effort: $G =$
- Path Effort: $F =$
- Stage Effort: $\hat{f} =$
- Path Delay: $D =$
- Gate sizes: $z =$ $y =$



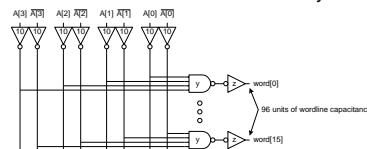5: Logical Effort CMOS VLSI Design Slide 41

Gate Sizes & Delay

- Logical Effort: $G = 1 \cdot 6/3 \cdot 1 = 2$
- Path Effort: $F = GBH = 154$
- Stage Effort: $\hat{f} = F^{1/3} = 5.36$
- Path Delay: $D = 3\hat{f} + 1 + 4 + 1 = 22.1$
- Gate sizes: $z = 96 \cdot 1/5.36 = 18$ $y = 18 \cdot 2/5.36 = 6.7$



5: Logical Effort CMOS VLSI Design Slide 42

Comparison

- Compare many alternatives with a spreadsheet

Design	N	G	P	D
NAND4-INV	2	2	5	29.8
NAND2-NOR2	2	20/9	4	30.1
INV-NAND4-INV	3	2	6	22.1
NAND4-INV-INV-INV	4	2	7	21.1
NAND2-NOR2-INV-INV	4	20/9	6	20.5
NAND2-INV-NAND2-INV	4	16/9	6	19.7
INV-NAND2-INV-NAND2-INV	5	16/9	7	20.4
NAND2-INV-NAND2-INV-INV-INV	6	16/9	8	21.6

5: Logical Effort

CMOS VLSI Design

Slide 43

Review of Definitions

Term	Stage	Path
number of stages	1	N
logical effort	g	$G = \prod g_i$
electrical effort	$h = \frac{C_{in}}{C_{in,0}}$	$H = \frac{C_{out,0}}{C_{in,0}}$
branching effort	$b = \frac{C_{out,0} + C_{in,0}}{C_{in,0}}$	$B = \prod b_i$
effort	$f = gh$	$F = GBH$
effort delay	f	$D_f = \sum f_i$
parasitic delay	p	$P = \sum p_i$
delay	$d = f + p$	$D = \sum d_i = D_f + P$

5: Logical Effort

CMOS VLSI Design

Slide 44

Method of Logical Effort

- 1) Compute path effort $F = GBH$
- 2) Estimate best number of stages $N = \log_g F$
- 3) Sketch path with N stages
- 4) Estimate least delay $D = NF^{\frac{1}{N}} + P$
- 5) Determine best stage effort $\hat{f} = F^{\frac{1}{N}}$
- 6) Find gate sizes $C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$

5: Logical Effort

CMOS VLSI Design

Slide 45

Limits of Logical Effort

- Chicken and egg problem
 - Need path to compute G
 - But don't know number of stages without G
- Simplistic delay model
 - Neglects input rise time effects
- Interconnect
 - Iteration required in designs with wire
- Maximum speed only
 - Not minimum area/power for constrained delay

5: Logical Effort

CMOS VLSI Design

Slide 46

Summary

- Logical effort is useful for thinking of delay in circuits
 - Numeric logical effort characterizes gates
 - NANDs are faster than NORs in CMOS
 - Paths are fastest when effort delays are ~ 4
 - Path delay is weakly sensitive to stages, sizes
 - But using fewer stages doesn't mean faster paths
 - Delay of path is about $\log_g F$ FO4 inverter delays
 - Inverters and NAND2 best for driving large caps
- Provides language for discussing fast circuits
 - But requires practice to master

5: Logical Effort

CMOS VLSI Design

Slide 47