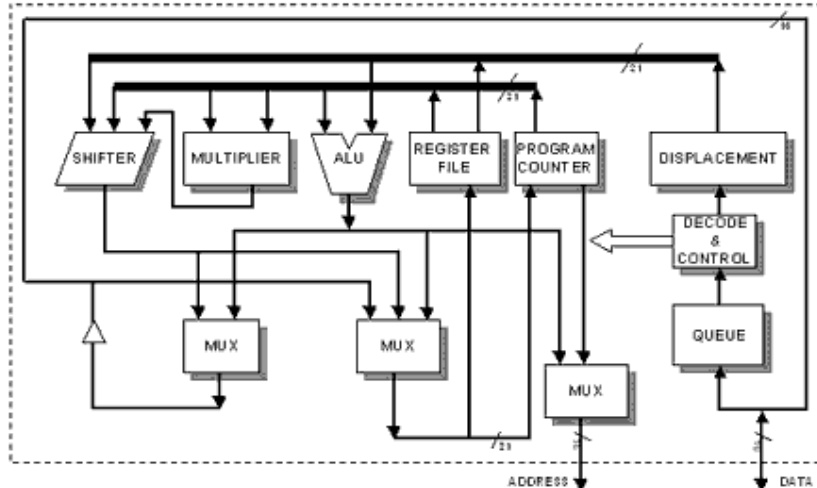




Where are we?

- ▶ Subsystem Design
 - ▶ Registers and Register Files
 - ▶ Adders and ALUs
 - ▶ Simple ripple carry addition
 - ▶ Transistor schematics
 - ▶ Faster addition
 - ▶ Logic generation
 - ▶ How it fits into the datapath

Data Path Design



 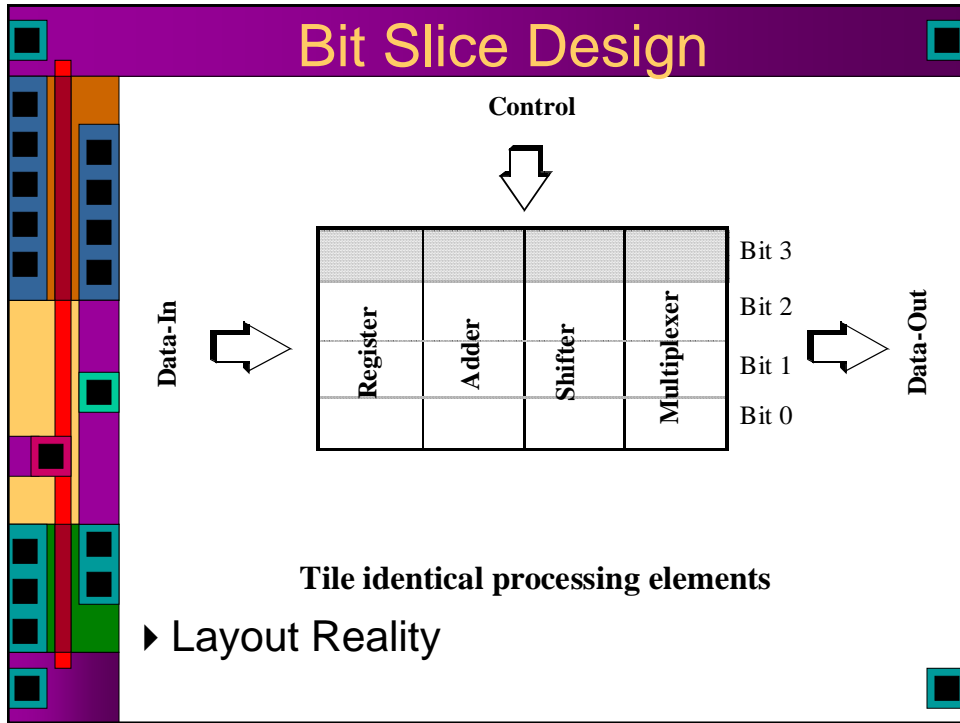- ▶ Block-diagram style data path description







Bit Slice Plan



- ▶ Recall planning a DFF to make a register
 - ▶ Inputs on top in M2
 - ▶ Outputs on bottom in M2
 - ▶ Clock and Clock-bar routed horizontally in M1

Bit Slice Plan

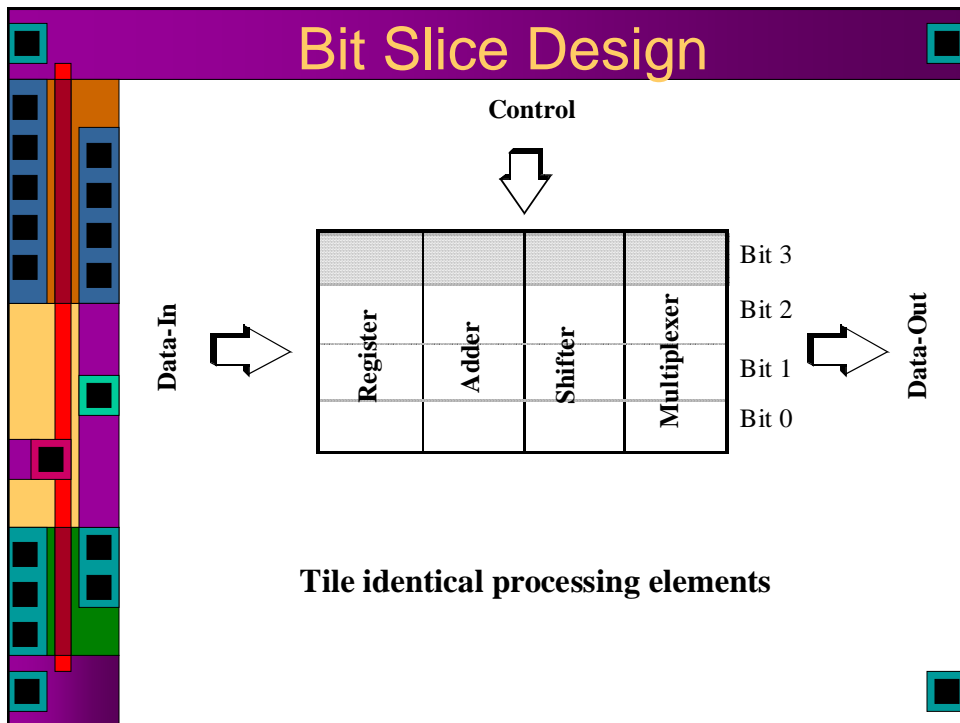 - ▶ Now extend this to a register file
 - ▶ D inputs go to all cells
 - ▶ Can select one register for writing by controlling the clock
 - ▶ Q outputs go all the way through the register file
 - ▶ Each cell can drive Q from enabled inverter
 - ▶ Now you can select one register for reading by selecting which cell is driving its output



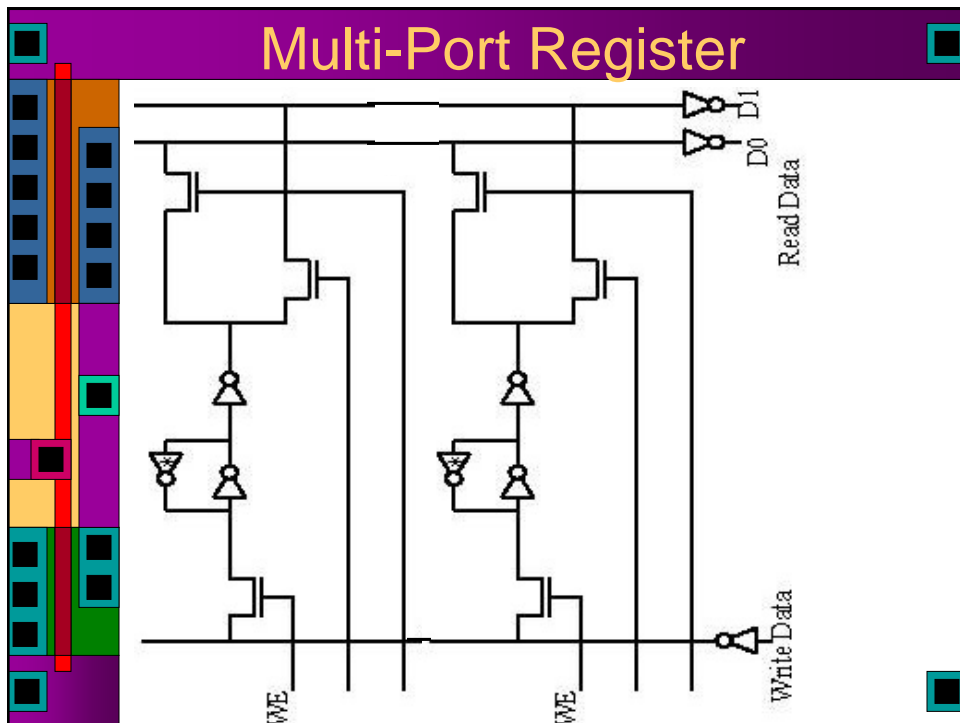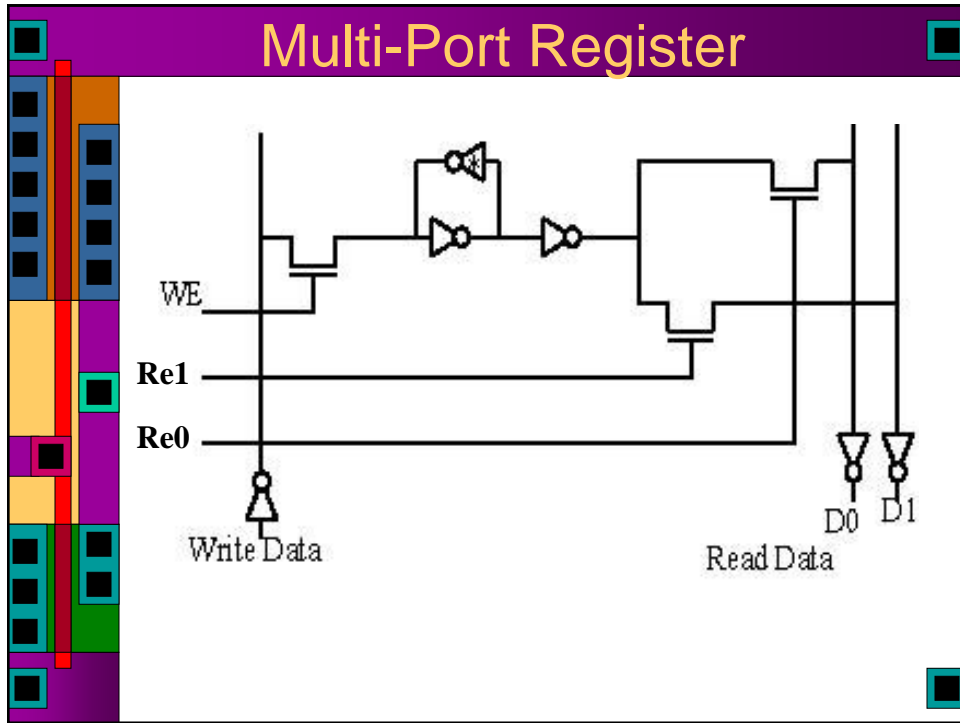

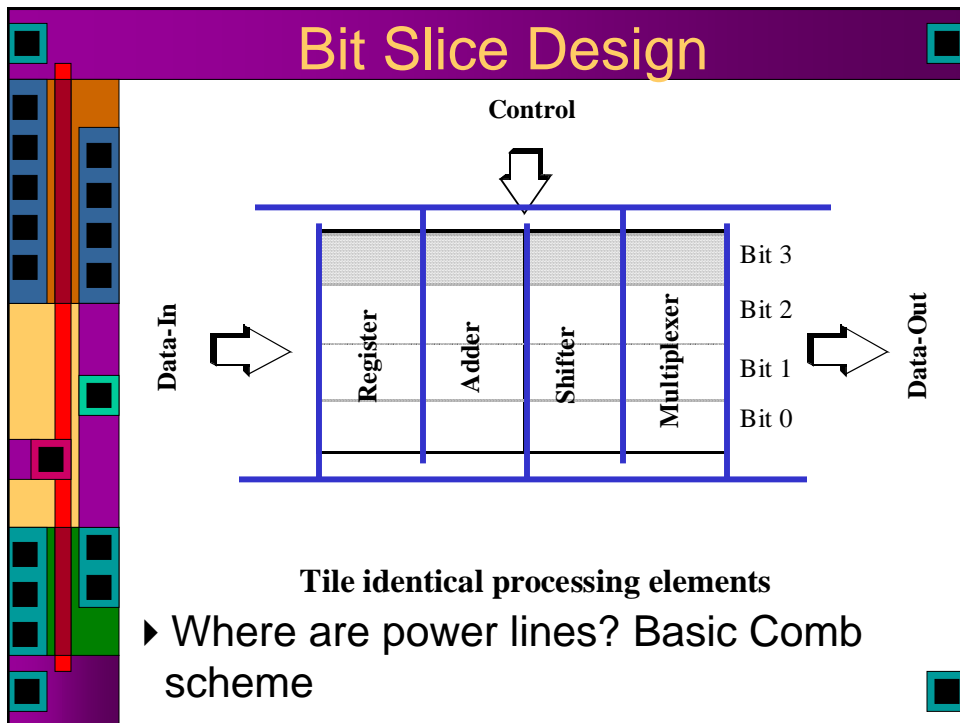
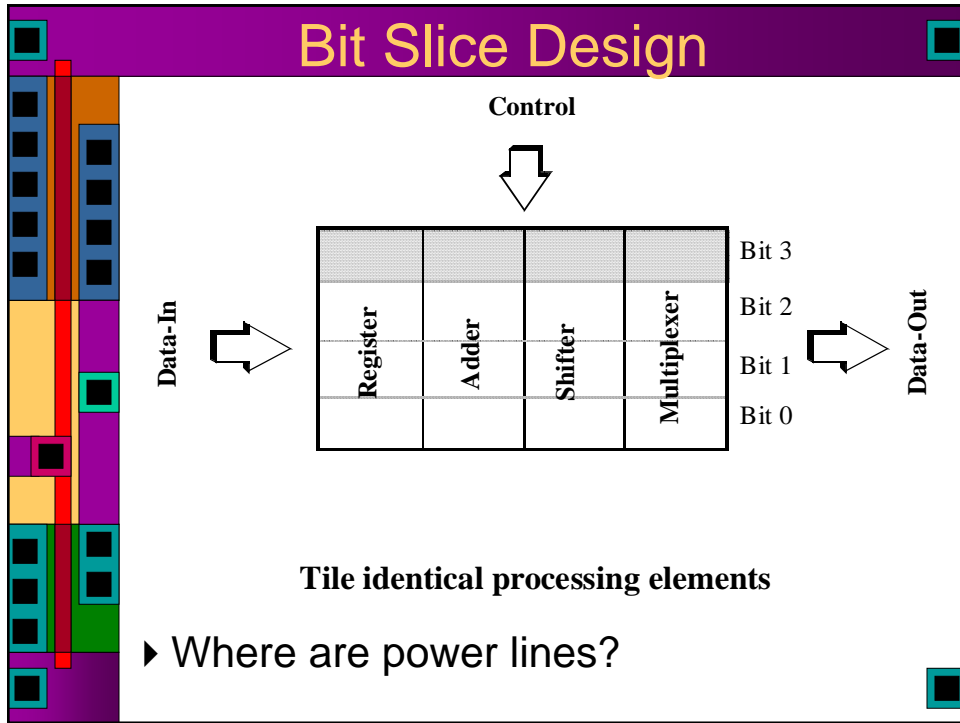


Chip-Wide View of Power

- ▶ Power Routing is a global chip-wide issue
- ▶ Here's another approach
- ▶ Note the Vdd and Gnd pads
- ▶ Global rings with combs for regions of the chip

Chip-Wide View of Power

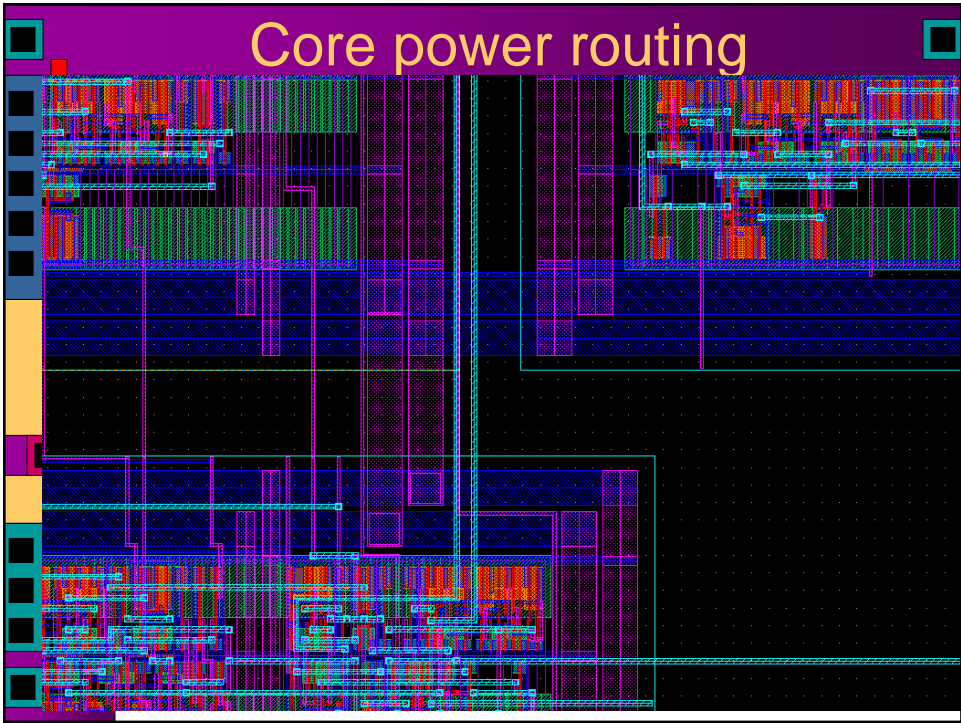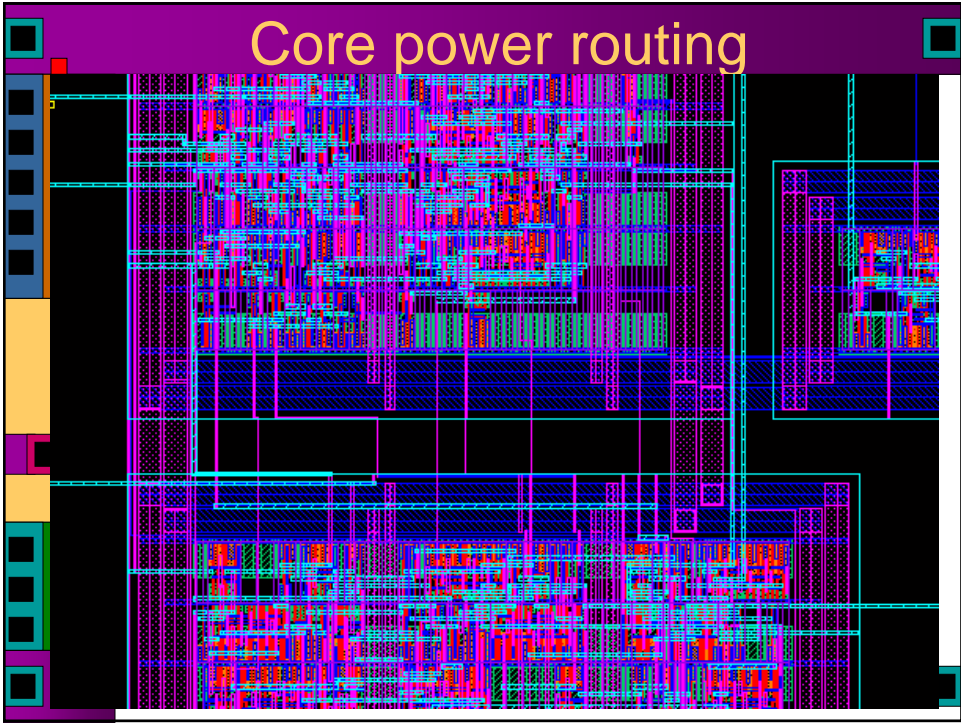- ▶ Power Routing is a global chip-wide issue
- ▶ Here's another approach
- ▶ Note the Vdd and Gnd pads
- ▶ Global rings with combs for regions of the chip



Chip-Wide View of Power

- ▶ Another view of the same issue
- ▶ Watch out for routing blockages!

The diagram illustrates a power distribution network on a chip. It features a central core with several functional blocks: two large yellow blocks on the left and right, a blue block at the top center, and several green blocks at the bottom. The core is surrounded by a power ring consisting of an outer Vdd loop and an inner Gnd loop. Internal jumpers connect the ring to the core blocks. Labels 'Vdd' and 'Gnd' are placed at various points along the rings and jumpers.

A Tweak on the Scheme


- ▶ Same basic scheme
- ▶ But with no internal jumpers
- ▶ Jumpers are restricted to outer loops

The diagram illustrates a power distribution network on a chip, similar to the one above, but with a different jumper configuration. The internal jumpers are restricted to the outer Vdd loop, and there are no jumpers connecting to the inner Gnd loop.

Adders Etc.


► Check out Chapter 10 in your text

Basic Addition: Full Adder

 

A	B	C_i	S	C_o	<i>Carry status</i>
0	0	0	0	0	delete
0	0	1	1	0	delete
0	1	0	1	0	propagate
0	1	1	0	1	propagate
1	0	0	1	0	propagate
1	0	1	0	1	propagate
1	1	0	0	1	generate
1	1	1	1	1	generate

Boolean Equations

 

- $SUM = A \oplus B \oplus C$
- $= C(AB + \bar{A}\bar{B}) + \bar{C}(\bar{A}B + A\bar{B})$
- $CARRY = AB + AC + BC$
- $= AB + C(A + B)$
- Above equations may be implemented as complex gates
- These equations may be manipulated to yield:
 $SUM = ABC + (A + B + C)\overline{CARRY}$

A Direct Implementation



 


Fig 10.3 in your text...

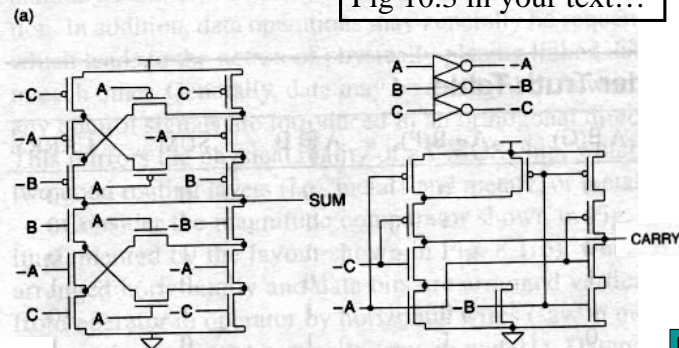

32 transistors


Use the Factored Equations

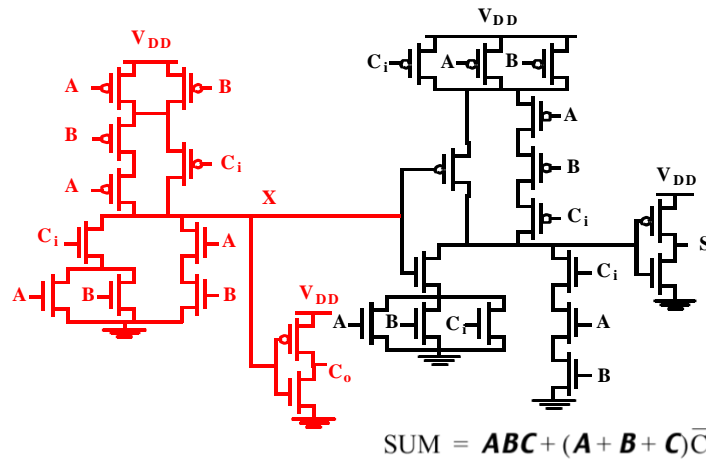

28 Transistors

► Fully static, complex gate implementation

Getting Rid of Inverters

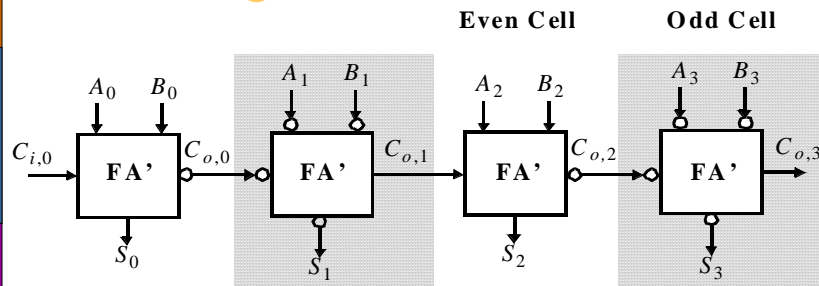


Exploit Inversion Property

Note: need 2 different types of cells


► Can improve performance by removing inverters from carry chain

A Better Static Gate

 

► Combine gates and reuse subterms

A Better Static Gate

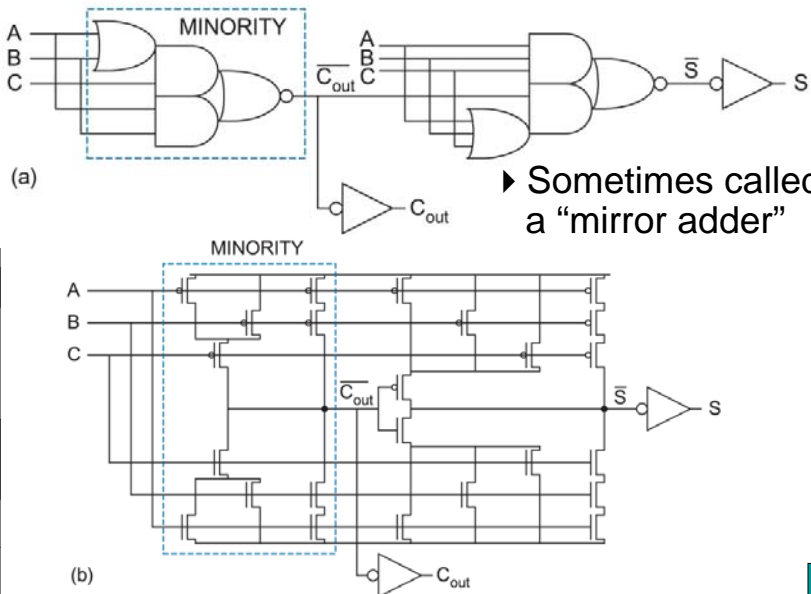


Mirror Adder Considerations


- Feed the Carry-In to the inner inputs so the internal capacitance is already discharged
- Make all transistors whose gates are connected to C_{in} and carry logic minimum size – minimizes branching effort on critical path (carry out)
- Determine gate widths by Logical Effort – reduce effort from C to C_{out} at the expense of Sum
- Use relatively large transistors on critical path so that stray wiring cap is a small fraction of overall cap

Adder Layout

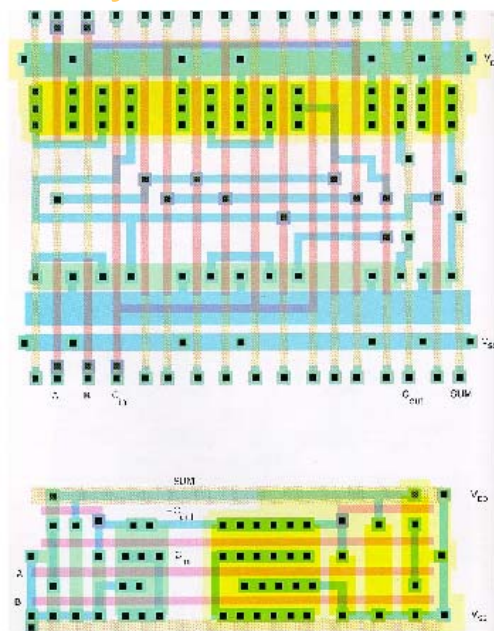- ▶ Examples from Weste and Eshraghian
- ▶ “Standard Cell” vs. “Datapath”
- ▶ Definitely worth looking at carefully






Datapath Layout

 

- ▶ A little tricky to figure out
 - ▶ You may not want to use this exact layout, but it might give you ideas
 - ▶ Start by identifying vdd and gnd paths
 - ▶ Think about rotating it ccw...
 - ▶ Think about a taller circuit that matches the bit-pitch of your register...

Datapath Layout

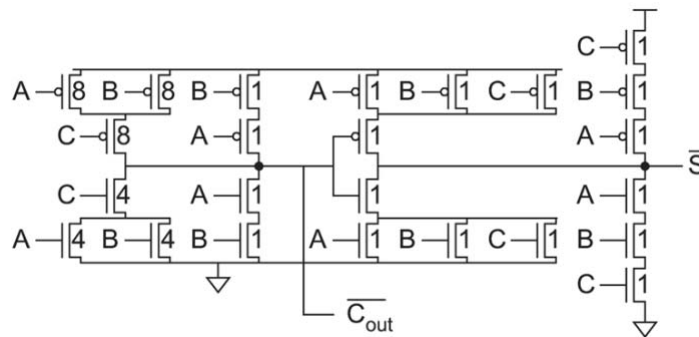 

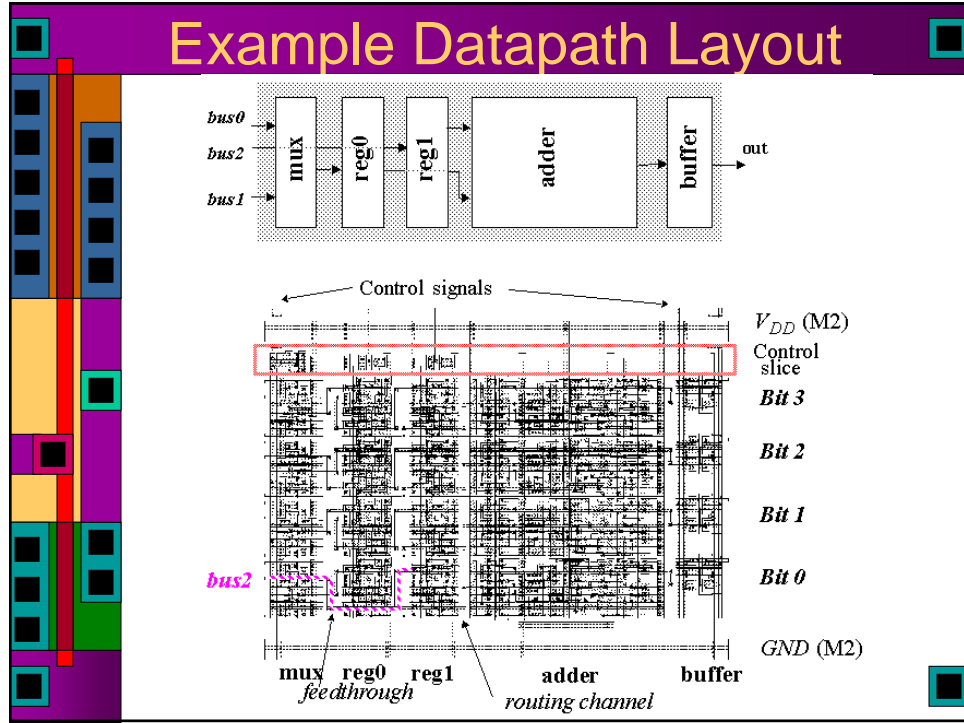


Addition and Subtraction

- ▶ Remember back to your logic design class
 - ▶ Add the two's complement to subtract
 - ▶ Take two's complement by inverting all the bits and adding one
 - ▶ Use the carry-in to add one
 - ▶ Use an XOR to invert or not


A	B	Out
0	0	0
0	1	1
1	0	1
1	1	0

Two's Complement Add/Sub

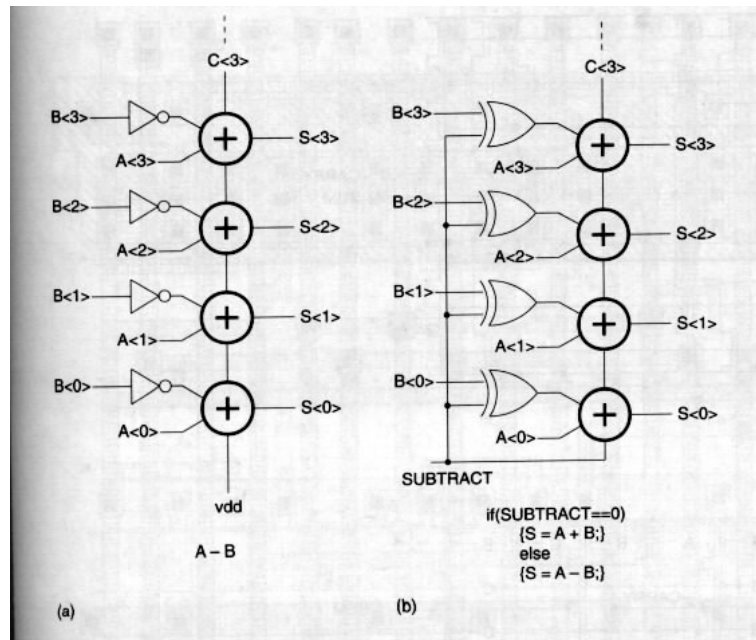


Aside: XOR Gates

 - ▶ Slightly tricky gate, $\sim AB + A\sim B$
- ▶ Lots of different schematics...




Another XOR gate

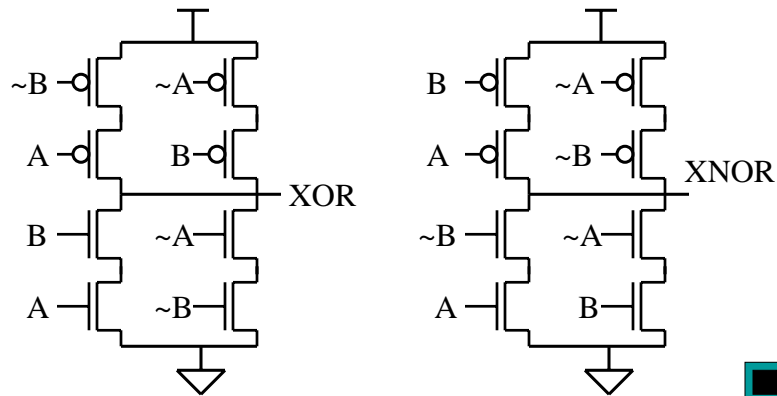- ▶ Not too bad if you already have A , $\sim A$, B , $\sim B$ floating around
 - ▶ If not, you'll need a couple inverters too...




Yet Another XOR Gate

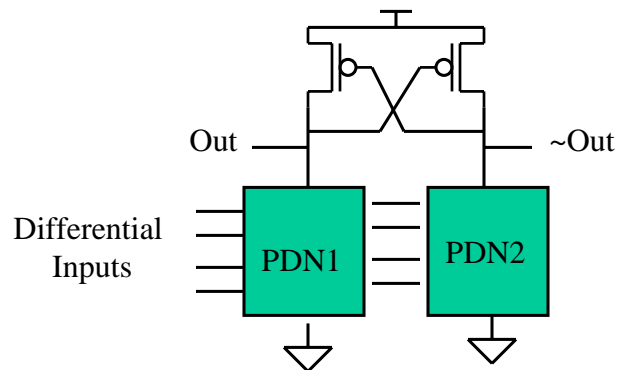- ▶ DCVSL (section 6.2.3 in your text)
 - ▶ Differential Cascode Voltage Switch Logic
 - ▶ Make sure that the combinational pull-down networks are complementary




DCVSL XOR/XNOR


 


- ▶ Generates both XOR/XNOR
- ▶ Still static, but might be slower than others


Another DCVSL Example

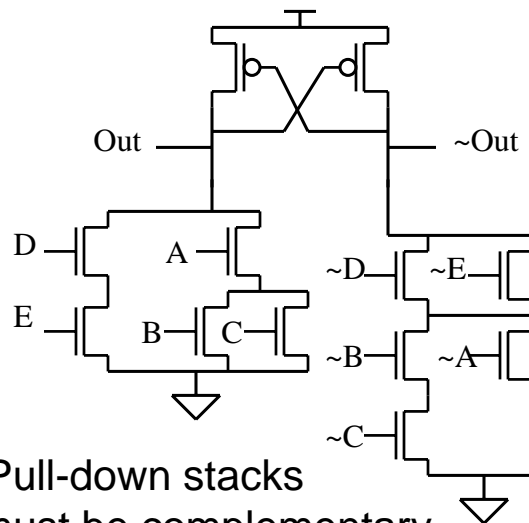

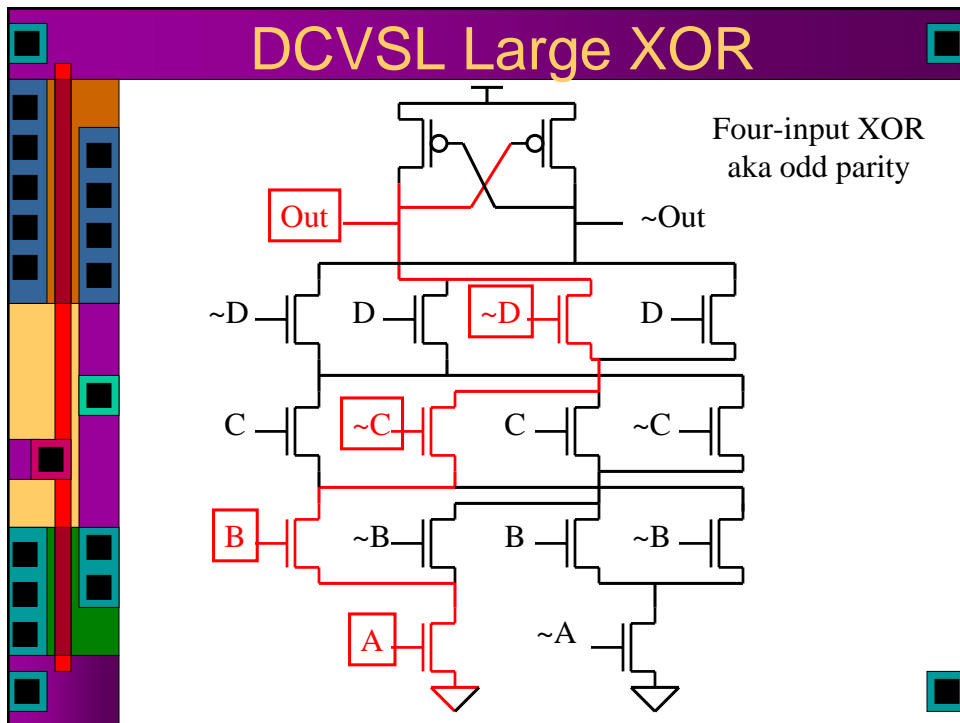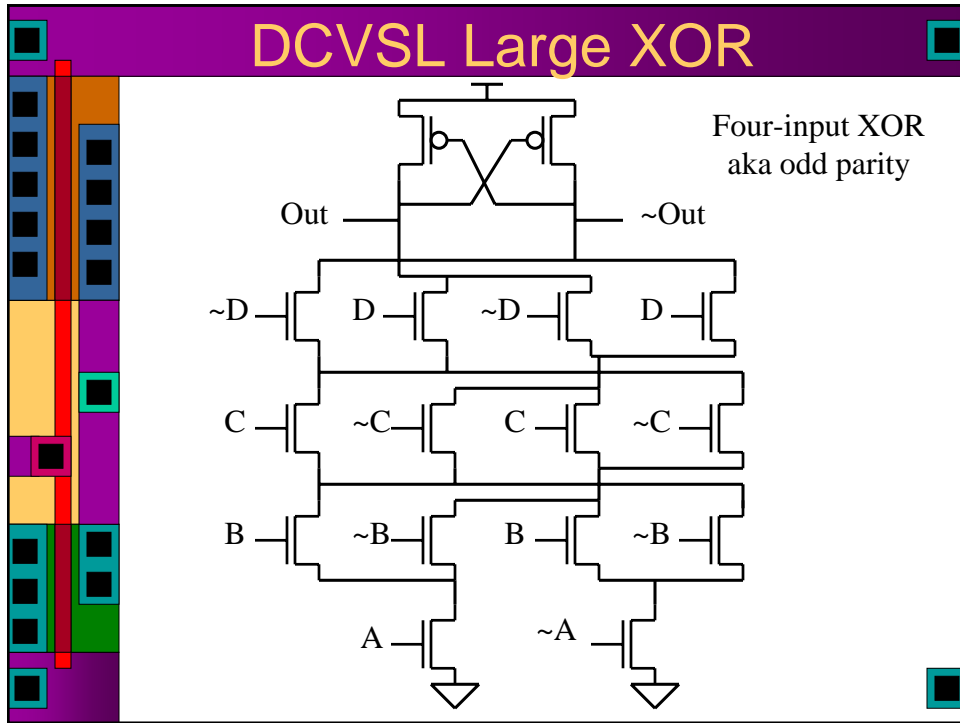
- ▶ Pull-down stacks must be complementary



DCVSL Large XOR

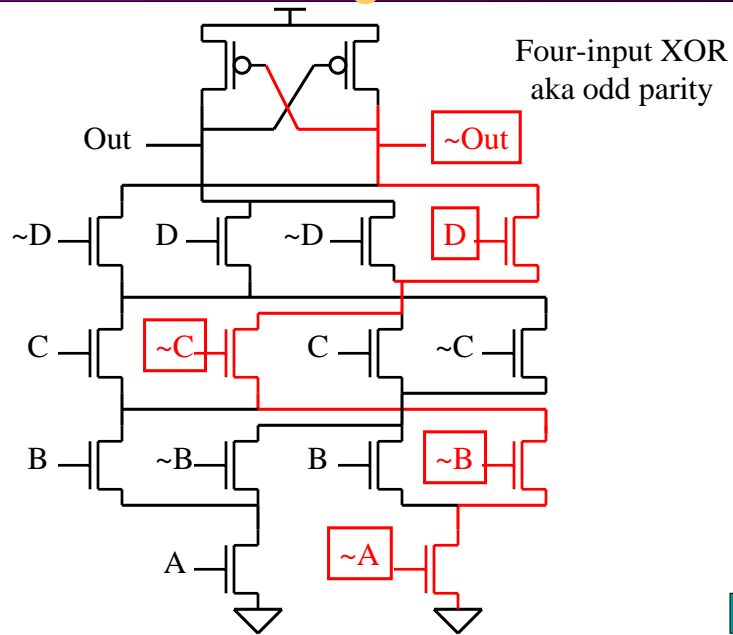

Transmission Gate XOR

 

- ▶ Tiny, clever circuit
 - ▶ If A is high, N1, P1 act like inverter
 - ▶ If A is low, B is passed to the output through transmission gate

Transmission Gate Adder

- Truth Table**

A	B	C	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- When $A \oplus B = 0$, SUM = C , and Carry = B .
- When $A \oplus B = 1$, SUM = \bar{C} , and Carry = C .
- Using the 6T XOR, this full adder uses 18T.


Another Version

Setup


Sum Generation

Carry Generation

Yet Another Version

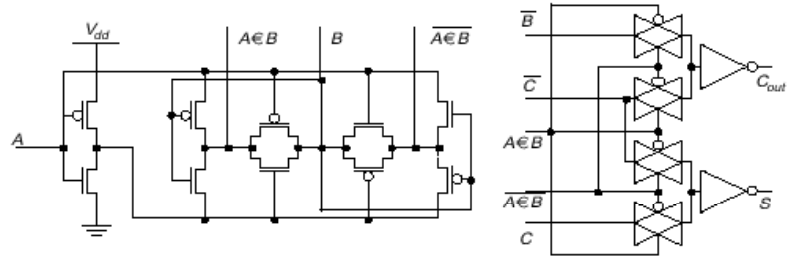


An Example Layout...

 

► Not the same style we're used to seeing...


More Pass Transistors

 - ▶ Complementary Pass Transistor Logic (CPL)
 - ▶ Slightly faster, but more area



Speeding Up Addition

 - ▶ It all comes back to the carry circuit
 - ▶ Ripple carry delay goes from low-order to high-order bit
 - ▶ This determines the speed of the addition




Delay is proportional to n

- ▶ Many many ways to speed up the carry calculation

Section 10.2.2 in your text

Carry Lookahead

 - A carry out C_i is generated from bit position i , when both A_i and B_i are '1' i.e. $G_i = A_i B_i$
- A carry in is propagated to the carry out at bit position i when either A_i or B_i is '1' (if both are '1' G_i will cover) e.g. $P_i = A_i \oplus B_i$



$$\text{Sum} = P \oplus C_i$$


complex gate (6T)

- Thus the carryout, $C_i = G_i + P_i C_{i-1}$
- ▶ Key is that the carry depends ONLY on A and B, not the carry-in
- ▶ Catch is that the gates have large fan-in

Carry Lookahead


- ▶ Restated: $C_i = G_i + P_i C_{(i-1)}$
- ▶ $C_0 = G_0 + P_0 C_{in}$
- ▶ $C_1 = G_1 + P_1 C_0$
 $= G_1 + P_1(G_0 + P_0 C_{in})$
 $= G_1 + P_1 G_0 + P_1 P_0 C_{in}$
- ▶ $C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_{in}$
- ▶ $C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_{in}$
- ▶ Or $C_3 = G_3 + P_3(G_2 + P_2(G_1 + P_1(G_0 + P_0 C_{in})))$

Carry Lookahead

 


- ▶ The C equations get larger with each stage
- ▶ Usually do lookahead in small blocks (i.e. 4) and the combine in a tree


Carry Lookahead Logic

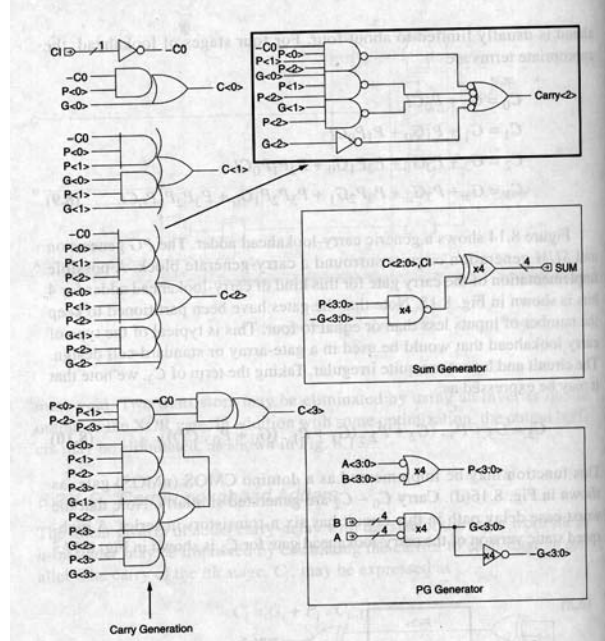


Fast Carry Lookahead Logic

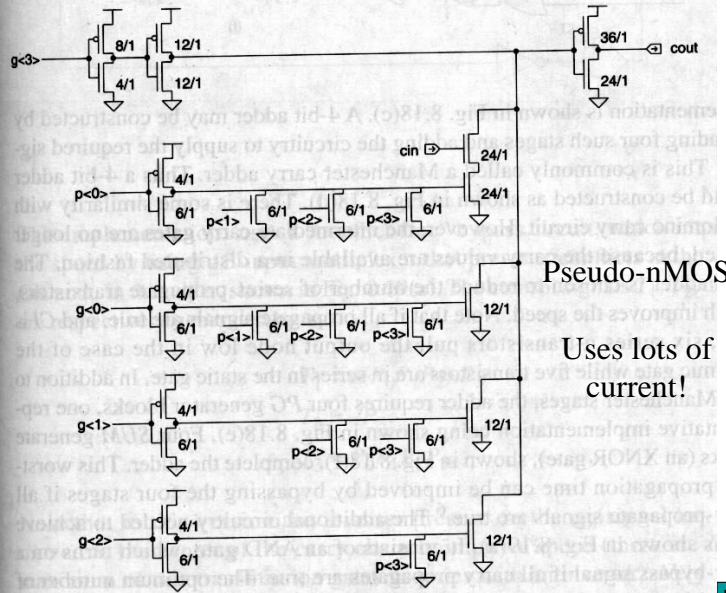


Another Version

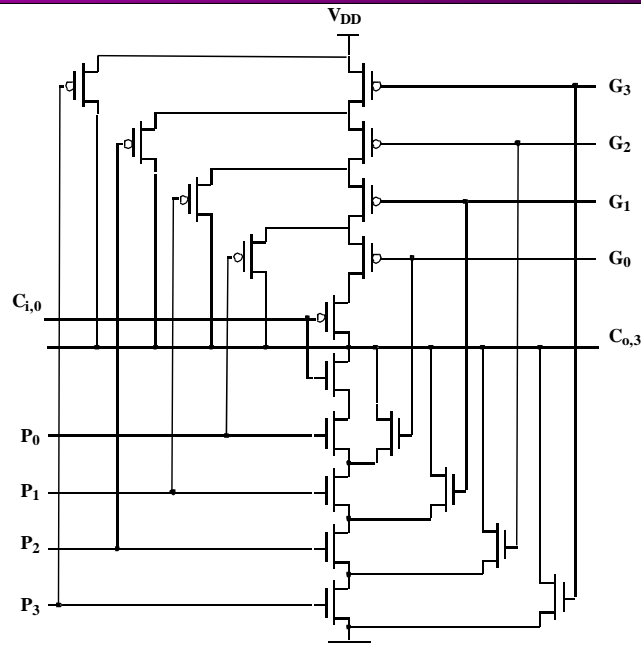


Another View

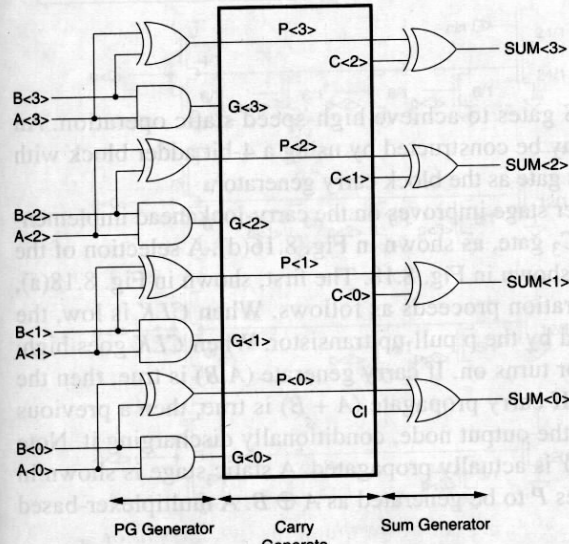


Another View

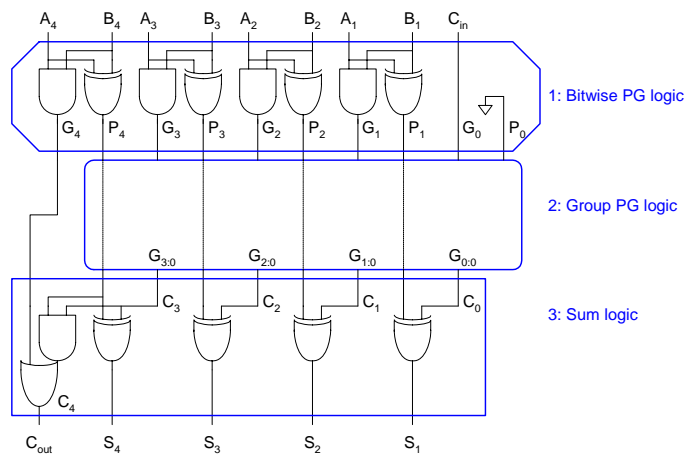

Ripple Carry

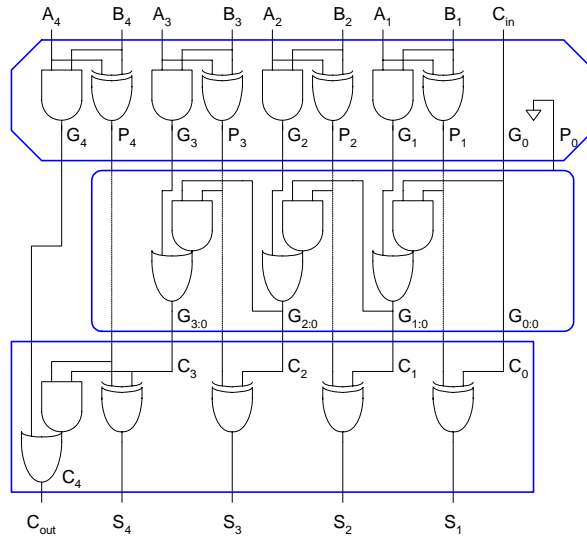


PG Diagram Notation

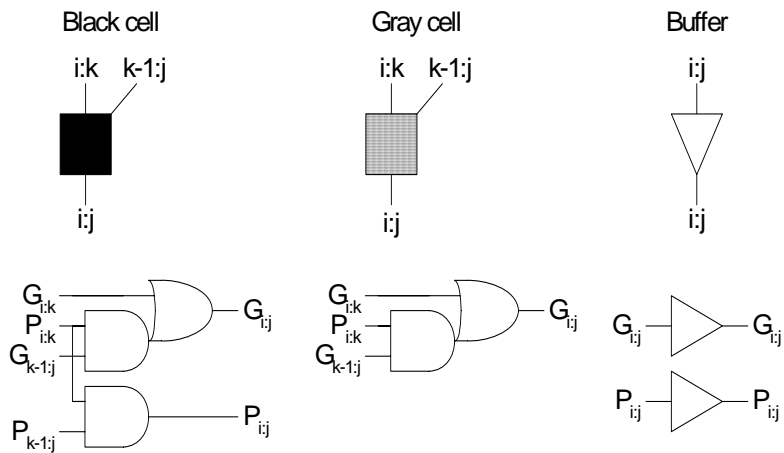


Ripple Carry
 
$$t_{\text{ripple}} = t_{pg} + (N - 1)t_{AO} + t_{xor}$$




Carry-Lookahead Adder

 
- ▶ Carry-lookahead adder computes $G_{i:0}$ for many bits in parallel.
- ▶ Uses higher-valency cells with more than two inputs.



CLA PG Diagram

 


Higher-Valency Cells

 

Carry-Select Adder


▶ Carry-Select

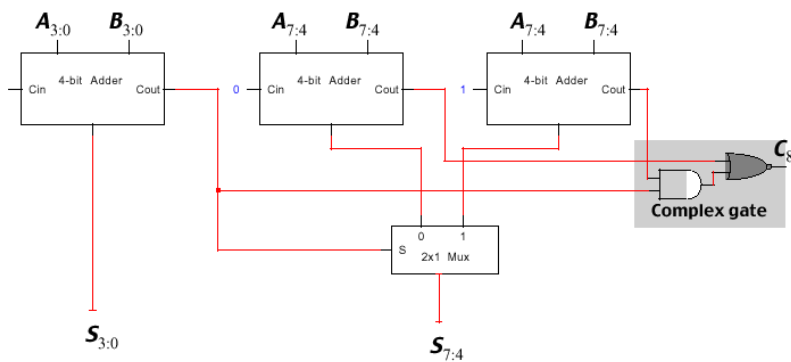- ▶ Compute result for a block based on carry-in of 1 and carry-in of 0, then select the right one




Carry-Select Adder

 - ▶ Trick for critical paths dependent on late input X
 - ▶ Precompute two possible outputs for $X = 0, 1$
 - ▶ Select proper output when X arrives
- ▶ Carry-select adder precomputes n-bit sums
 - ▶ For both possible carries into n-bit group




Carry-Skip Adder

 - ▶ Compute the P and G for an entire block
- ▶ If the block generates or kills, don't propagate



Carry-Skip PG Diagram

 


$$t_{\text{skip}} = t_{pg} + [2(n-1) + (k-1)]t_{AO} + t_{xor}$$

For k n -bit groups ($N = nk$)


Tree Adder

- ▶ If lookahead is good, lookahead across lookahead!
 - ▶ Recursive lookahead gives $O(\log N)$ delay
- ▶ Many variations on tree adders


Brent-Kung

 

Sklansky

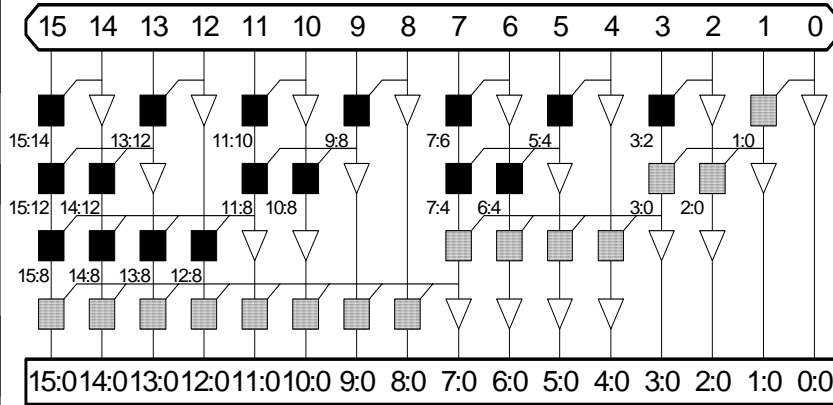


Kogge-Stone

 

Manchester Carry Chain


► Instead of changing the architecture of the adder, use a clever circuit to ripple the carry more effectively

 - Propagate and generate signals computed in about two gate delays
- Active low carry is propagated through a chain of transmission gates
- The three shaded areas of the circuit are mutually exclusive, and represent P_i , G_i , and $\overline{P_i G_i}$.




Alternate Implementation

 - The Manchester carry chain computation may also be implemented with a 2x1 mux.



Four Bit Block

 - Signal propagation through a chain of transmission gates must be restored after about 4 gates



- A block propagate (bypass) circuit may be added to further improve performance on wide adders


Summary

Adder architectures offer area / power / delay tradeoffs.

Choose the best one for your application.

Architecture	Classification	Logic Levels	Max Fanout	Tracks	Cells
Carry-Ripple		$N-1$	1	1	N
Carry-Skip $n=4$		$N/4 + 5$	2	1	$1.25N$
Carry-Inc. $n=4$		$N/4 + 2$	4	1	$2N$
Brent-Kung	$(L-1, 0, 0)$	$2\log_2 N - 1$	2	1	$2N$
Sklansky	$(0, L-1, 0)$	$\log_2 N$	$N/2 + 1$	1	$0.5 N \log_2 N$
Kogge-Stone	$(0, 0, L-1)$	$\log_2 N$	2	$N/2$	$N \log_2 N$

Design as Trade-Off

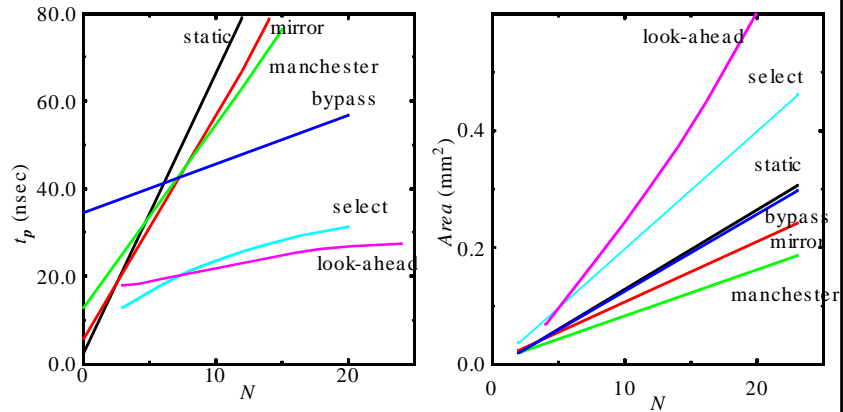

- ▶ Do you want speed or size?
- ▶ There's always power to consider too...

How well does Synopsys do?

 


FIG 10.47 Area vs. delay of synthesized adders


- ▶ Design compiler using a 180nm library

What should you use?

- ▶ Ripple if timing allows
 - ▶ Compact, easy
- ▶ CLA or carry-skip work well for 8-16 bits
- ▶ For 32, and especially 64 bits tree adders are faster
- ▶ Adders designed and tiled by hand will be much smaller (and probably faster) than synthesized adders


Logic Functions

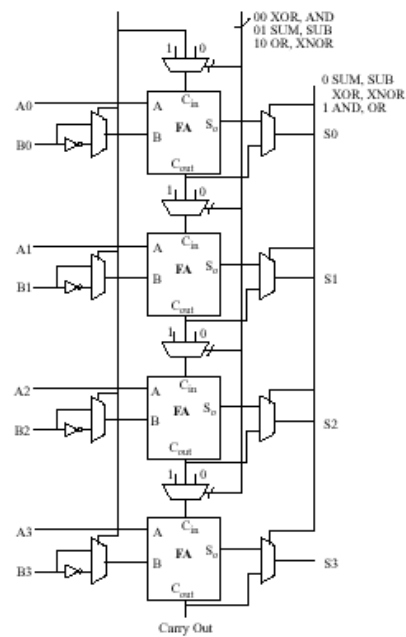- ▶ Use the features of the full adder cell to generate logic functions
- ▶ Lots of other ideas in your text...




General Logic Generator

 - 4x1 multiplexor can implement any function of two variables




- Simply place the truth table for F on the inputs of the mux.
- The operands A and B will select the correct value of the function


One Possible MUX Version

 

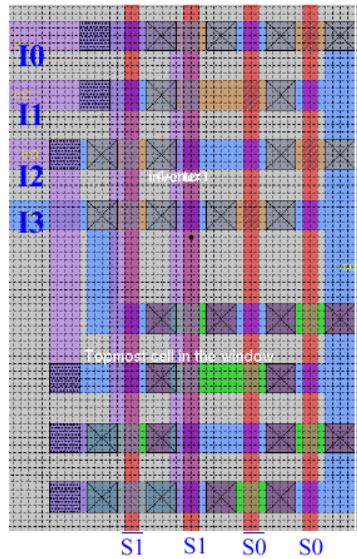- Note: Two t-gates in series do not need the internal connection between p-fet and n-fet




Remember the Big Picture

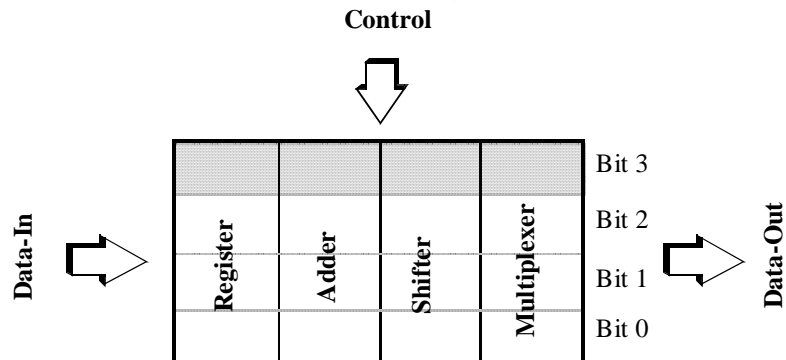

- ▶ We want things to stack up nicely in the datapath

Shifters

 

- ▶ Essentially a muxing operation... select the shift you want (section 10.8)

Barrel Shifter

— : Data Wire
 - - : Control Wire

- ▶ Shift any number of bits in one shot
- ▶ Clever layout is possible...
- ▶ Lots of wiring...

Barrel Shifter

— : Data Wire
 - - : Control Wire

- ▶ Shift any number of bits in one shot
- ▶ Clever layout is possible...
- ▶ Lots of wiring...

