Pad Capacitance Extraction SPICE Simulations

Hazem Hegazy IBIS Development Engineer

June 13, 2002 IBIS Summit Meeting New Orleans, Louisiana

R

Agenda

- Why it's so important !!!
- Time domain methods
- Frequency domain technique
 - Sweeping the whole domain
 - **Tank construction**
 - Enhancement





Time Domain Methods

- Apply ramp voltage source (b*t) & measure the current.
- Subtract DC current in pull up/down device.
- C(t) = (I1 I2)/2b =
 (I(t)_{Source}- I(t)_{Device})/b.
 Ccomp varies with b !!!!





Time Domain Capacitance





Frequency Domain Technique

- Time domain methods fails to give one simple result.
- Frequency domain analysis might be the alternative !!
- Spice AC analysis is a <u>small signal</u> time averaging per unit cycle.
- Enhancements to emulate large signal response.



Sweeping the Whole Domain



Graphics

Tank Construction

- Capacitance physically exists.
- It only varies with voltage.
- Adding Shunt L for resonance.
- Ccomp frequency dependence is omitted.
- One single value for Ccomp.









Graphics

Voltage Dependence





Final Comparison







Summary

- Hard to get straight answer from time domain methods.
- Can't calculate Ccomp from a simple sweep of frequency domain (Which frequency will you take?).
- Tank method gives accurate answer at each voltage value.
- Large variation of Ccomp is a limitation for tank method as well as <u>IBIS standard</u>.



