



Modeling on-die terminations in IBIS (without double counting)

IBIS Summit at DAC 2003

Marriott Hotel, Anaheim, CA

June 5, 2003

IBIS Summit at DesignConEast 2003

Royal Plaza Hotel Marlborough, MA

June 23, 2003

Arpad Muranyi
Signal Integrity Engineering
Intel Corporation
arpad.muranyi@intel.com



Outline

- **Summary of advanced buffer features**
- **General guidelines for making models for buffers with advanced features**
- **Static parallel termination**
 - Algorithms to avoid double counting
- **Switched parallel termination**



Advanced buffer modeling

- **Pullup or pulldown “resistors”**
 - they prevent 3-stated buses from floating around the threshold voltages
 - usually in the $k\Omega$ range (I_{sat} in μA range)
 - usually implemented as a transistor turned on constantly
- **Integrated terminators**
 - static transmission line termination (low impedance)
 - dynamic implementations designed to save power
- **Bus hold circuits (may be dynamic)**
 - similar to pu/pd resistor idea, but usually has a lower impedance
 - could be time, edge or level dependent if dynamic
- **Dynamic clamping mechanisms**
 - strong clamps turn on momentarily to prevent excessive overshoot
- **Staged buffers**
 - mostly used in slew rate controlled drivers
- **Kicker circuits**
 - transition boosters and then turn off
- **Anything else you can invent goes here...**

Modeling static advanced features




- **Anything that is ON constantly should be modeled using the [Power Clamp] or [GND Clamp] I-V curves**
 - pullup or pulldown “resistors”
 - static integrated terminators
 - static clamps, ESD circuits
 - static bus hold circuits
- **Make sure you are using the appropriate rail for correct power and GND bounce simulation purposes**
 - use [Power Clamp] for pullup resistor
 - [GND Clamp] for pulldown resistor, etc.
- **Some additional post processing may be required to avoid double counting**

Modeling dynamic advanced features



- **Use IBIS version 3.2 features**
 - keywords: [Driver Schedule],
[Add Submodel], [Submodel], [Submodel Spec]
 - subparameters: Dynamic_clamp, Bus_hold
- **Detailed knowledge of circuit behavior is required**
- **Familiarity with buffer's SPICE netlist required**
- **May have to dissect or modify SPICE netlist to generate necessary data in separate steps**
- **It may not be possible to make such models from simple and/or direct lab measurements**

Block diagram of a CMOS IBIS model

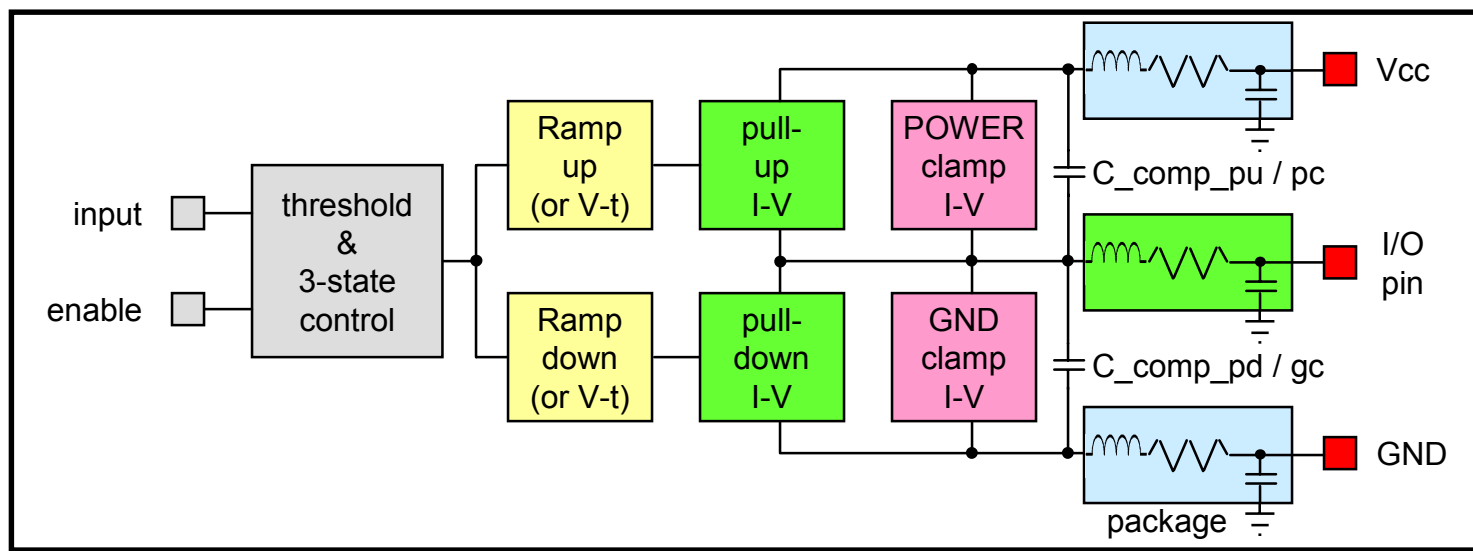


- **Power/GND clamp IV curves are always ON**
 - Use these for everything that is static
 - Parasitic diodes
 - ESD circuits
 - On-die terminations, etc...
- **Pullup/Pulldown IV curves are switched ON/OFF by the Ramps/Vt curves**
 - Use these for everything that is switched or dynamic
 - Drivers, “kickers”
 - Dynamic clamps
 - Dynamic on-die terminations, etc...

On-die terminations


- **Series termination**
 - does not require any special work because it is described by the shape of the I-V curve
- **Parallel termination**
 - if the parallel termination is on all the time, use the method described for pullup/pulldown resistors
- **Switched parallel termination**
 - the parallel termination device is turned off while the opposite half of the buffer is driving
 - make a normal complementary model for the driver portion of the buffer
 - make a difference I-V curve for the terminator device and use the **[Add Submodel]** keyword in **non-driving** mode with the **[Submodel]** keyword's **dynamic_clamp** in static mode (without a pulse)

Pullup resistor example

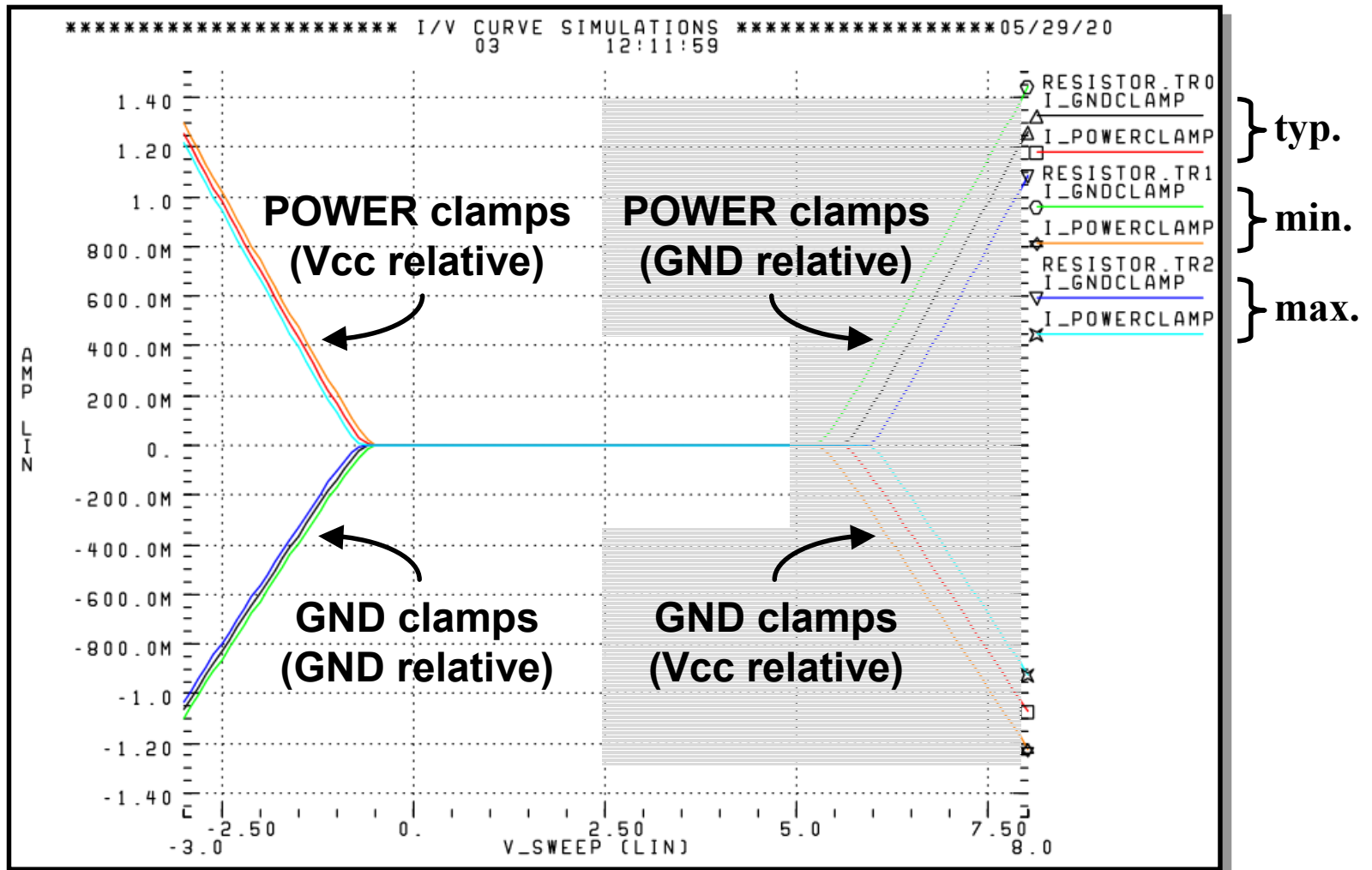


I-V curves of a 3-stated buffer with pullup R

Zooming in on I-V curves

 


Algorithm in pictures

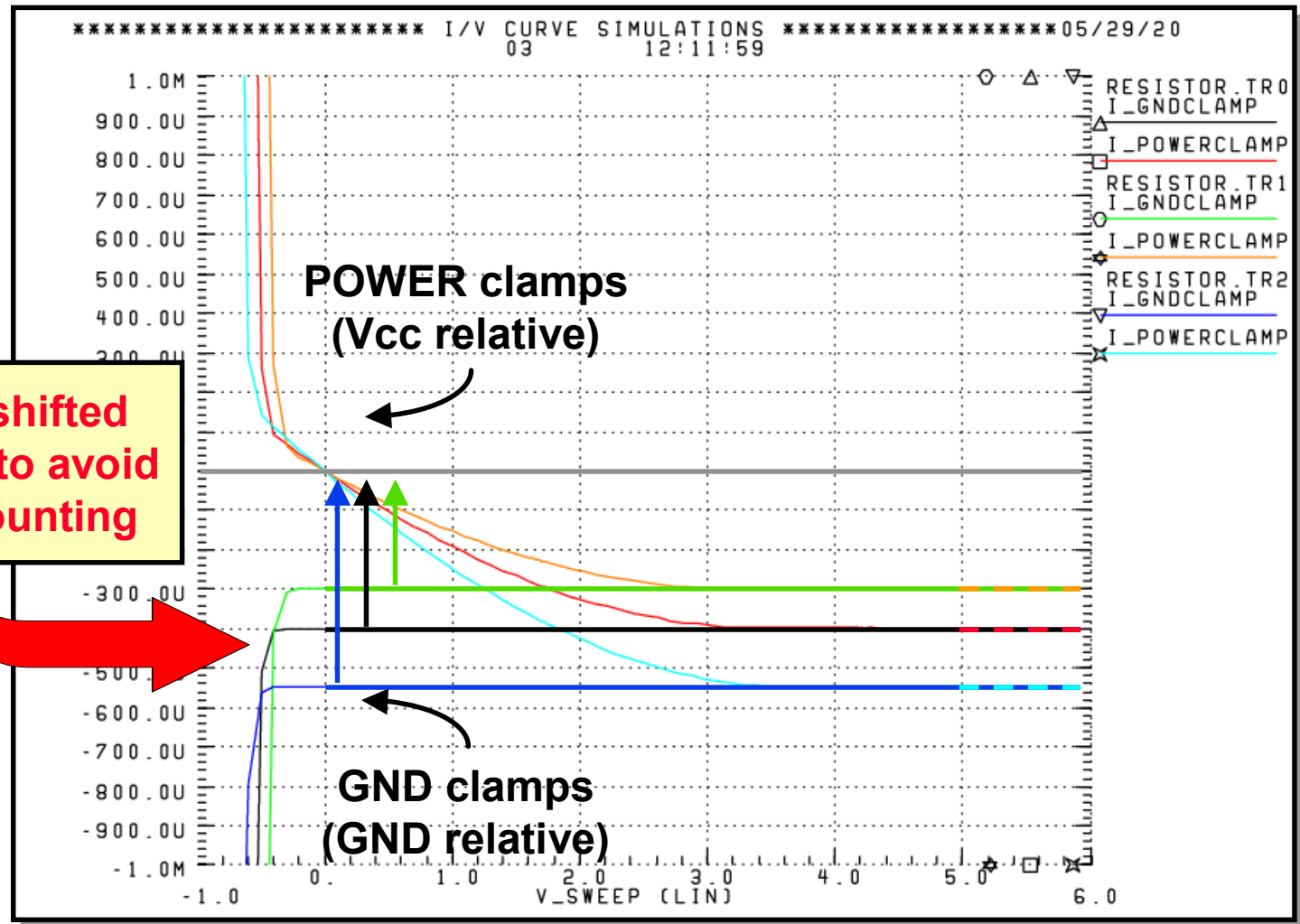

Algorithm in words


- Sweep device from $-V_{cc}$ to $2*V_{cc}$ twice:
GND and V_{cc} relative
- Cut clamp curve which will include the resistor at V_{cc}
 - This can be automated by detecting which group of IV curves goes through the origin
- Cut other clamp curve at 0V
- Normalize (shift) the clamp curve which will not include the resistor to zero current at 0V
- Extrapolate both clamp curves horizontally to $2*V_{cc}$

Pullup and pulldown resistor example

 


- Looking into the output pad we see $R_{thevenin}$
- It is not possible to separate $R_{thevenin}$ into R_{pu} and R_{pd} from a single measurement at the pad
- The algorithm described on the following pages is only a crude approximation, but it may be better than leaving everything in one IV curve
 - Useful for POWER and GND bounce simulations

IV curves of pu and pd R example

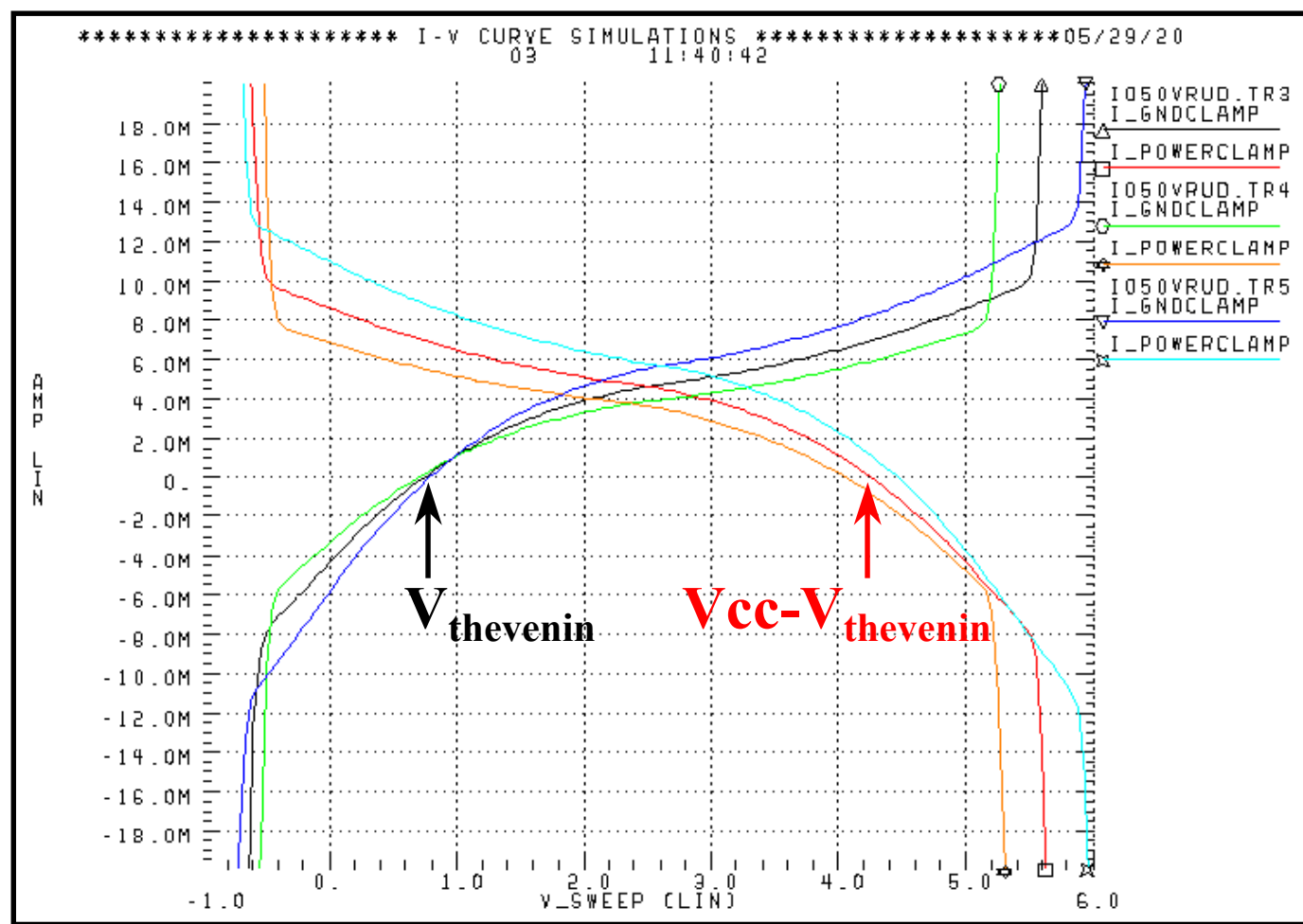

I-V curves of a 3-stated buffer with both pu and pd R

Algorithm in pictures

 

Algorithm in words

- Sweep device from $-V_{cc}$ to $2*V_{cc}$ twice:
GND and V_{cc} relative
- Cut clamp curves where they reach zero current
going left to right
- Extrapolate all clamp curves horizontally to $2*V_{cc}$

Switched parallel termination example

- This buffer is a normal CMOS driver, but its pullup is ON in receive mode acting as a parallel terminator

```
*****
[Add Submodel]
| Submodel name      Mode
ParTerm              Non-Driving
*****

[Submodel]      ParTerm
Submodel_type   Dynamic_clamp
*****

[POWER Clamp]

      Voltage          I (typ)          I (min)          I (max)

      -1.79999995E+0    14.23263550E-3    17.10075140E-3    12.31312752E-3
      . . .
      . . .
The I-V curve table of the [Pullup] is repeated here, because the
terminator is actually the pullup left on in receive mode.
      . . .
      . . .
      3.59999990E+0    -44.34032738E-3    -44.32120919E-3    -48.62782359E-3
*****
```