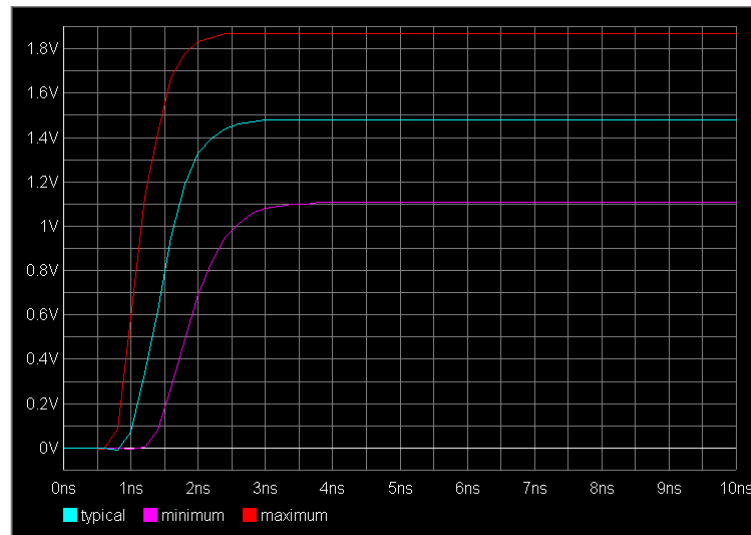


Things You Can Learn From V/I Curves


**IBIS Summit / DAC 2005
Todd Westerhoff
Cisco Systems, Inc.**

Components of a [Model] Declaration

Cisco.com



V/T Curves

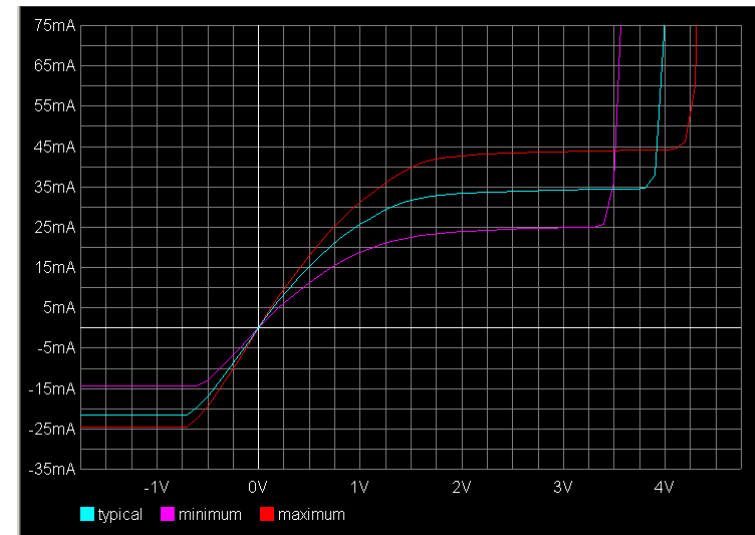


V/I Curves

- Pullup/Pulldown
- PWR/GND Clamps


For Purposes of this Presentation ...

Cisco.com

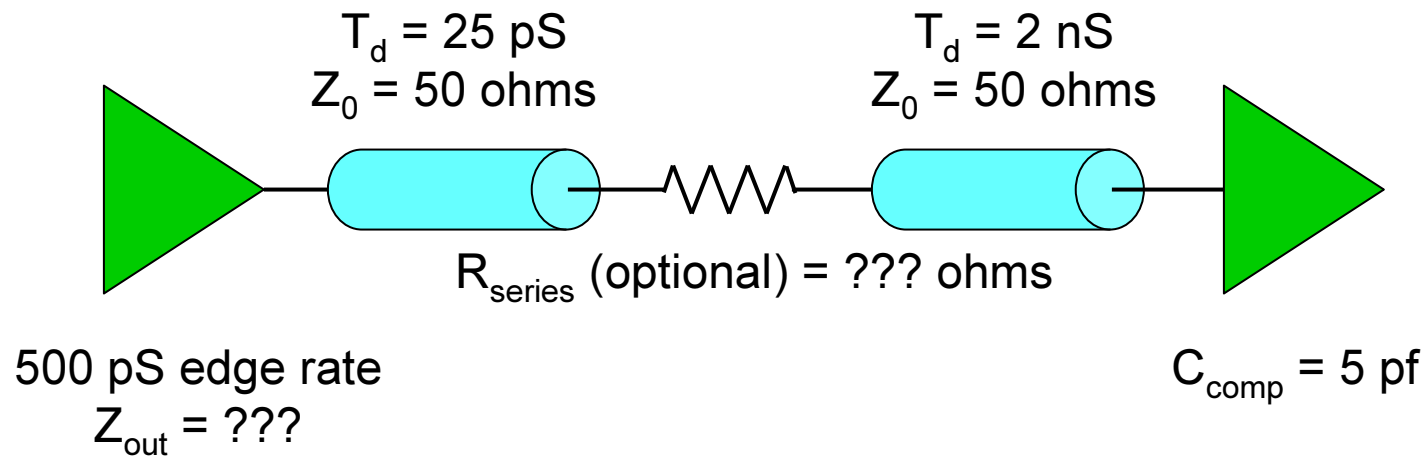


Electrically ...

Cisco.com

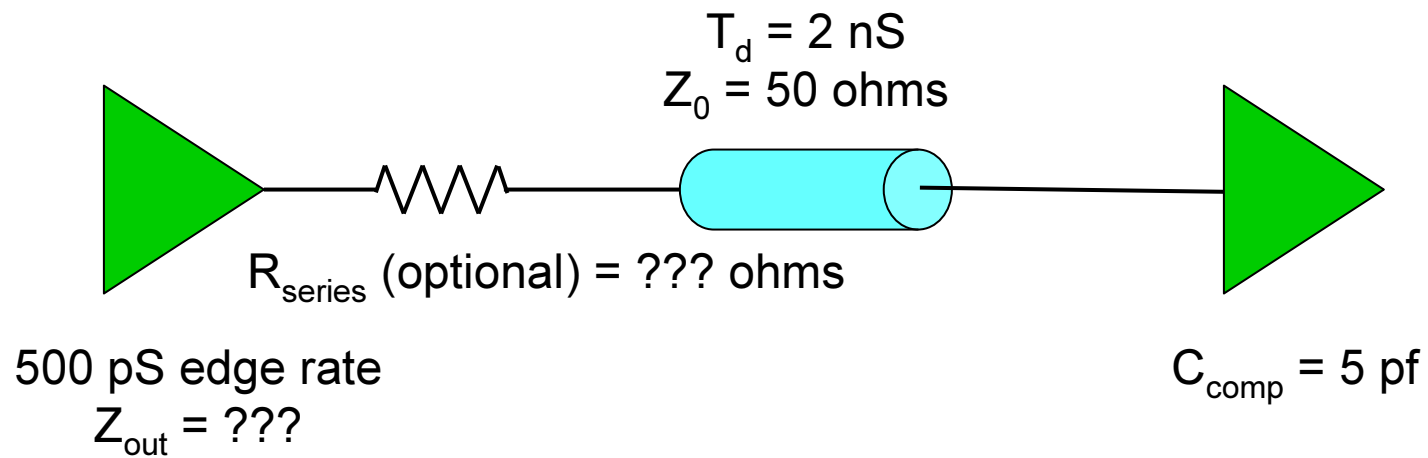


Rising Edge Behavior, $t=0$

Cisco.com

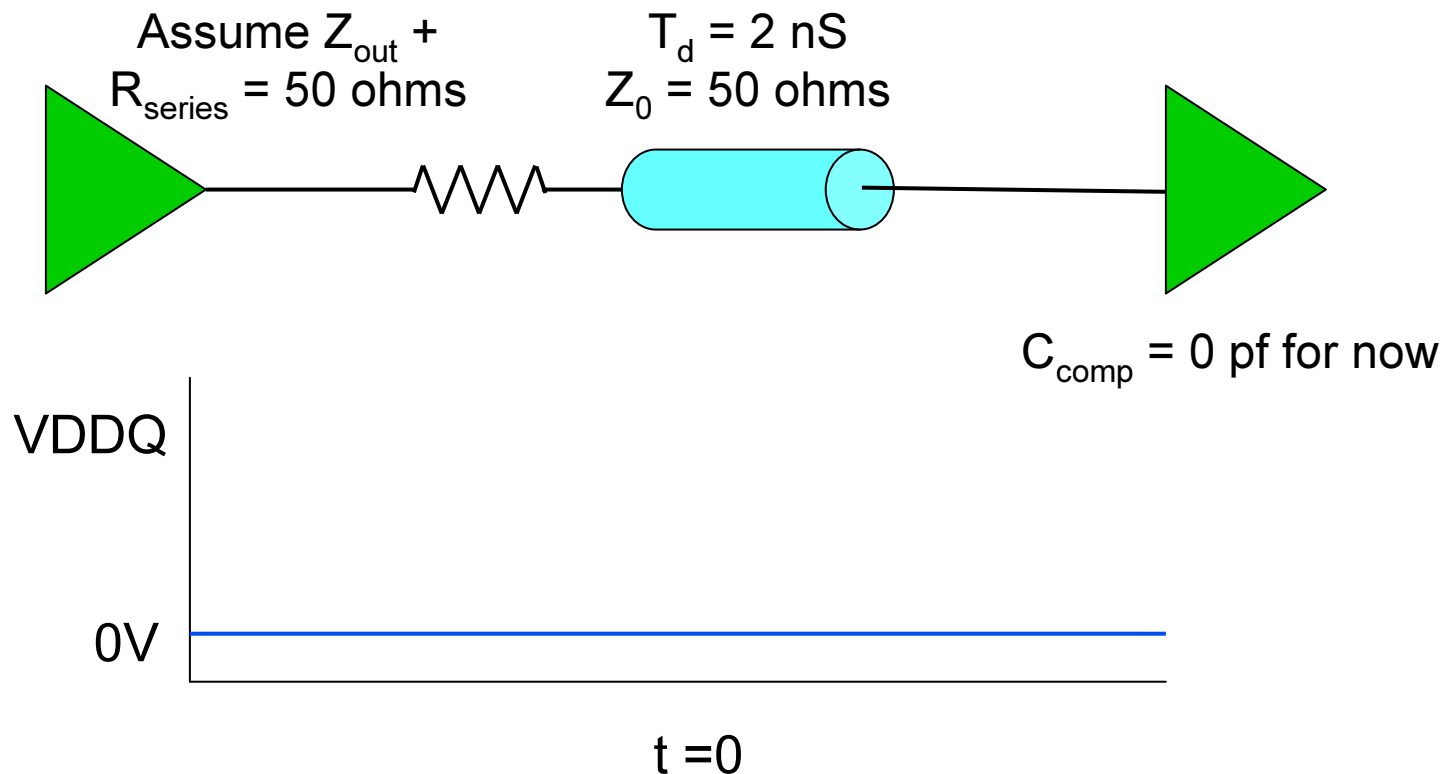


Rising Edge Behavior, $t=500\text{ps}$

Cisco.com

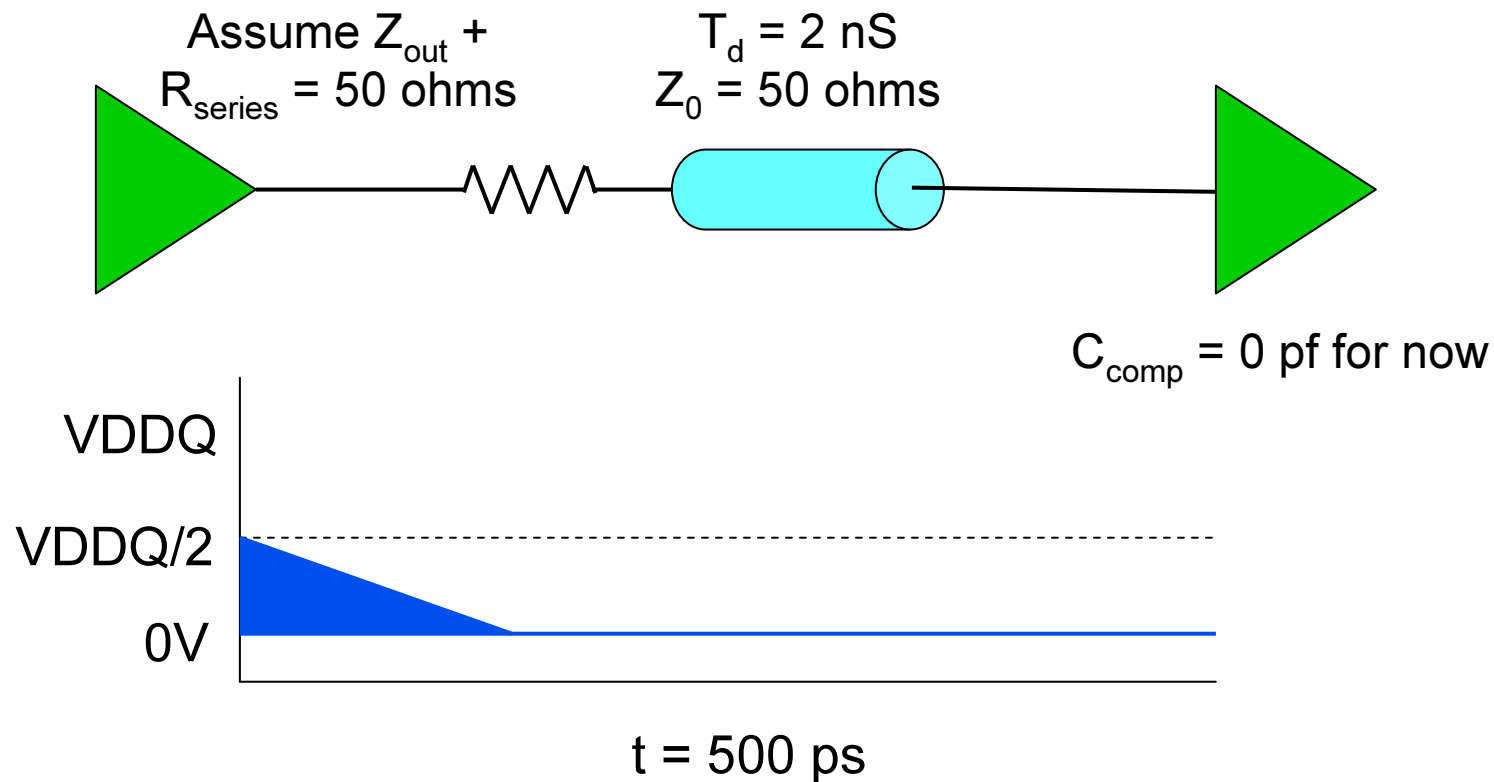


Rising Edge Behavior, $t=1\text{ns}$

Cisco.com

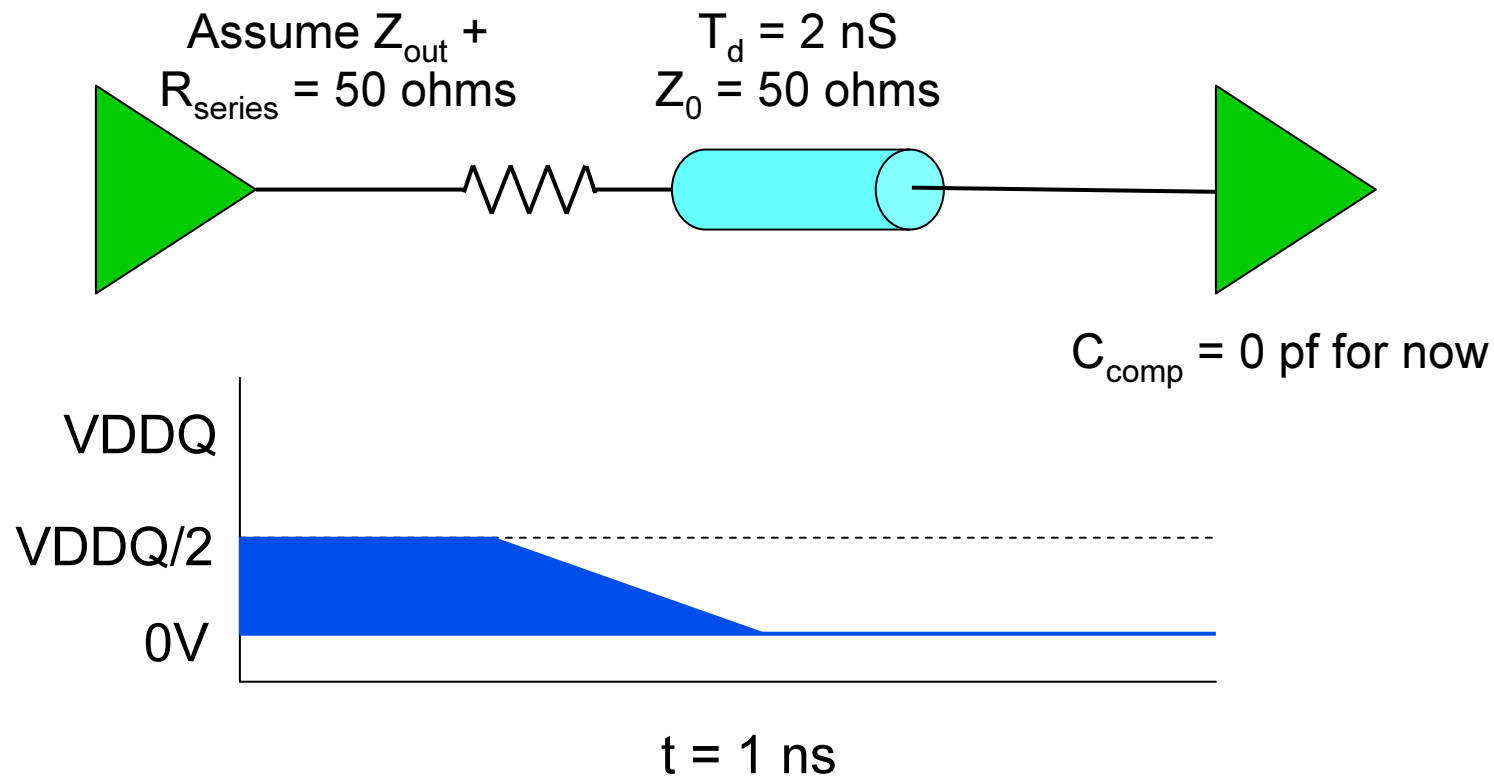


Rising Edge Behavior, $t=2\text{ns}$

Cisco.com

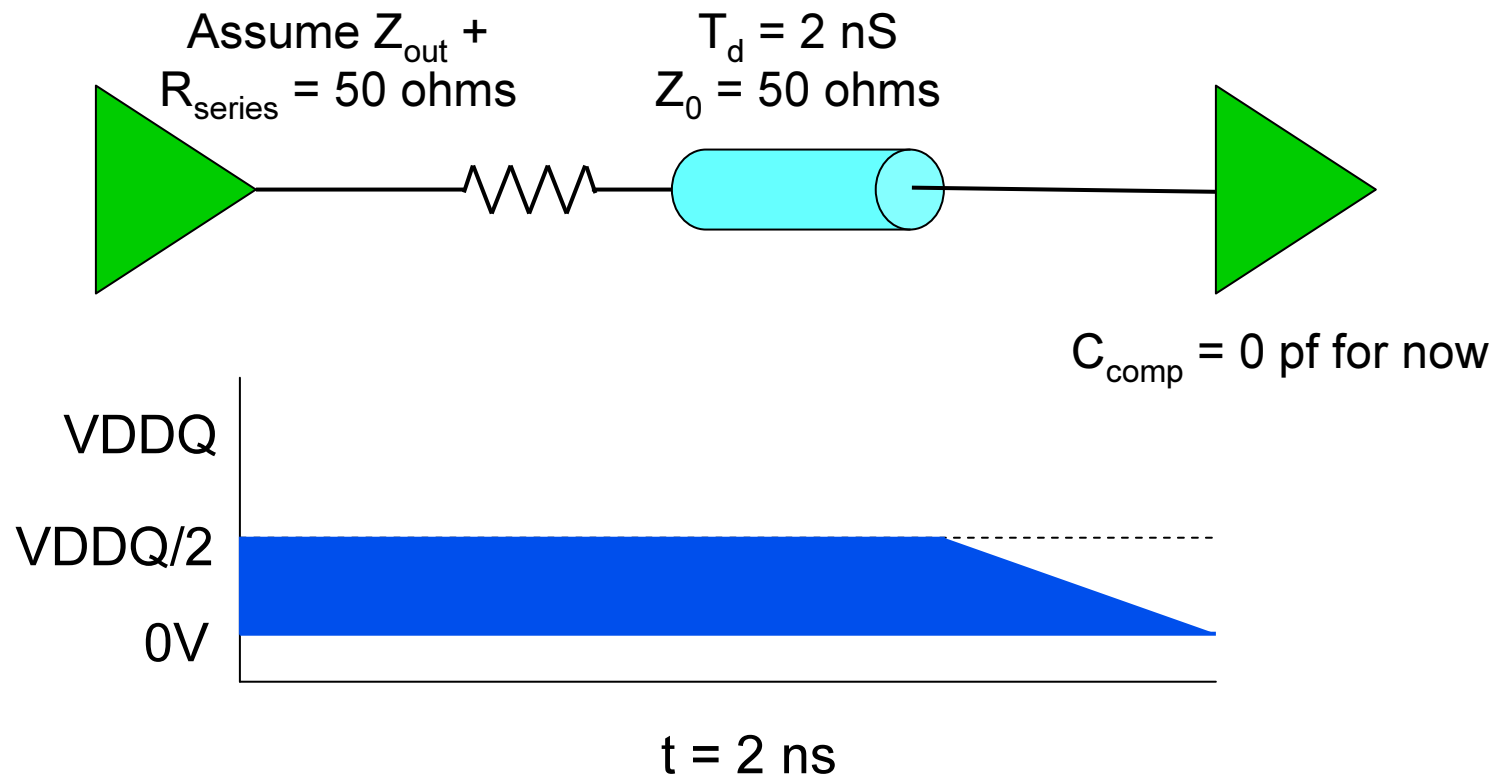


Rising Edge Behavior, $t=2.5\text{ns}$

Cisco.com

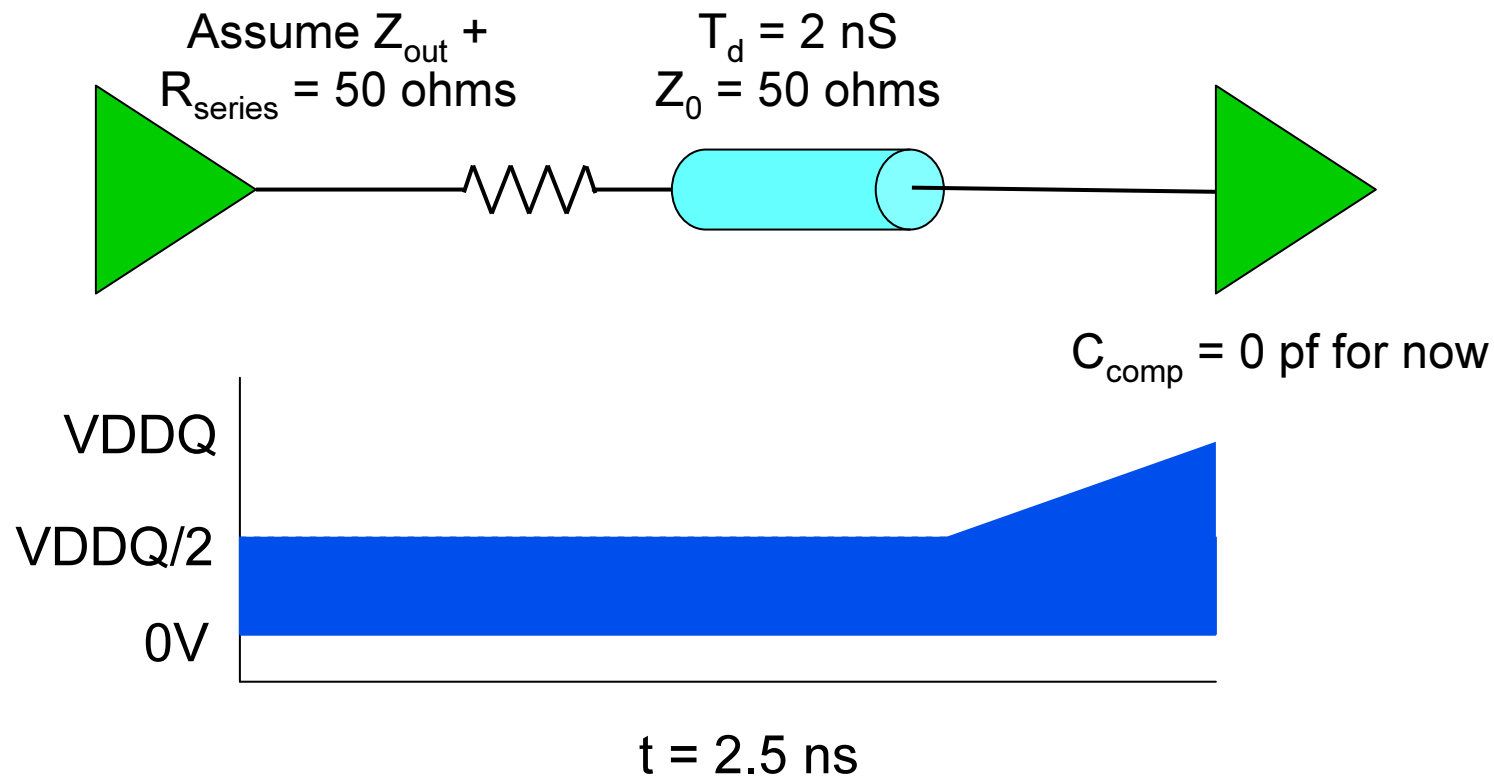


Rising Edge Behavior, $t=3\text{ns}$

Cisco.com

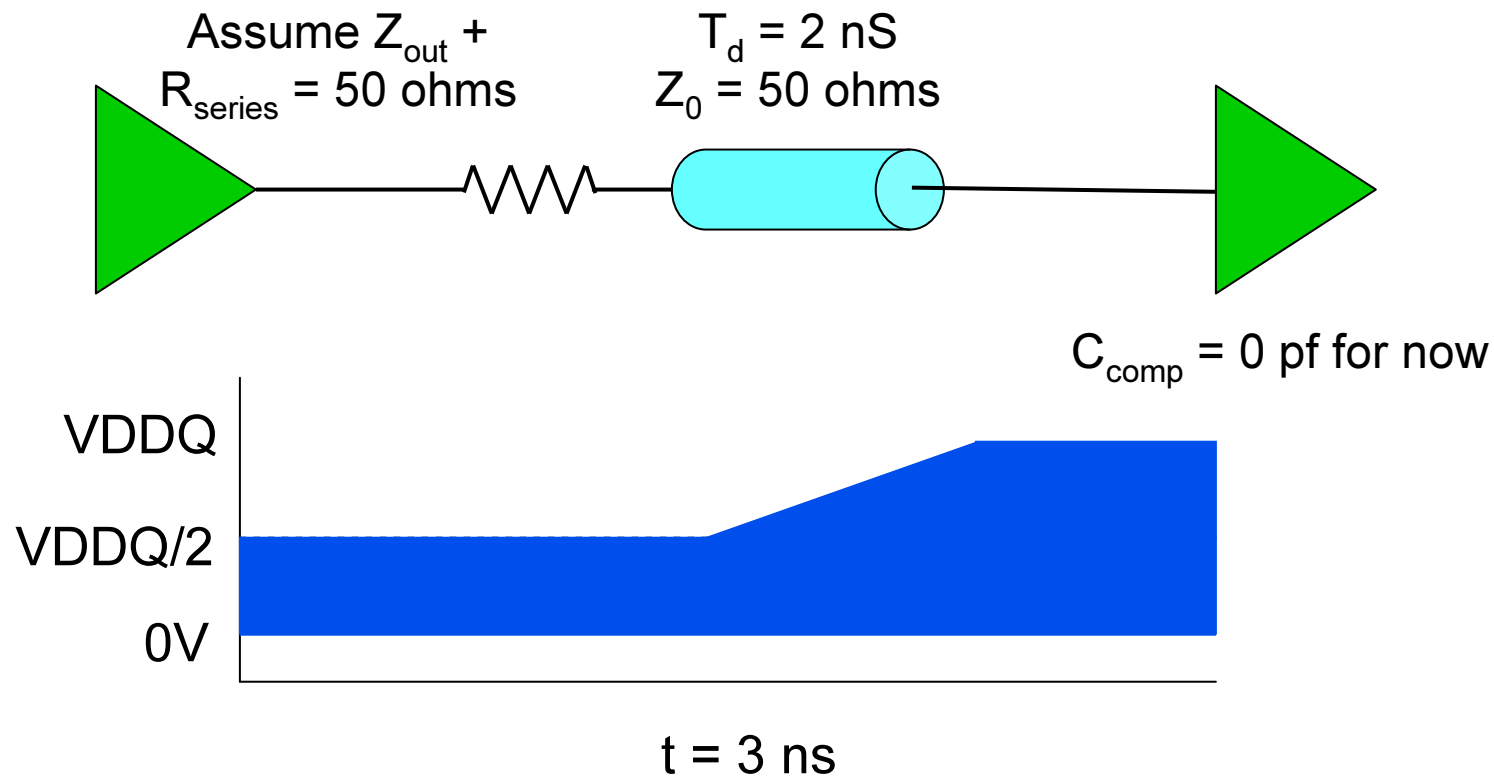


Rising Edge Behavior, $t=4\text{ns}$

Cisco.com

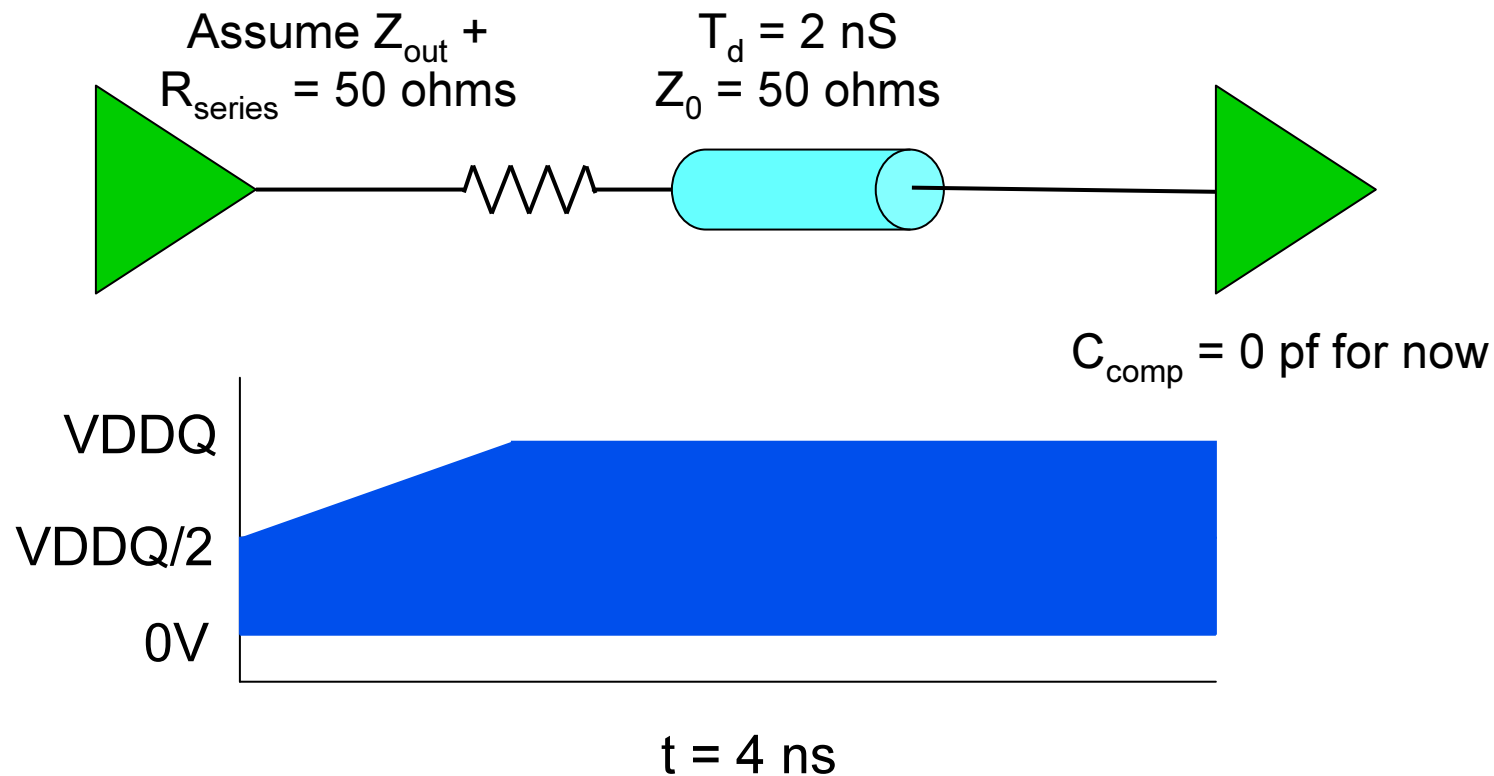

Rising Edge Behavior, $t=4.5\text{ns}$

Cisco.com

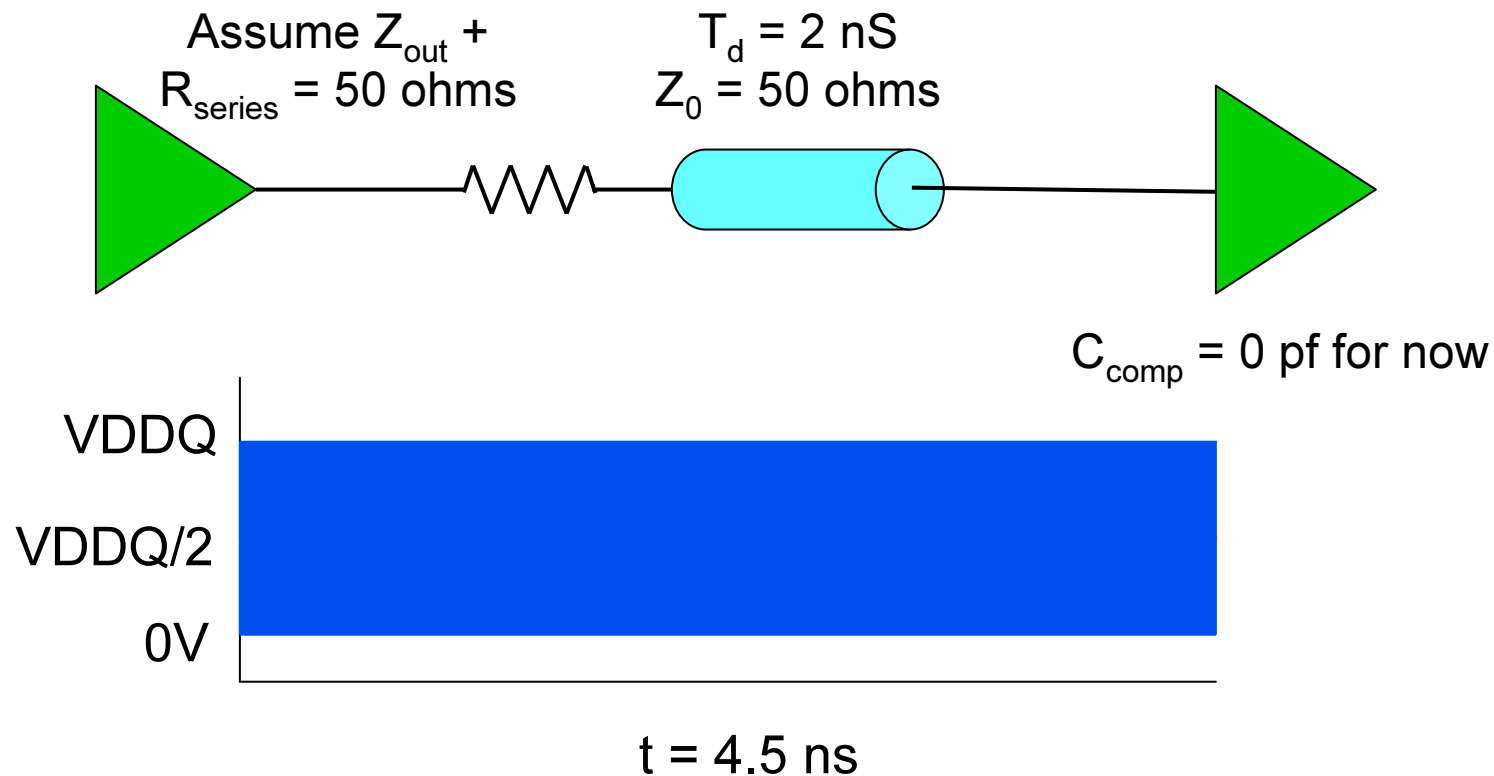


Observations

- **The buffer output changes voltage only when the edge is launched and the reflection is received**
 - Launch: 0 to 0.5 ns
 - Reflection: 4 to 4.5 ns
- **The buffer spends most of its time in the steady-state condition, where behavior is determined by the V/I curve**
 - Reflection behavior is also determined by the V/I curve


Dynamic vs. Steady State Behavior

Cisco.com

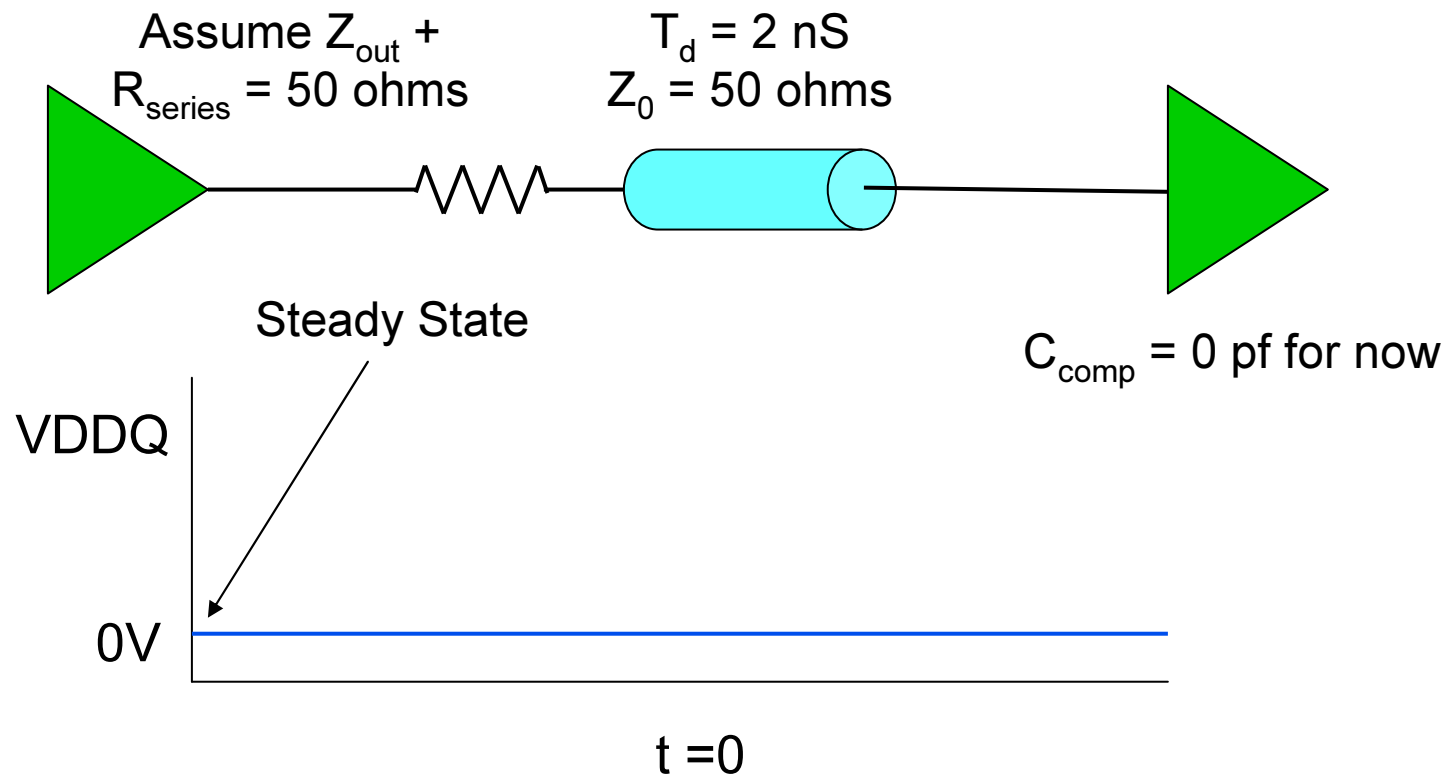


Dynamic vs. Steady State Behavior

Cisco.com

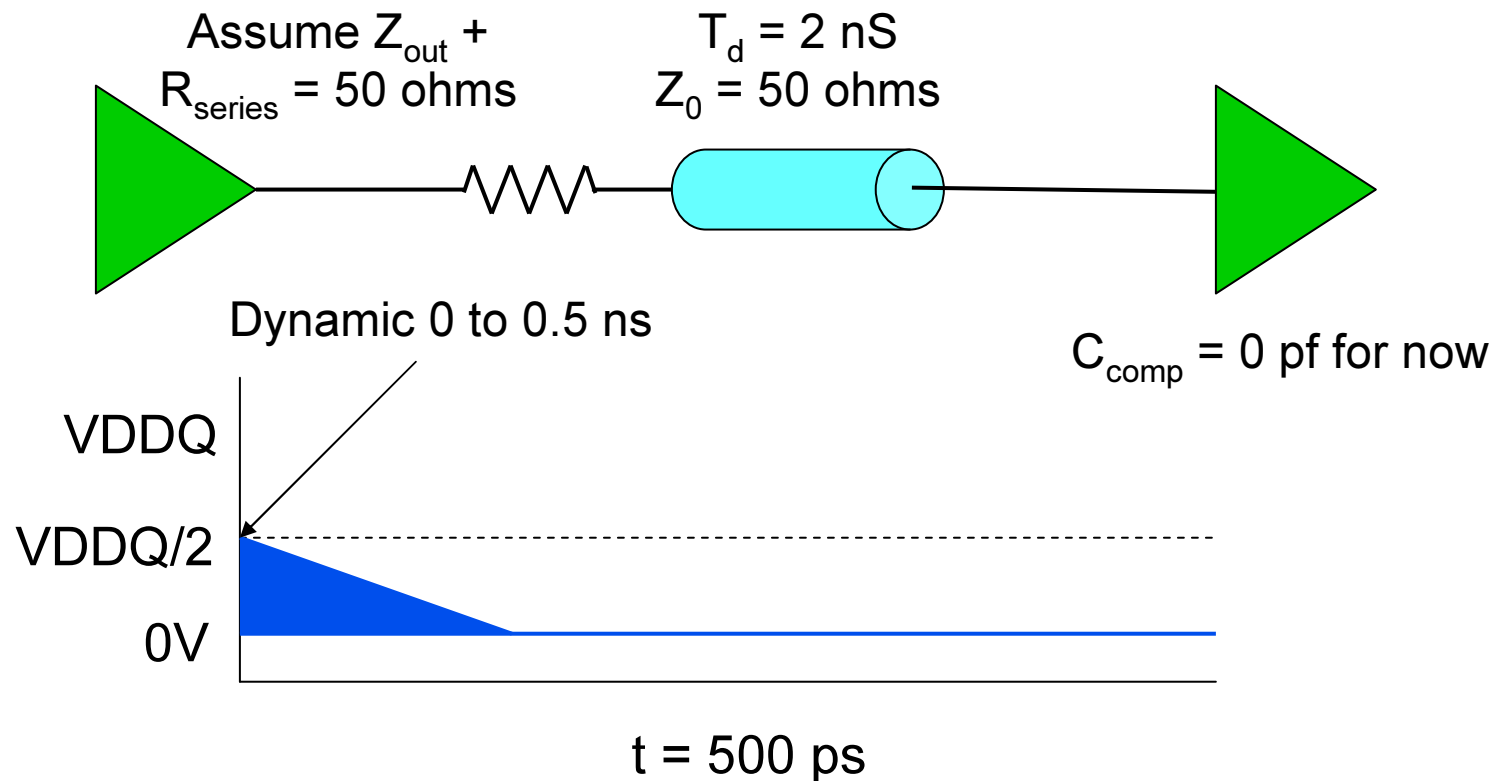


Dynamic vs. Steady State Behavior

Cisco.com

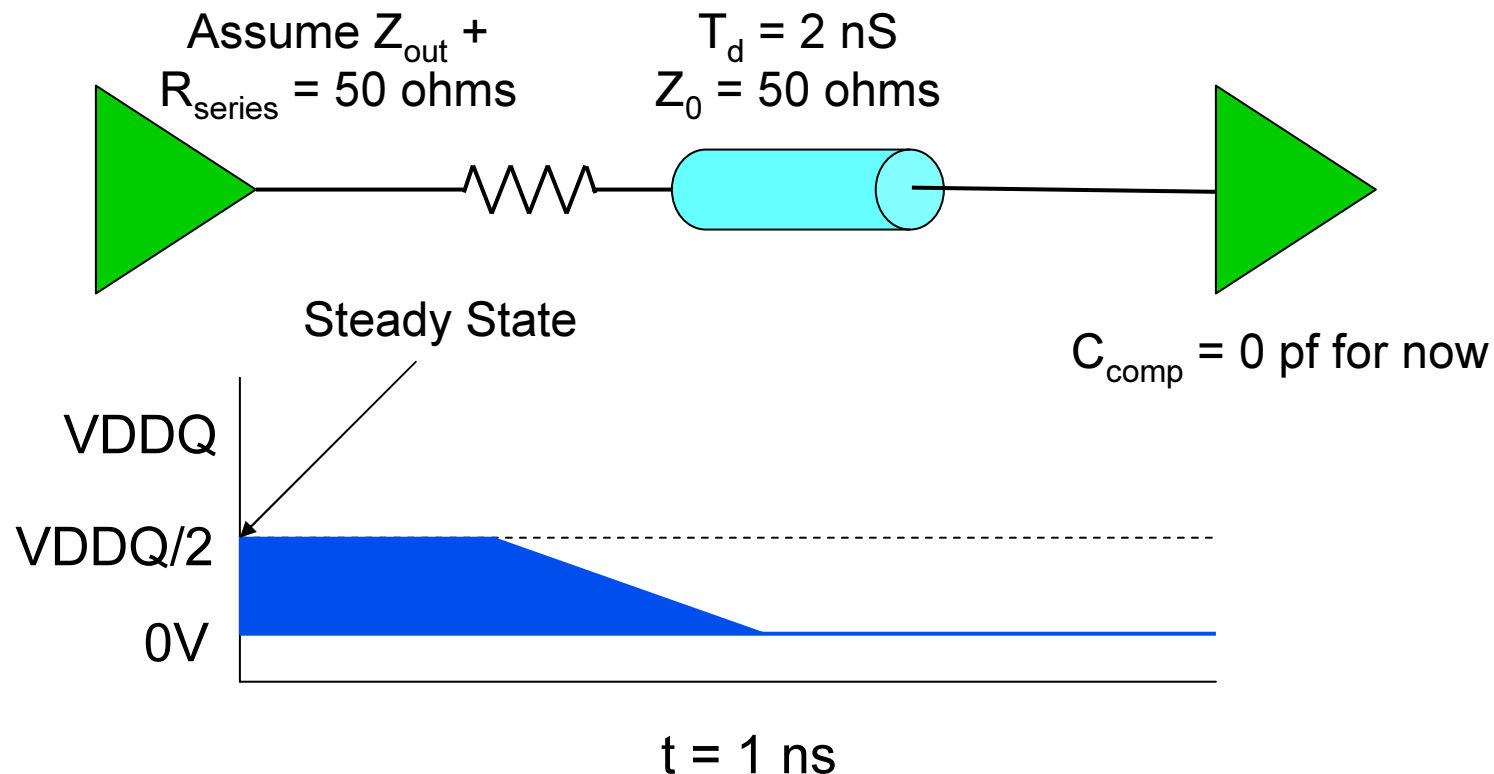


Dynamic vs. Steady State Behavior

Cisco.com

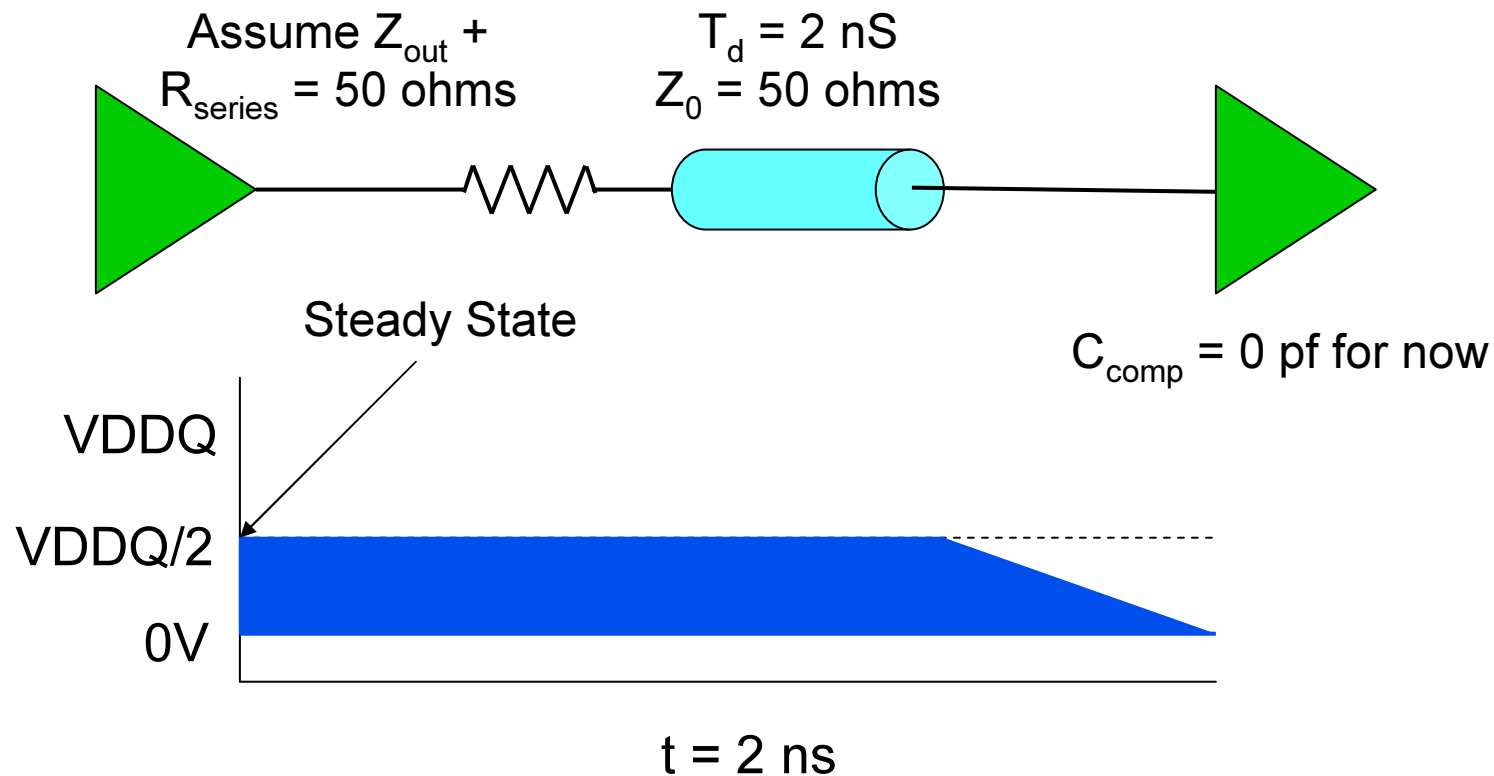


Dynamic vs. Steady State Behavior

Cisco.com

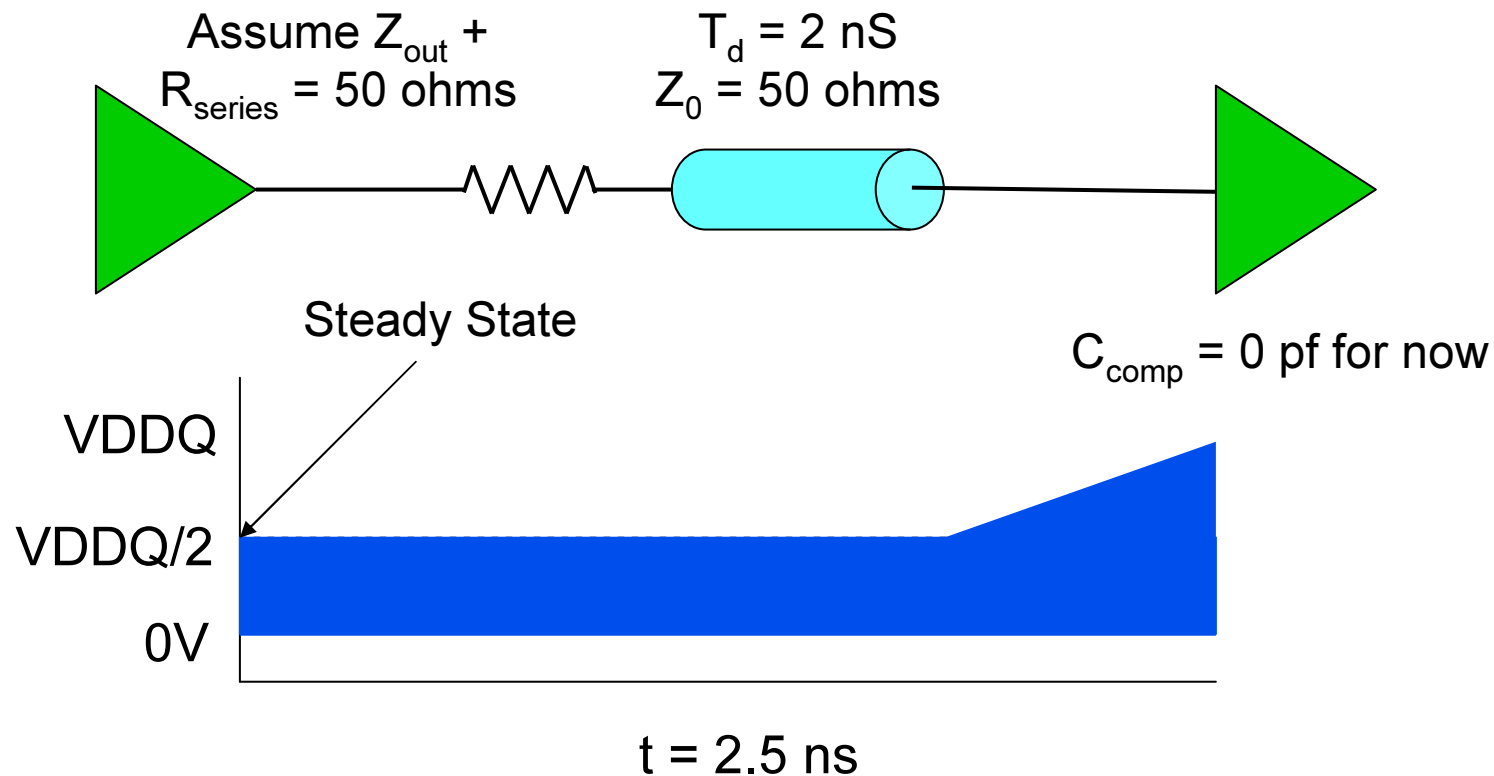


Dynamic vs. Steady State Behavior

Cisco.com

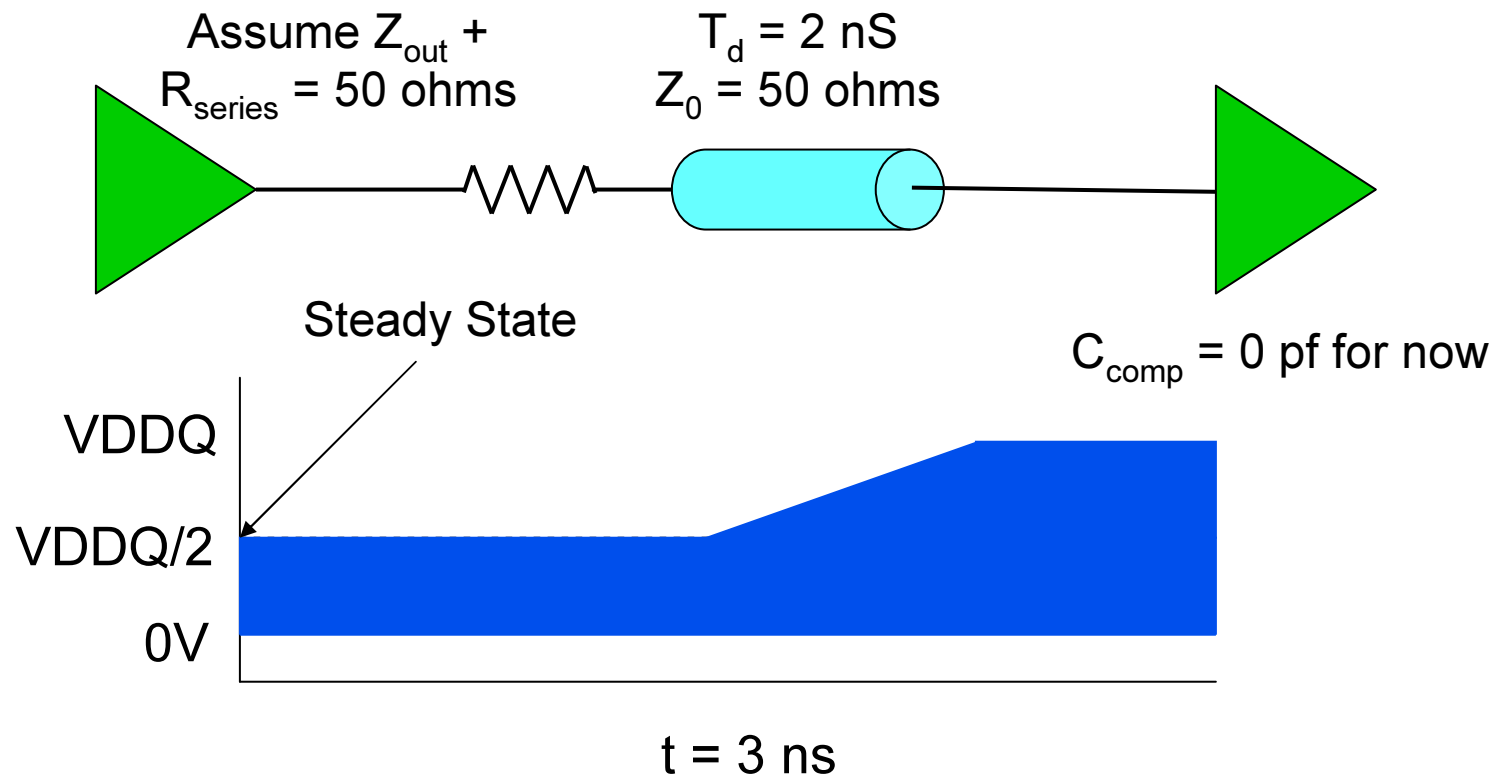


Dynamic vs. Steady State Behavior

Cisco.com

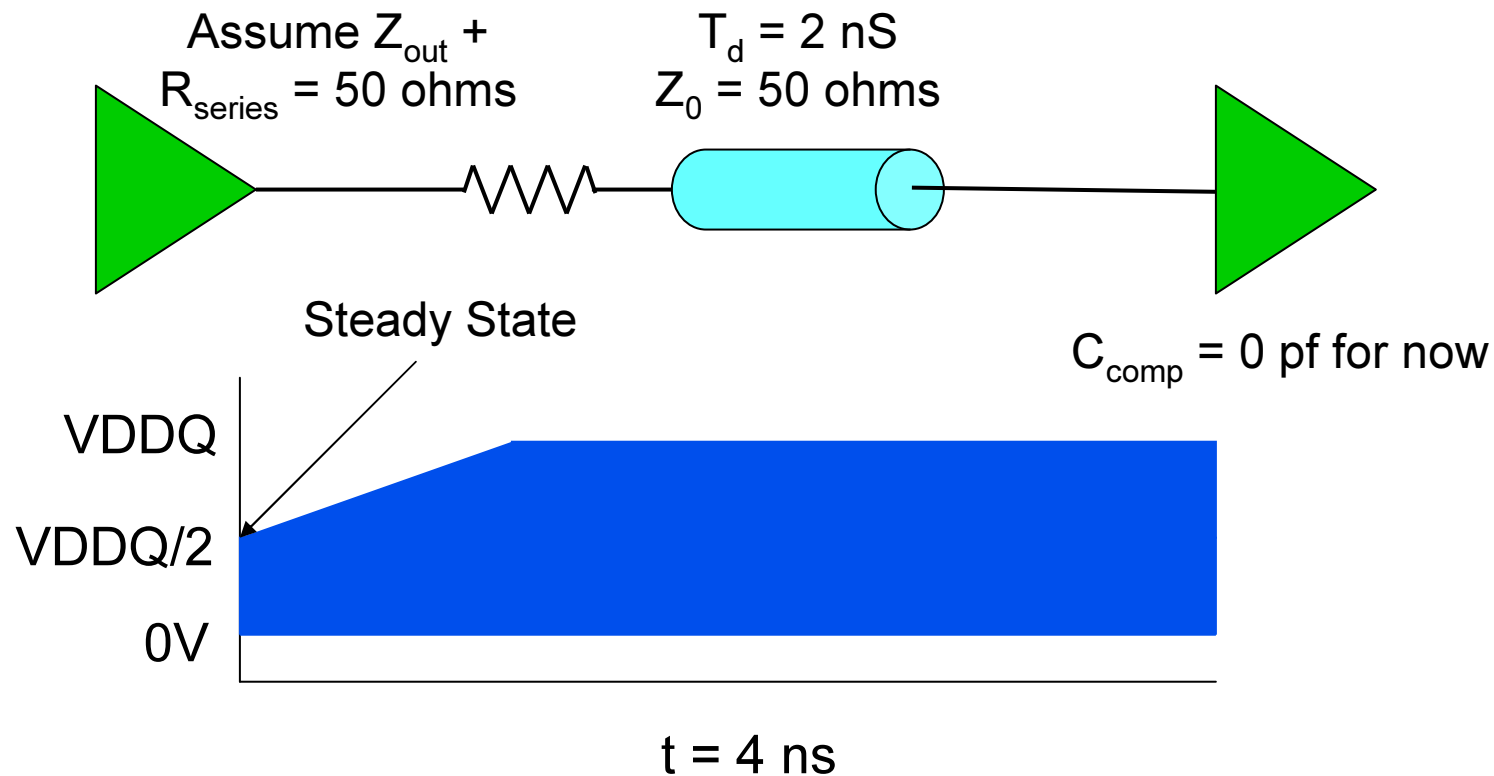


Dynamic vs. Steady State Behavior

Cisco.com

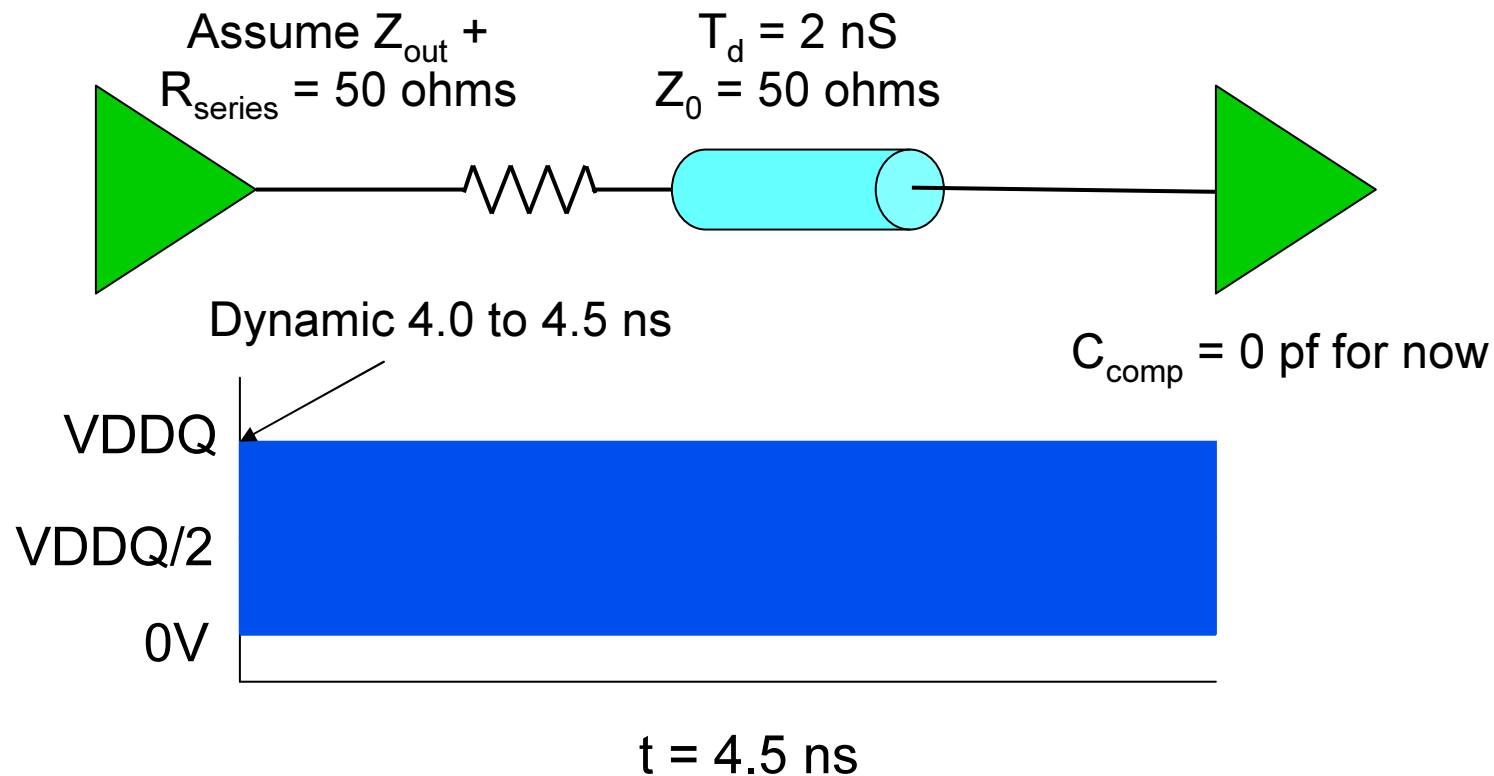


... So What Determines Steady-State Values?

Cisco.com

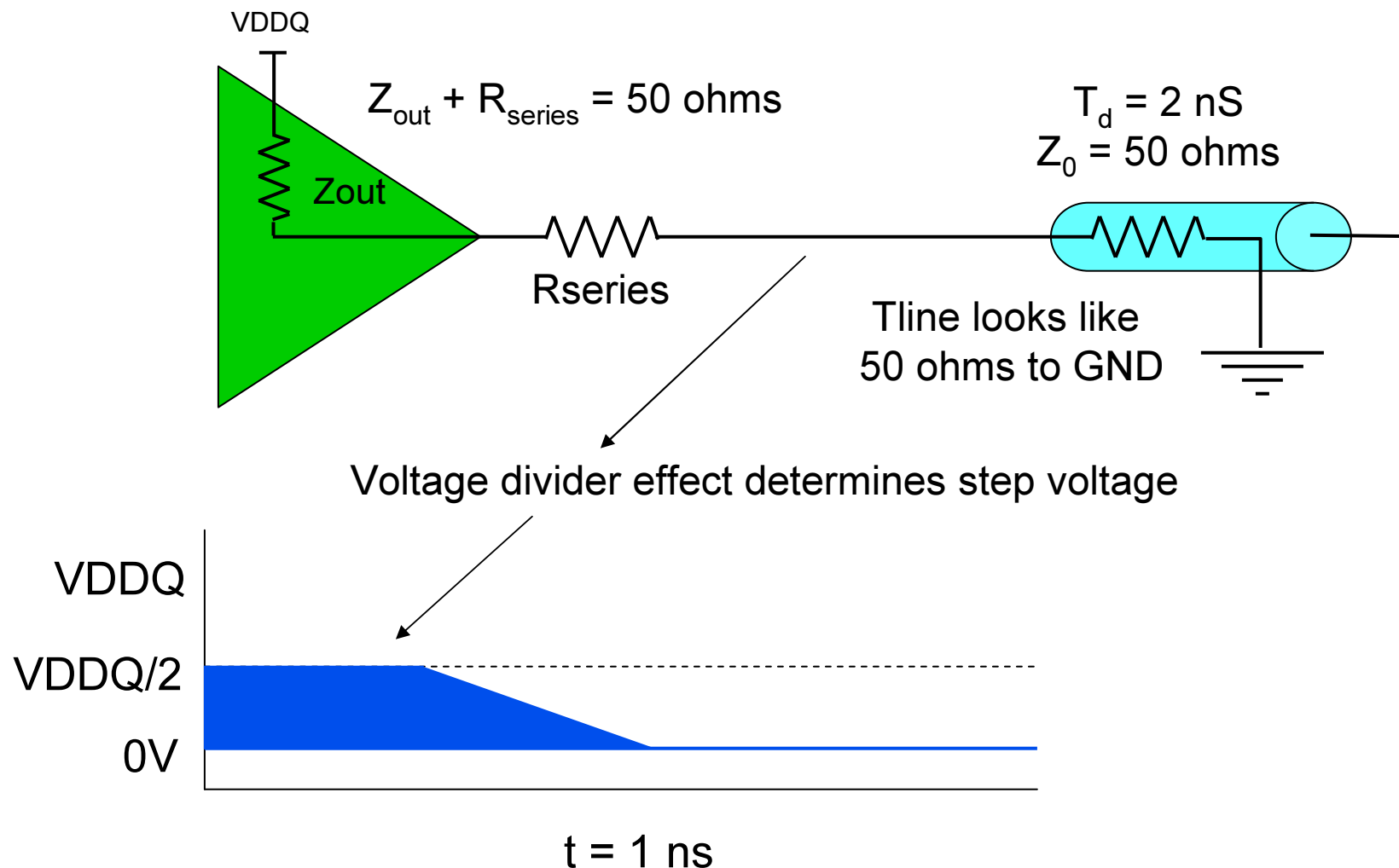

How to Determine Z_{out} ?


Cisco.com

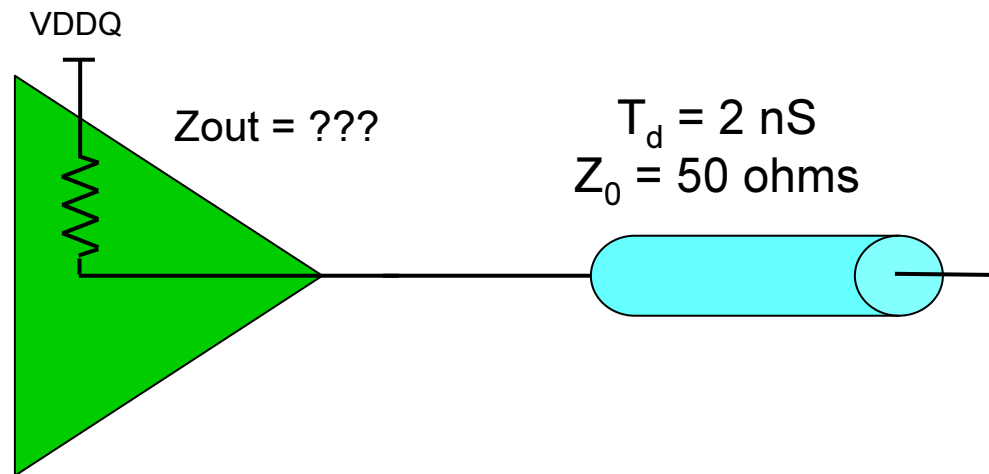

- If we know Z_{out} , we can compute step voltage
- Can select R_{series} such that $Z_{out} + R_{series} = Z_0$

Remember Transistor Curves and Load Lines?


Cisco.com

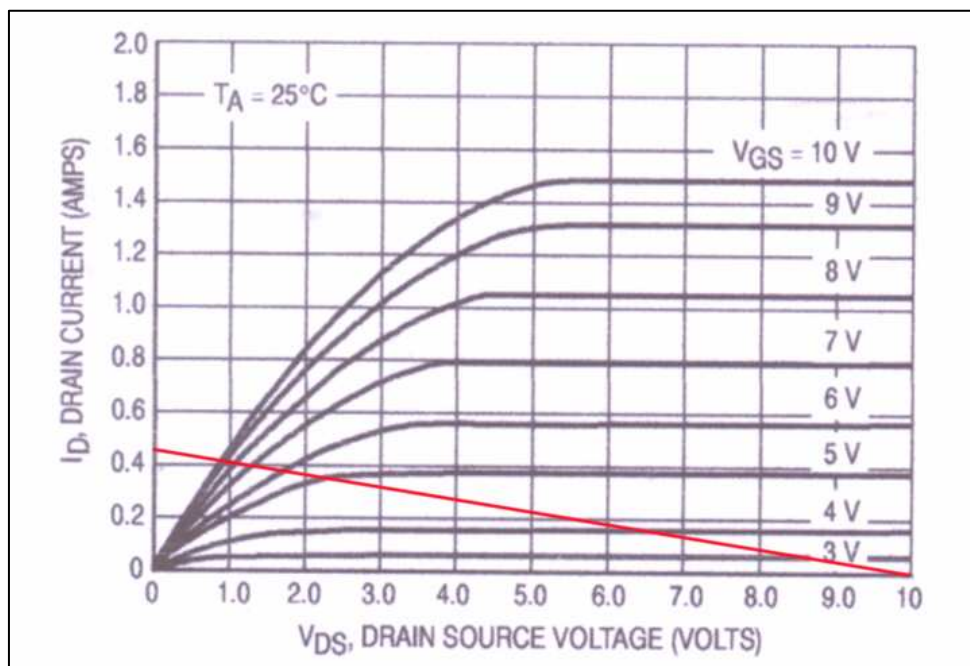

- We used them to find DC bias points for amplifier circuits back in college
- They're equally valid for digital circuit analysis
 - Digital circuits simply operate with V_{GS} saturated

1.8V HSTL Class 1 Pulldown V/I Curve


Cisco.com

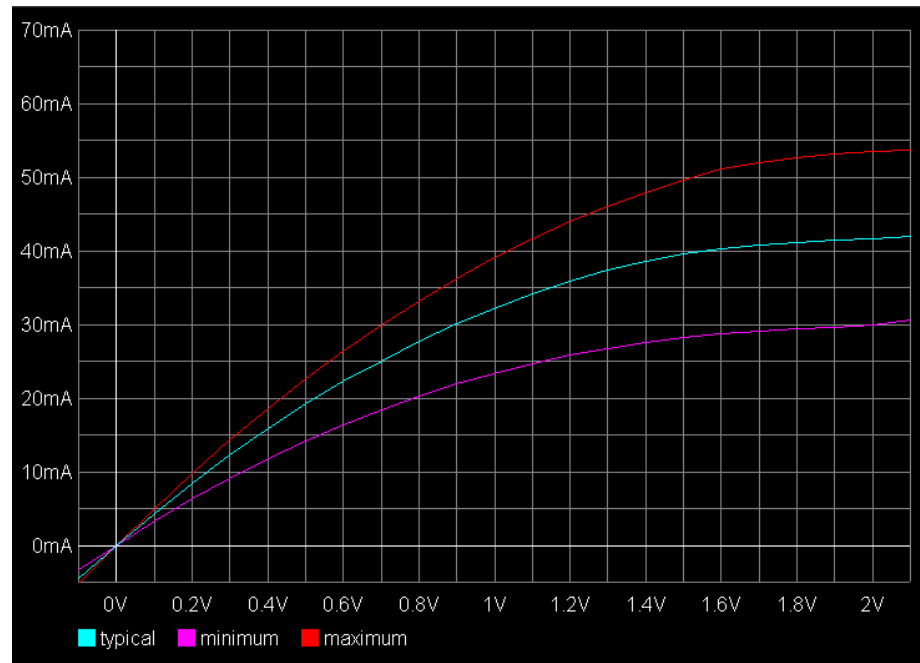

- **Look like a transistor curve? That's because it is!**
 - Special case where $V_{GS} = V_{DDQ}$
- **Load line analysis will find the operating point**

1.8V HSTL Class 1 Pulldown Load Line


Cisco.com

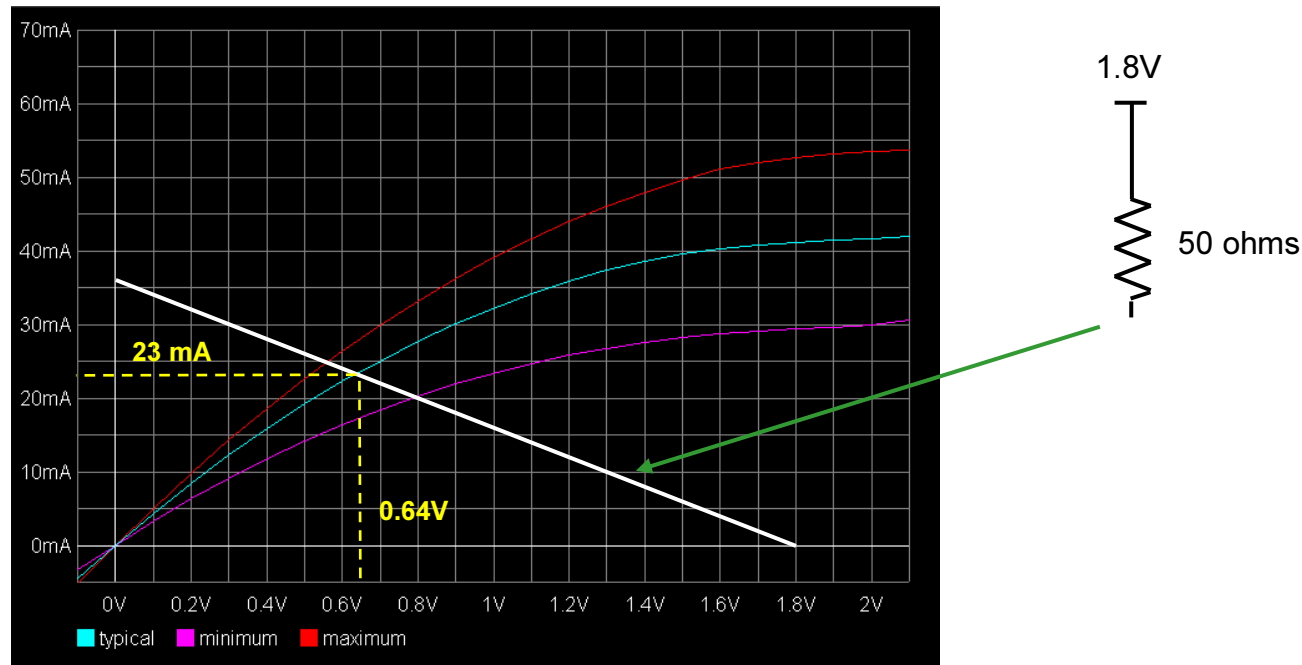


- Since this is a pull down, load line should be 50 ohms to VDDQ
- Step voltage for unterminated line is 0.64V
- This buffer will overdrive a 50 ohm line in the nominal case

Simulation Results

Cisco.com

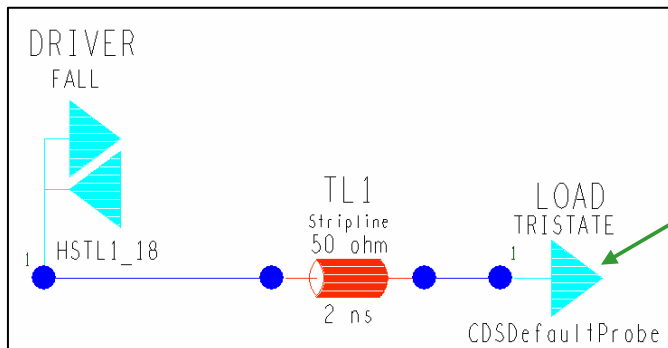

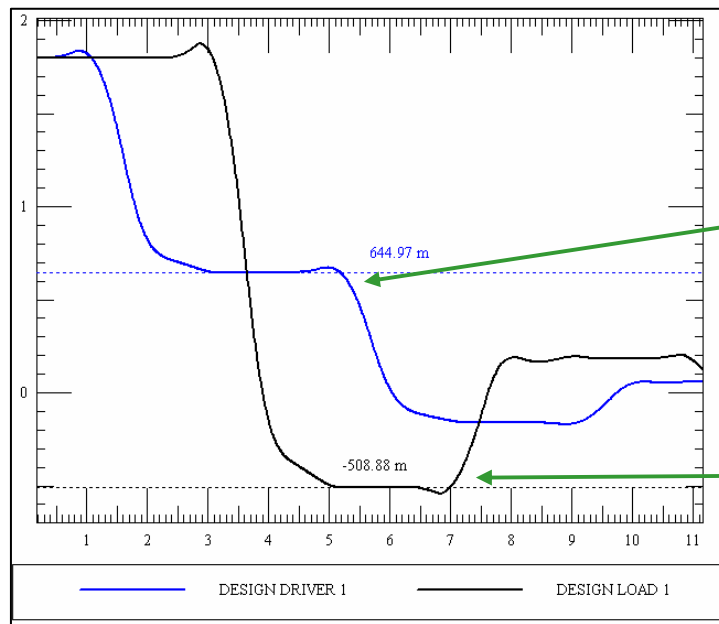
Dummy load has no effect; gives simulator a node to measure



Step voltage is 645 mV

Overshoot is 509mV below GND


What Else Do We Know?

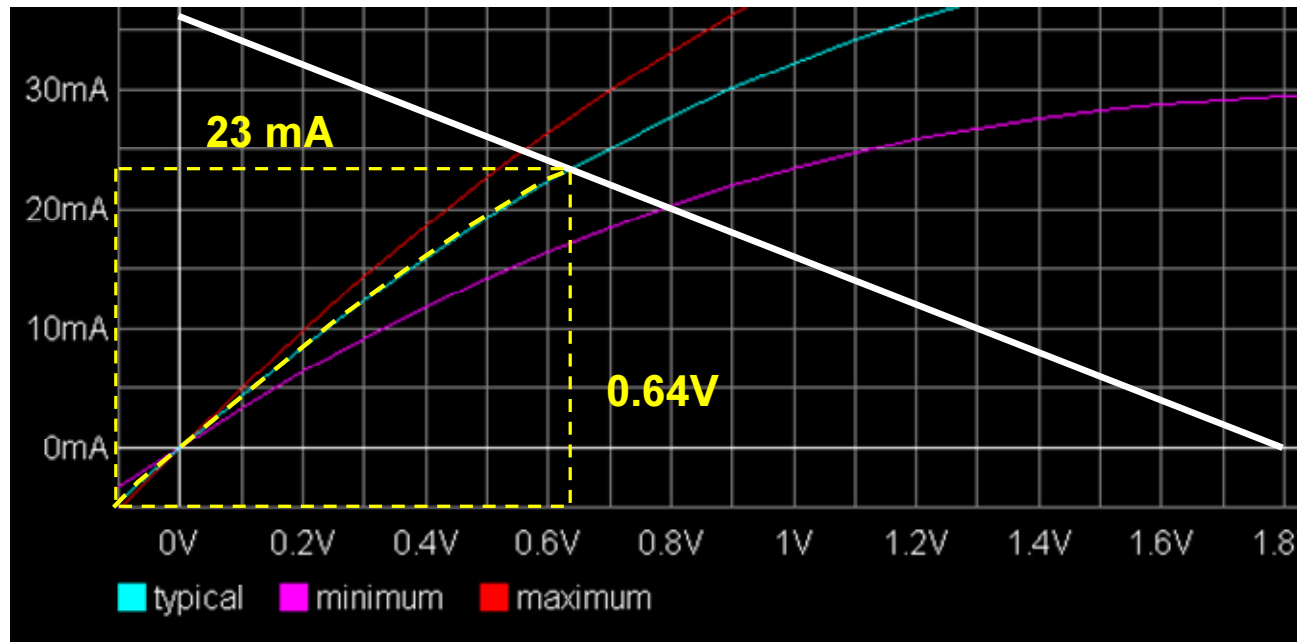

- Pulldown will operate along the V/I curve from the origin to the load line intersection
- The slope of the V/I curve corresponds to Z_{out} , if the curve is linear, the device will behave as a resistor

Serial Termination Basics


Cisco.com

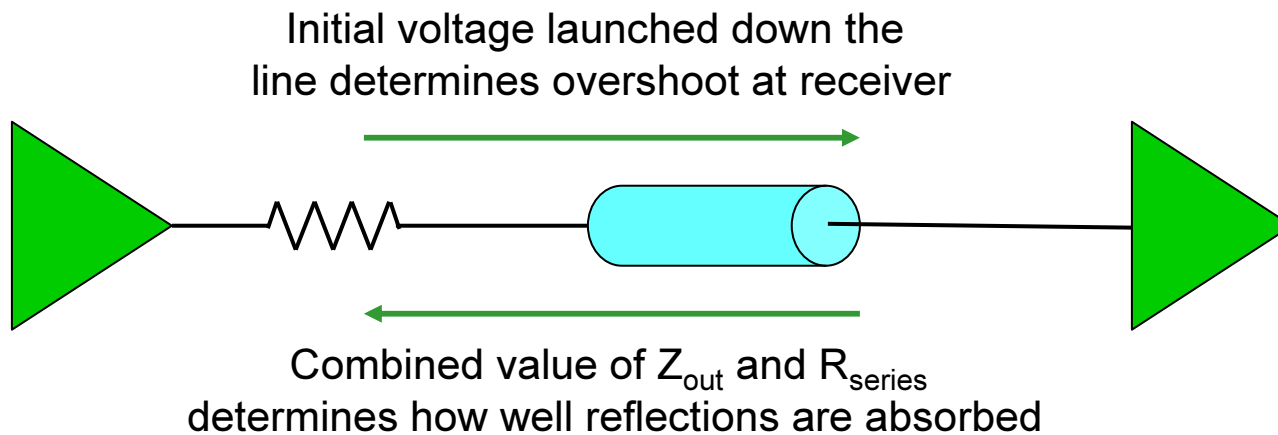

It's a Current Thing ...

Cisco.com

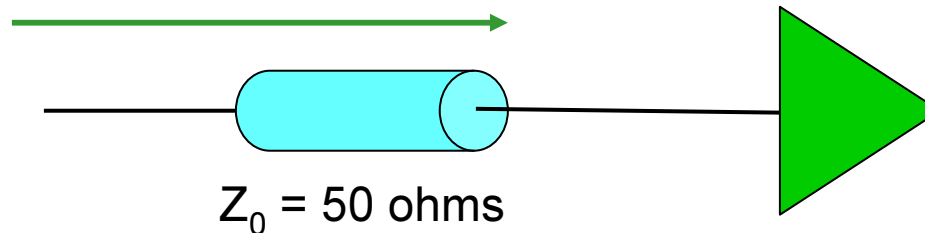
What current gives us the ideal response at the receiver input?



- **Ideal step voltage is $V_{DDQ}/2$**
 - From Ohm's law: $E=IR$, $I=E/R$
 - $E = V_{DDQ}/2$, $R=50 \text{ ohms}$
 - $I = (V_{DDQ}/2)/50 = V_{DDQ}/100$
- **Our 1.8V receiver requires $1.8/100 = 18\text{mA}$ of line current for ideal reflection behavior**

How Strong Is Our HSTL Output?


Cisco.com

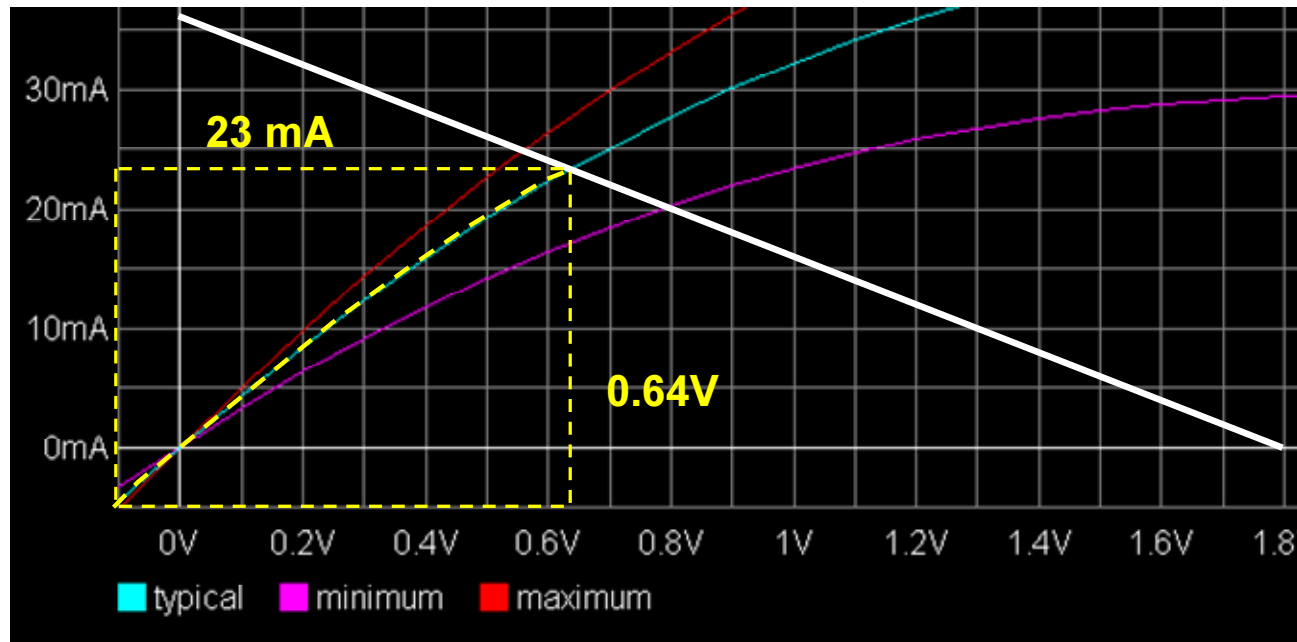

- At 50 ohm operating point, $R=E/I$
 - $E = 0.64V$, $I = 23 \text{ mA}$
- Effective output impedance = 28 ohms

... So, What Value of R_{series} ?



Cisco.com

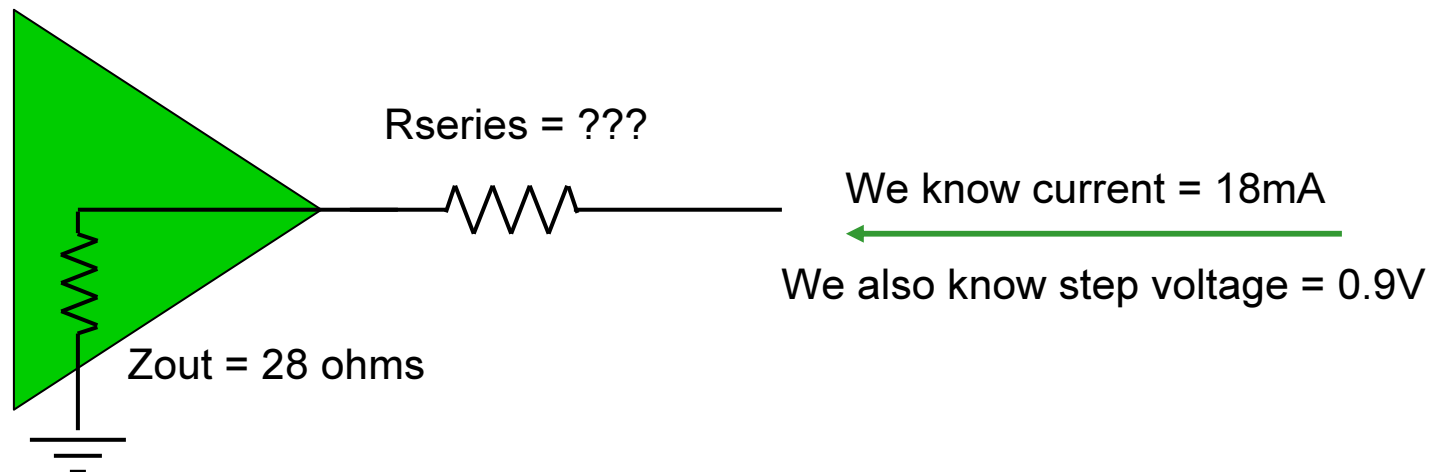

- **Effective Output Impedance, $R=E/I$**
 - $E = 0.9\text{V}$, $I = 18\text{mA}$, so $R = 50 \text{ ohms}$
- **$Z_{\text{out}} + R_{\text{series}} = 50$, $R_{\text{series}} = 22 \text{ ohms}$**

Updated Simulation Results

Cisco.com

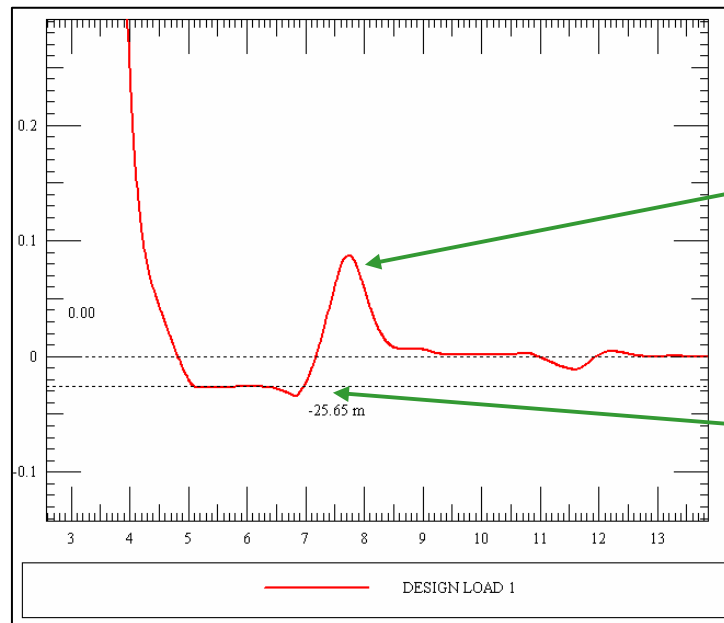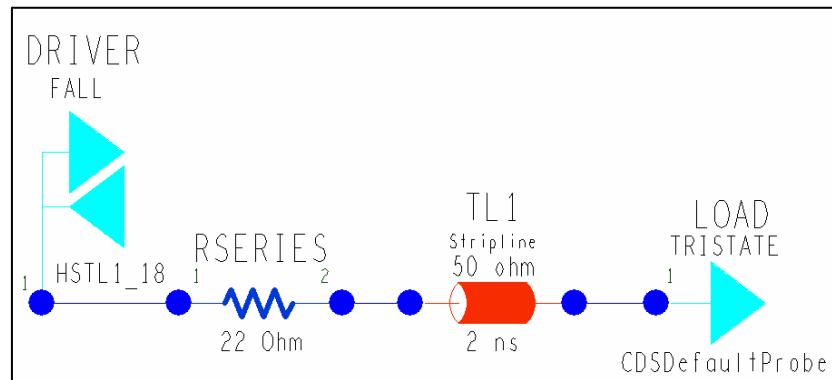


**Negative reflection
off driver's C_COMP**

**Still slight overshoot;
25mV below GND**

Why Is There Still Overshoot?



Cisco.com

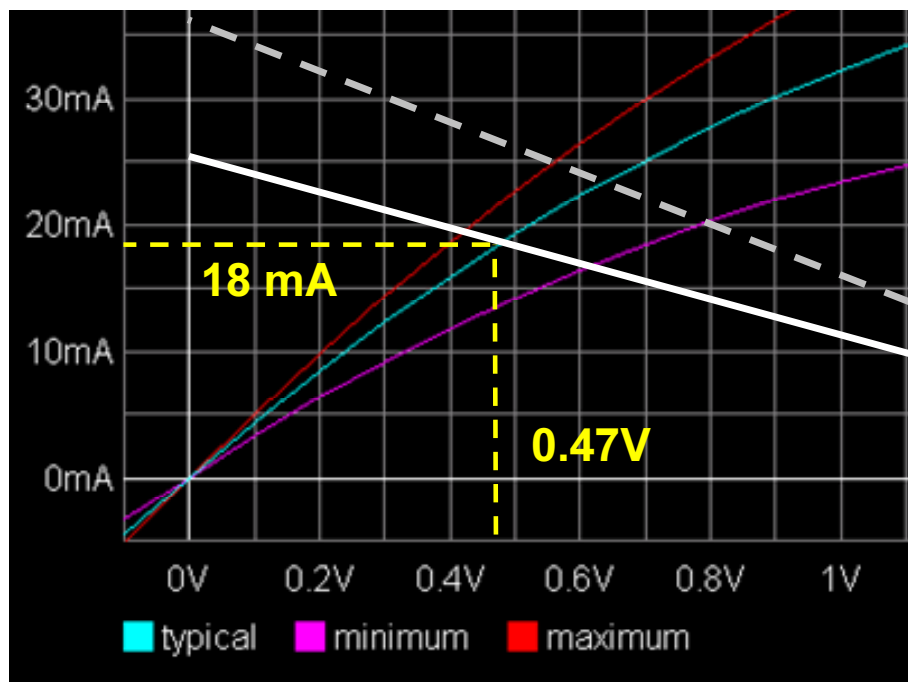

- The series resistor changes the transistor's operating point
- Load line is now 72 (50 + 22) ohms to VDDQ
- If the V/I curve isn't linear between the new and old operating points, Z_{out} will change
- New $Z_{out} = 0.47V/18mA = 26 \text{ ohms}$

Simulation Results For New Load Line

Cisco.com

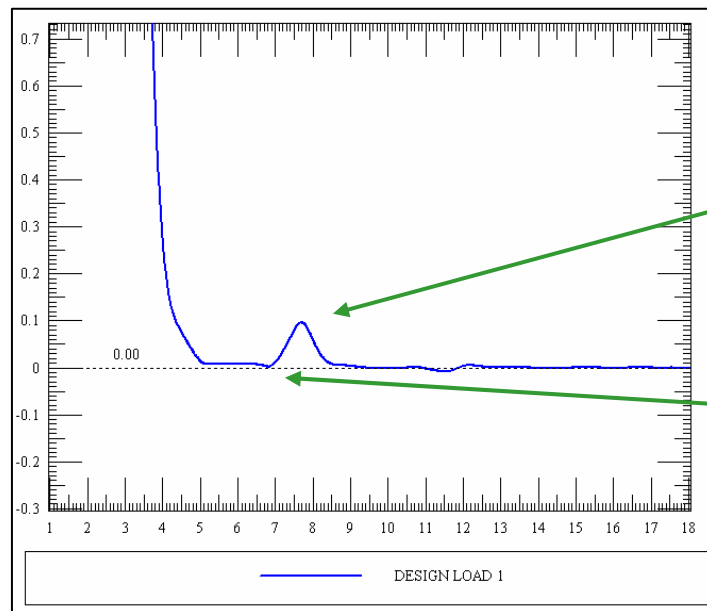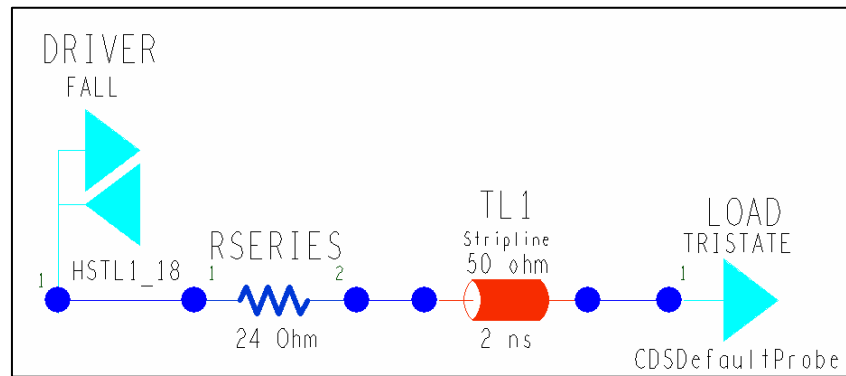


**Negative reflection
off driver's C_COMP**

**Overshoot is
basically gone**

How Do We Determine Z_{out} and R_{series} ?


Cisco.com

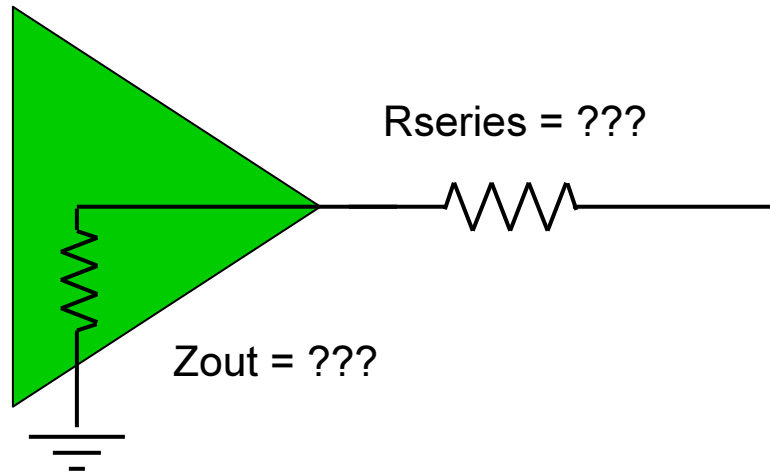

1. Determine ideal current from $I = VDDQ/100$
2. Find corresponding current point on V/I curve
3. Compute $Z_{out,eff} = E_{curve}/I_{curve}$
4. Assign R_{series} such that $Z_{out,eff} + R_{series} = Z_0$

For Our 1.8V HSTL Buffer ...


Cisco.com

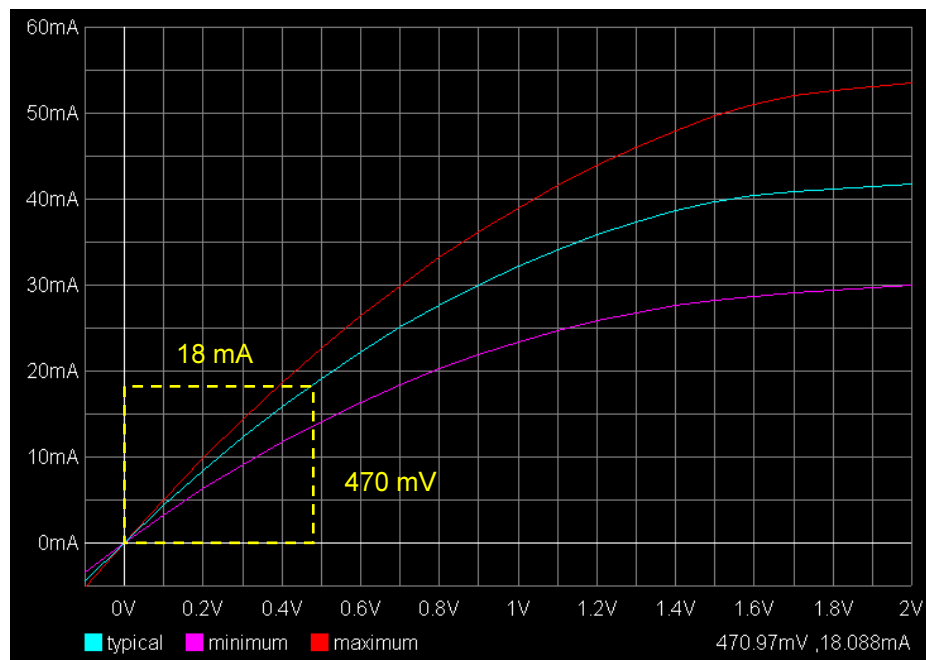

1. $I = 1.8V/100 = 18mA$
2. From the pulldown curve, $E=470mV$ at $I=18 mA$
3. $Z_{out,eff} = 0.47/0.018 = 26.1 \text{ ohms}$
4. $R_{series} = 23.9 \text{ ohms}$

Pullup Curves Work The Same Way



Cisco.com

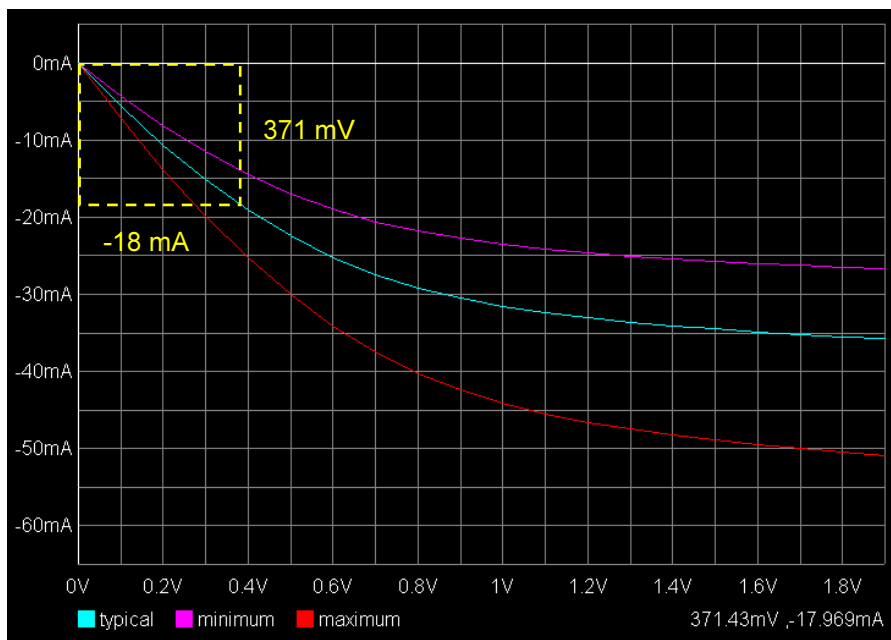

1. $I = 1.8V/100 = -18mA$
(IBIS convention)
2. From the pullup curve,
 $E=371mV$ at $I=-18 mA$
3. $Z_{out,eff} = 0.371/0.018$
 $= 20.6 \text{ ohms}$
4. $R_{series} = 29.4 \text{ ohms}$

Pullup/Pulldown Simulation Results

Cisco.com

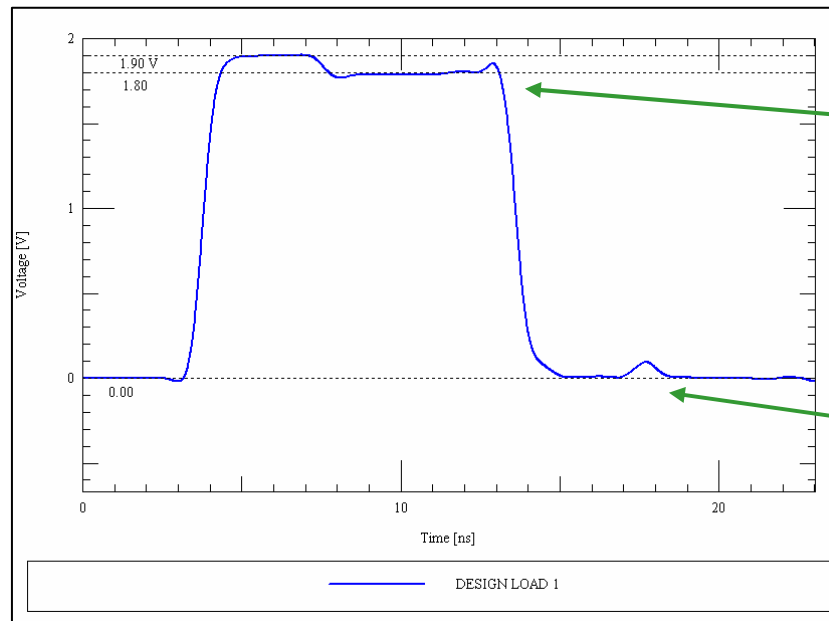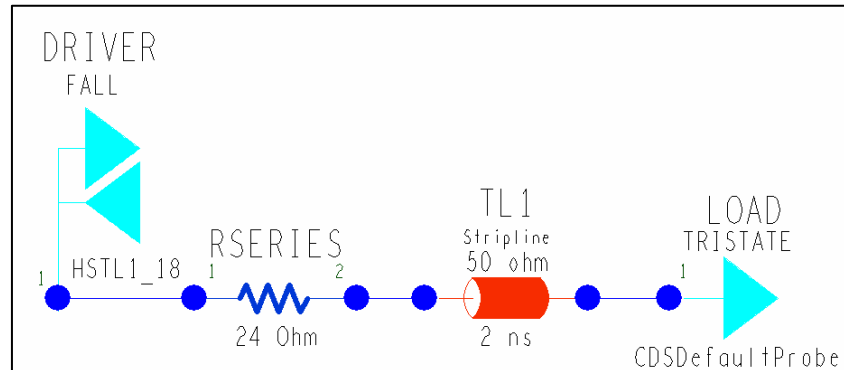

**Overshoot on
rising edge**

**R_{series} well matched
for falling edge**


Observations

- This is a HSTL Class 1 buffer; we'd expect it to be designed for point to point operation without termination (50 ohm Z_{out})
- $Z_{out,eff}$ ranges from 21-26 ohms, requiring a series resistor to avoid overshoot
- Pullup/Pulldown are not well matched (21 vs. 26 ohms)
- This could either be a buffer design issue or a modeling issue

More On V/I Curves

Cisco.com

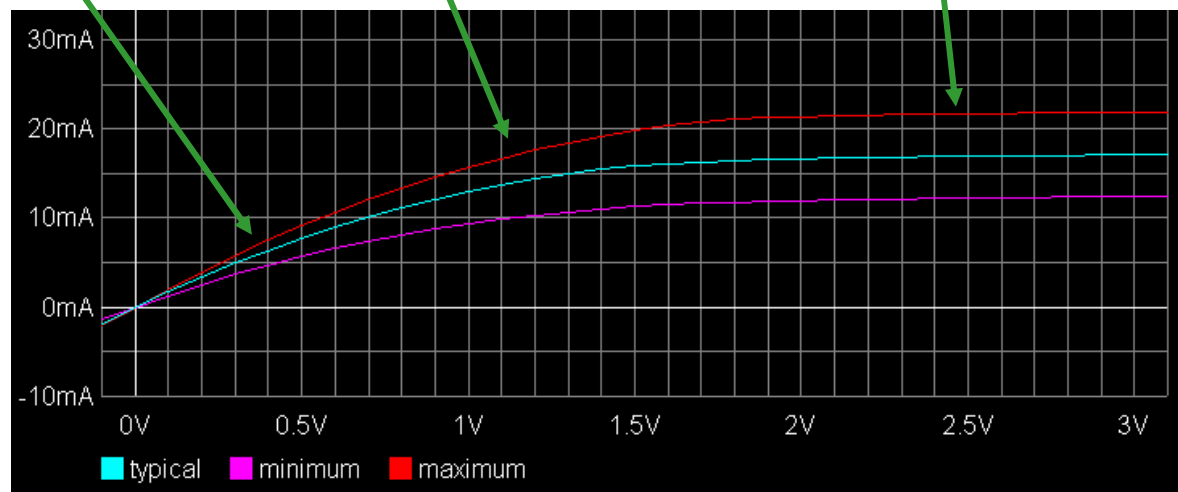
Linear Region Nonlinear Region Saturated Region



- **Where the load line intersects the V/I curve says a lot about how the device will behave**

3.3V, 4mA LVTTTL Buffer Pulldown Curve



Cisco.com

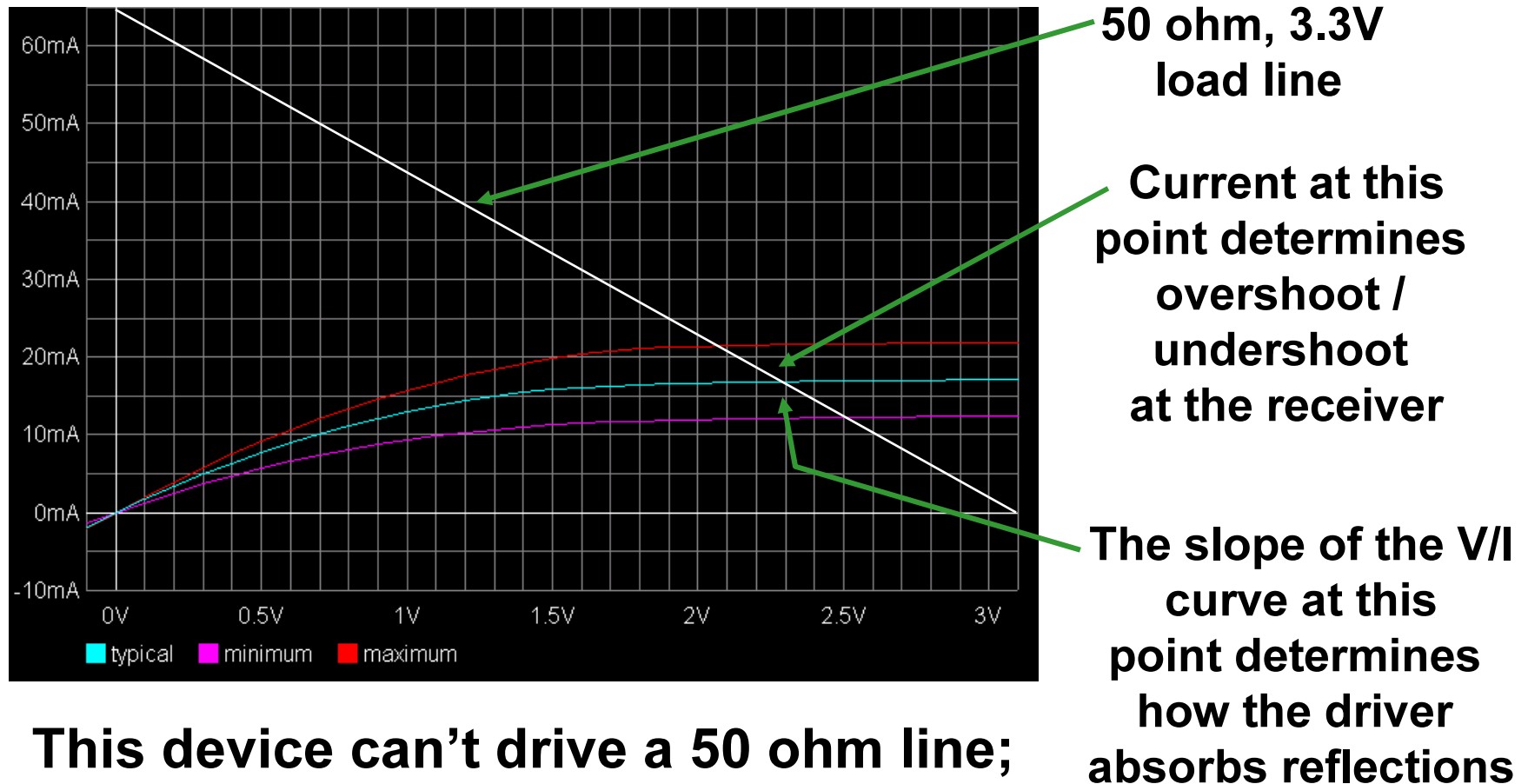

- This device can't drive a 50 ohm line; we need 30 mA, the output can only supply 17 mA

Simulation Results, 4mA Buffer


Cisco.com

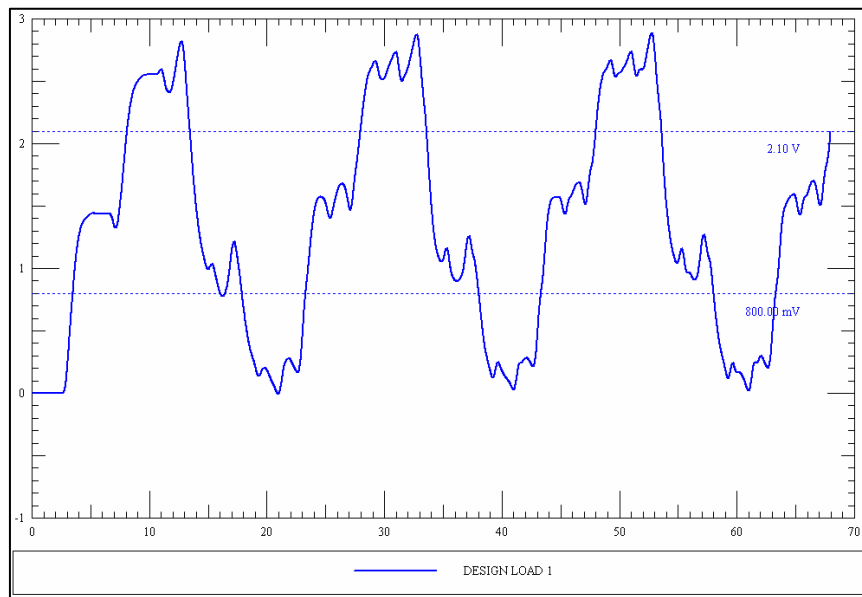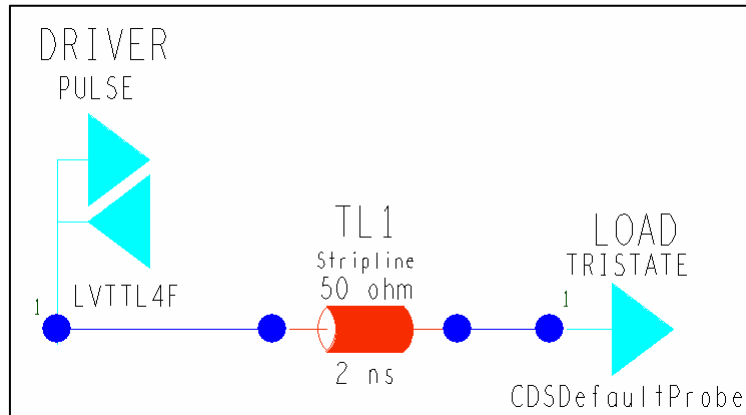

- **As expected, the driver cannot drive the line or adequately control the reflections**

3.3V Clock Output Buffer Pulldown



Cisco.com

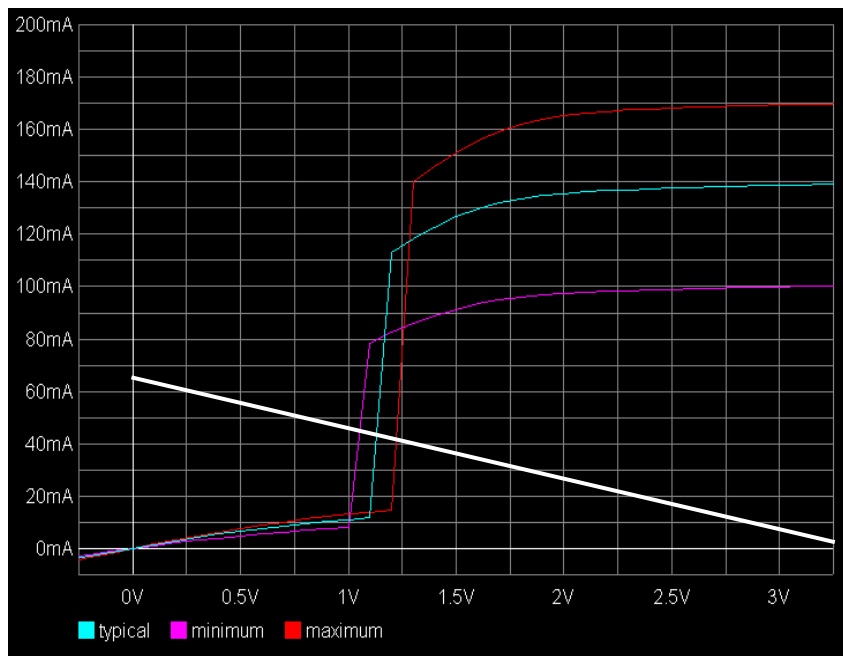

- Load line suggests buffer will drive about 42mA into a 50 ohm line; we only need 30mA
- Step voltage $E=IR$, $42 \text{ mA} \times 50 \text{ ohms} = 2.1\text{V}$, so we expect about 900 mV overshoot
- Slope of V/I curve at load line is very high; expect very poor absorption of reflections by driver

Simulation Results – Falling Edge



Cisco.com

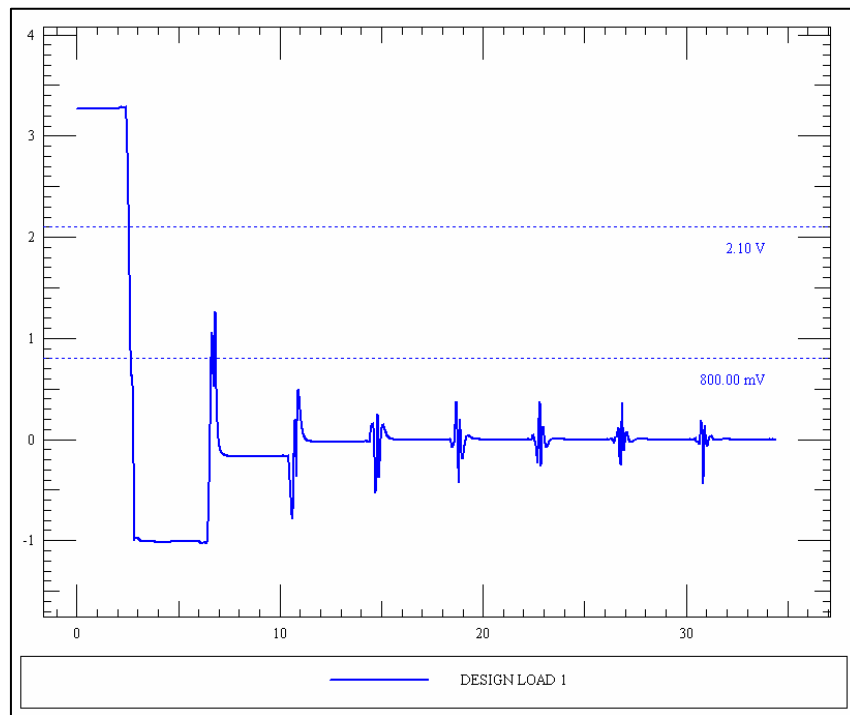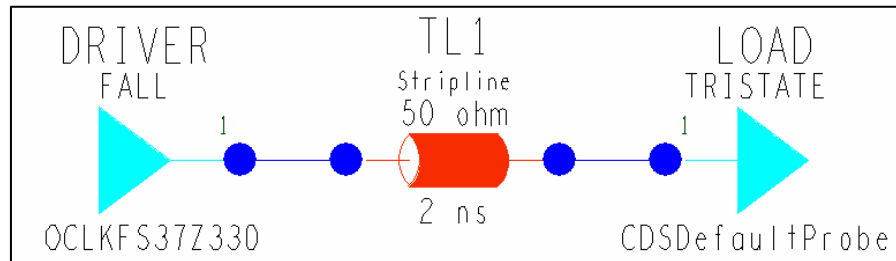

- **Overshoot slightly exceeds expectations**
- **“Ringing” occurs because of slope of V/I curve at the load line**

More Simulation Results ...



Cisco.com

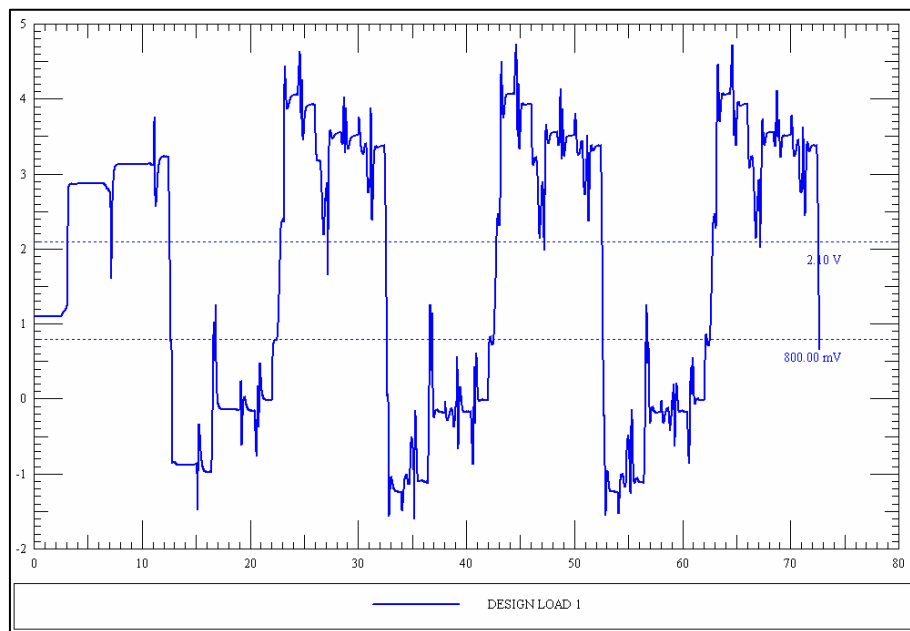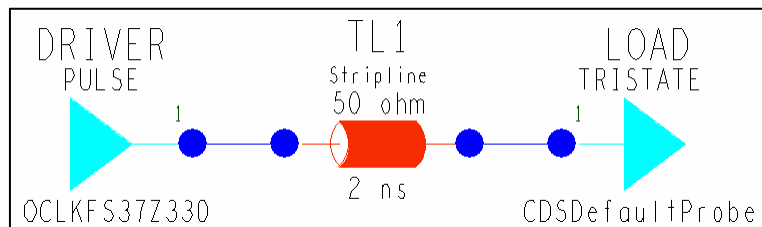

- “Ringing” amplifies over time; the model essentially spins out of control

Eliminate Reflections And ...

Cisco.com

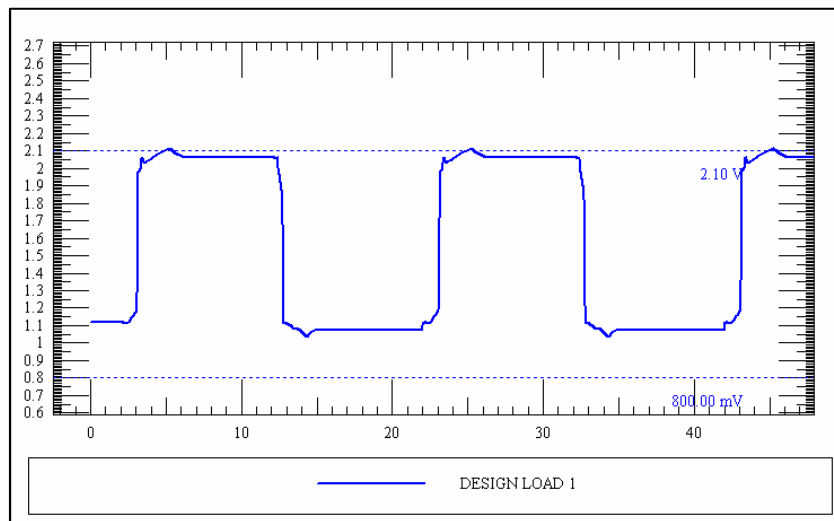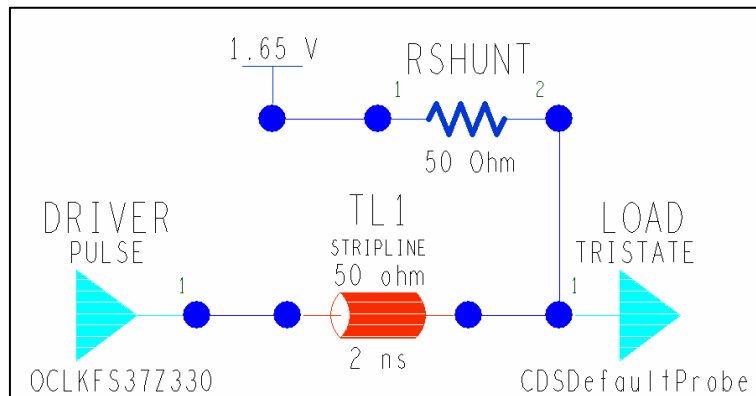

- **Ideal termination at the end of the line eliminates reflections off the driver**
- **Now we have a voltage threshold problem**
- **This may be a modeling problem anyway; should be investigated further**

Summary

- **Depending on the ratio of edge rate to line length, drivers can spend much of their time in “steady state” conditions**
- **“Steady state” behavior is driven by V/I curves**
- **Understanding the details behind V/I curve can provide valuable insight into**
 - **Buffer behavior**
 - **Model quality**
 - **Termination selection**

Yoda Says

Cisco.com



- **Mind your V/I curves!**
 - Important, they are!
 - Save you, they can!