

MODIFYING THE PFM OPERATION OF TPS61016 BY ADDING 1-M Ω RESISTOR AT COMP PIN

Sai Kee Loo

PMP Portable Power

ABSTRACT

This application report presents a way to modify the PFM mode of operation of the TPS61016 boost converter to meet low ripple voltage requirements at light load by changing the transconductance amplifier output compensation with detailed explanation and test results.

1 Description

The TPS61016 is a boost converter based on a fixed-frequency, current-mode PWM controller that goes automatically into power-save mode (i.e., PFM or pulsed frequency modulation) at light loads for higher efficiency during this load condition. The controller enters this power-save mode if the following two conditions are met:

1. Output voltage is 99% above nominal value.
2. Inductor current becomes discontinuous.

In power-save mode, the controller only switches on the internal switch if the output voltage trips below a set threshold voltage. It ramps up the output voltage with one or several pulses, and goes again into power-save mode once the output voltage exceeds a set threshold voltage. However, this mode of operation causes higher ripple voltage at the output during the PFM mode operation.

[Figure 1](#) shows the schematic with internal block diagram of the TPS61016, and [Figure 2](#) shows the output ripple voltage and inductor current of TPS6101x during PFM operation and PWM operation. [Figure 3](#) and all subsequent illustrations show the effect of adding the 1-M Ω resistor across the COMP pin of TPS61016.

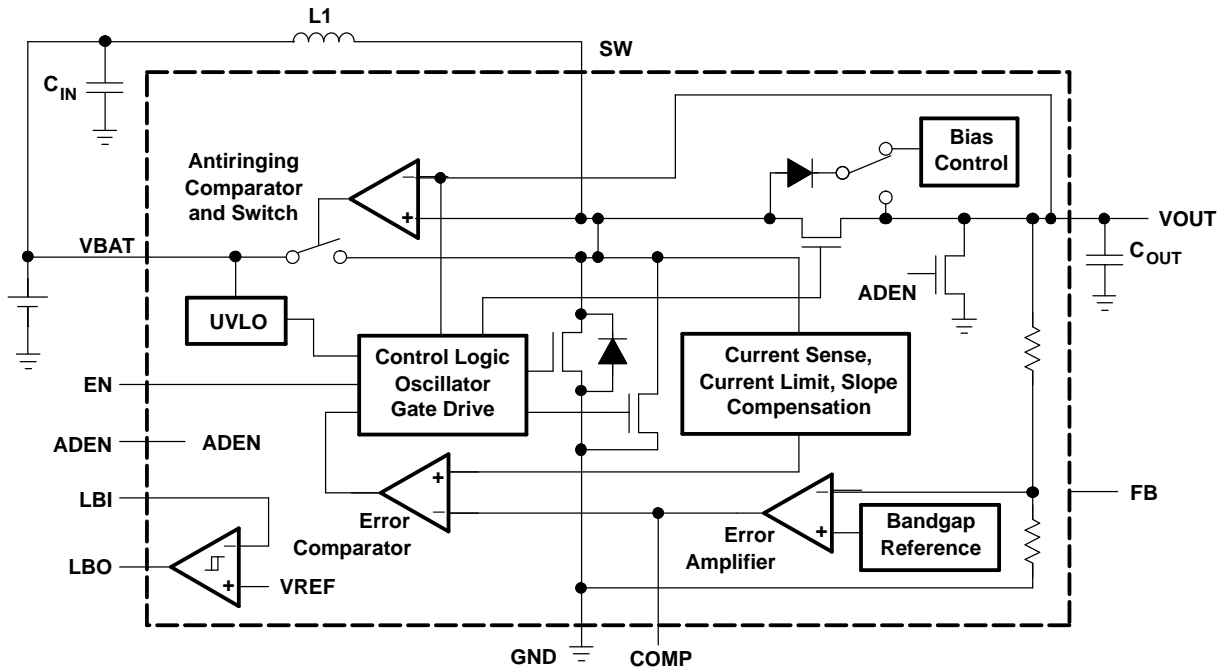


Figure 1. TPS61016 Internal Block Diagram

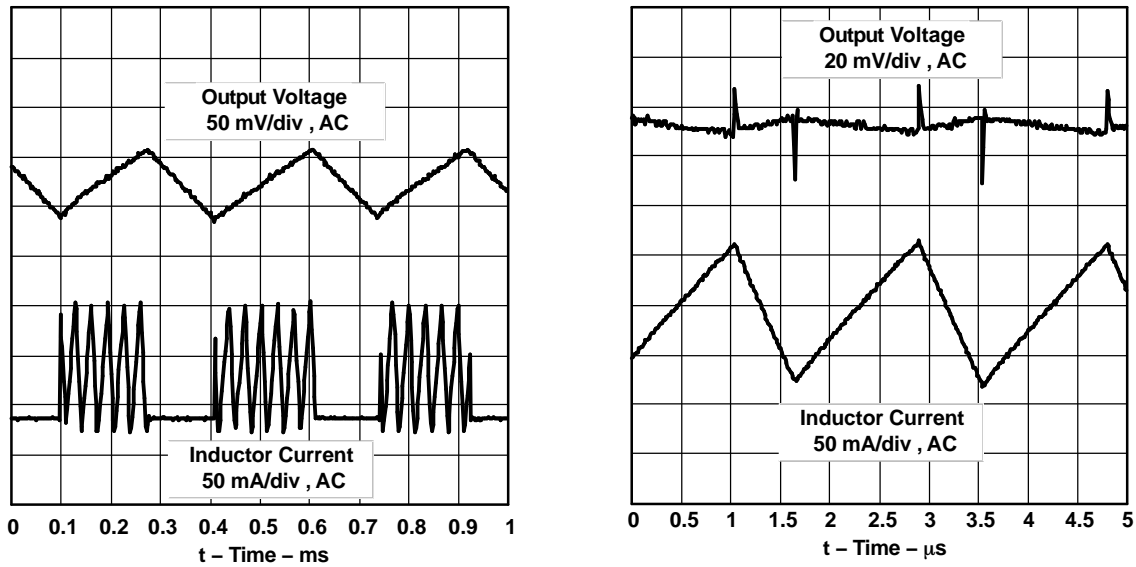


Figure 2. PFM Mode Operation (Left Waveform) and PWM Mode Operation (Right Waveform)

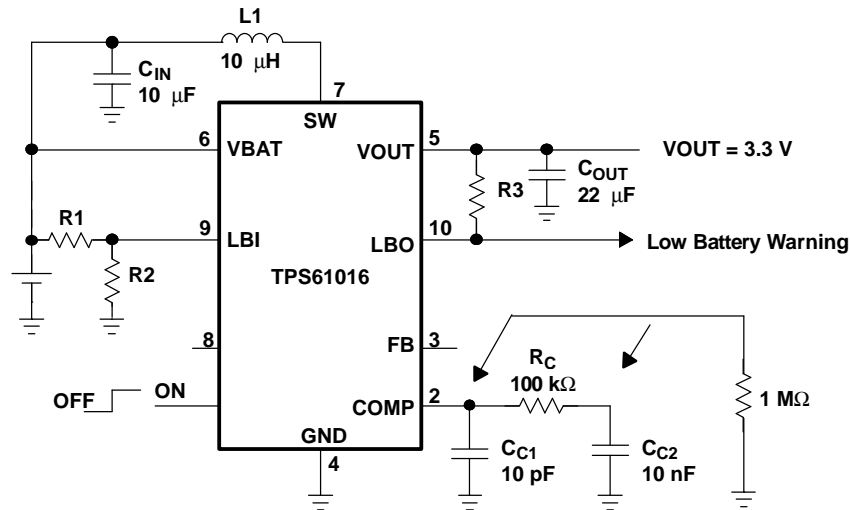


Figure 3. Adding an 1-M Ω Resistor Across COMP Pin

The COMP pin is the output of a transconductance amplifier (current output). When a resistor is connected at the COMP pin to ground, an offset at the error amplifier is generated, and the output voltage of the converter drops (in this example, the output voltage dropped from 3.289 V to 3.284 V).

With a 1-M Ω resistor connected at the COMP pin and with a COMP voltage of about 320 mV (see actual waveform in [Figure 4](#)), about 320 nA is drawn from the error amplifier output. This causes an input offset at the amplifier of 11.8 mV ($g_m = 27 \mu\text{A/V}$ for the amplifier). This means that the converter now regulates the output voltage to a voltage that is about 2% below the target value.

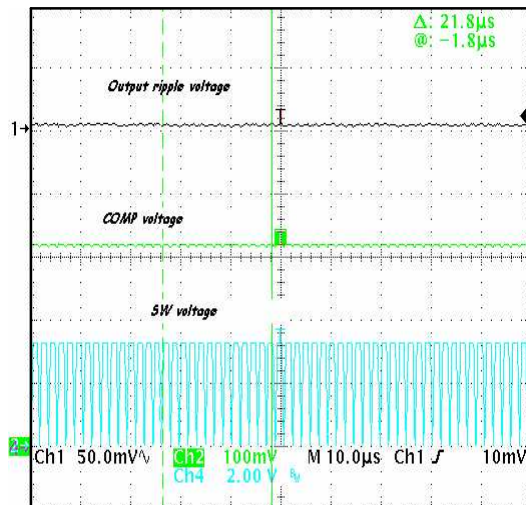


Figure 4. Output Ripple Voltage, COMP Pin Voltage, and SW Pin Voltage in Normal Operation

In the converter, a comparator detects if the output voltage is below or above -1% of the target output voltage. For output voltages below -1% of the target output voltage, the converter is not allowed to be in or go into the power-save mode. With an output voltage above this level, the converter enters the power-save mode when the inductor current is discontinuous.

Therefore, with a 1-M Ω resistor connected at the COMP pin, the converter regulates the output voltage to -2% of the target value; the converter does not go into power-save mode and operates in discontinuous inductor current mode. This results in a much-reduced output ripple voltage at a lower efficiency due to constant switching losses in fixed frequency PWM mode operation.

Description

When there is no load or a light load, the output voltage of the converter rises because of minimum on-time caused by the delays in the comparators, power stage, etc. When the output voltage rises above -1% of the target value, the converter enters power-save mode, and when the output voltage drops below the -1% point, the converter turns on again. (It is not exactly -1% because some hysteresis is also built in.)

Figure 5 shows that when the output load is low, the converter goes into power-save mode operation. This is with a $1\text{-M}\Omega$ resistor added across the COMP pin.

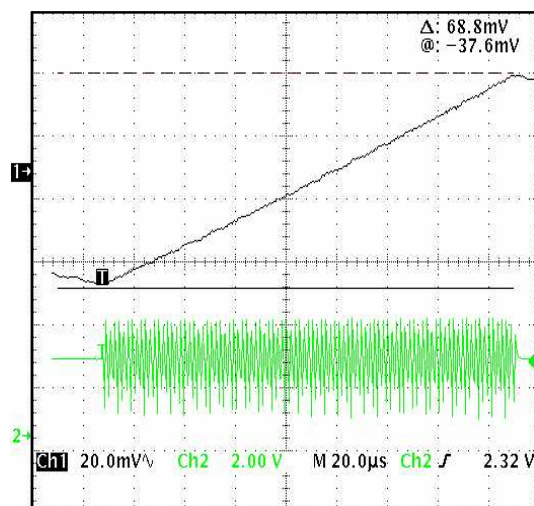


Figure 5. Output Ripple Voltage (Upper Trace) and SW Voltage (Lower Trace) Waveform, $V_{in} = 2.5\text{ V}$, $I_{out} = 3.5\text{ mA}$, PFM Mode Operation

Figure 6 shows that with the $1\text{-M}\Omega$ resistor in place, the converter operates in PWM mode and is not allowed to enter power-save mode operation as previously discussed. The output ripple is significantly reduced.

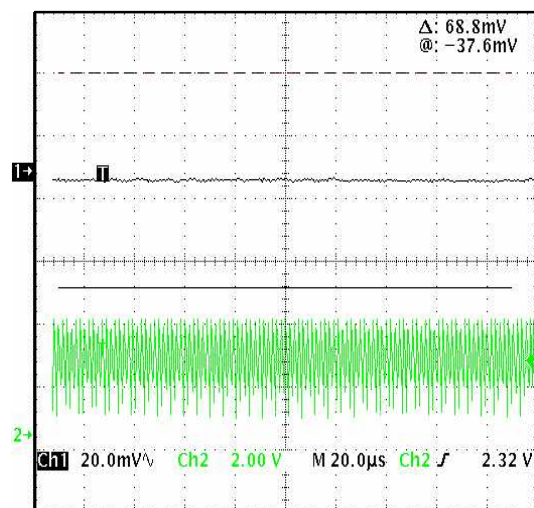


Figure 6. Output Ripple Voltage (Upper Trace) and SW Voltage (Lower Trace) Waveform, $V_{in} = 2.5\text{ V}$, $I_{out} = 13\text{ mA}$, PWM Mode Operation

Figure 7 shows that the ripple voltage reappears at the output ($\sim 10\text{ mV}$). However, this is not PFM mode operation; rather, the inductor current is switching between discontinuous inductor current and continuous inductor current operation. The discontinuous/continuous inductor current mode of operation is related to the output power vs input voltage and inductor value. This is a correct and expected behavior.

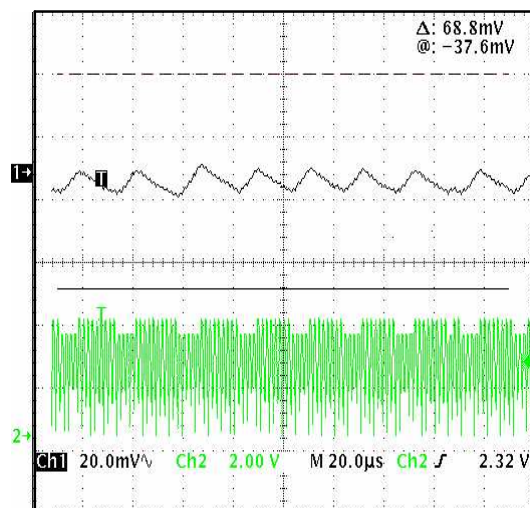


Figure 7. Output Ripple Voltage (Upper Trace) and SW Voltage (Lower Trace) Waveform, $V_{in} = 2.5\text{ V}$, $I_{out} = 40\text{ mA}$

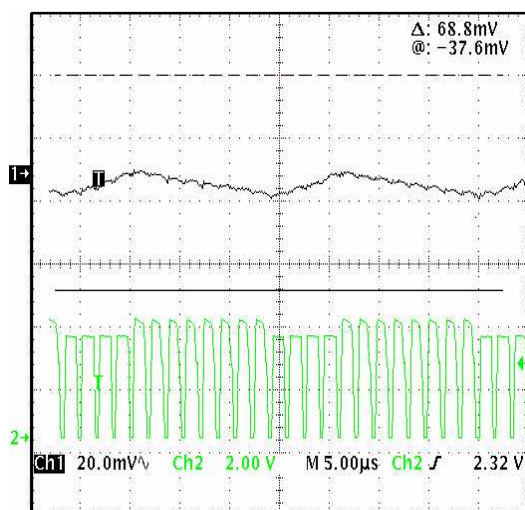


Figure 8. Expanded View of Figure 7

Figure 9 shows that with further increase of output load, the converter operates at continuous inductor current mode, and hence the output ripple is reduced again.

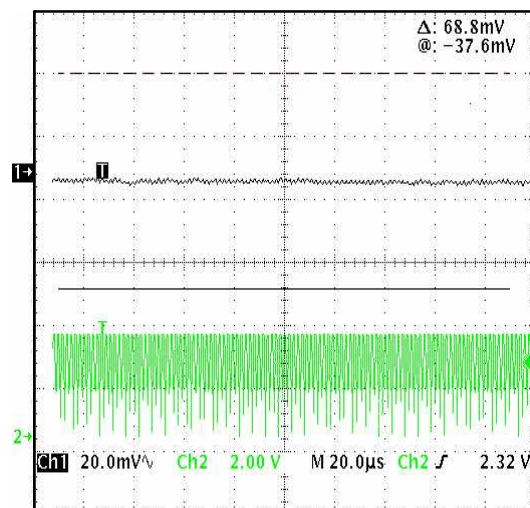


Figure 9. Output Ripple Voltage (Upper Trace) and SW Voltage (Lower Trace) Waveform, $V_{in} = 2.5\text{ V}$, $I_{out} = 65\text{ mA}$

Figure 10 shows the region of operation between continuous and discontinuous inductor current operation and region of operation between entering/exiting power-save mode operation when the 1-M Ω resistor is connected across the COMP pin.

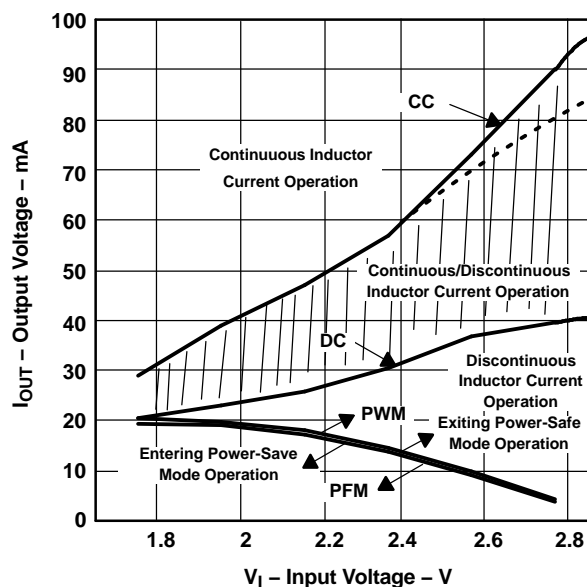


Figure 10. Regions of Operation Between Continuous/Discontinuous Inductor Current and Between Entering/Exiting Power-Save Modes

2 Summary

The TPS6101x automatically goes into PFM mode when the output voltage is 1% above the nominal voltage and when the inductor current is discontinuous. This might not be acceptable in noise-sensitive applications as the output ripple is much higher during PFM mode operation and might cause interference to their system performance. This application report presents a way to modify the PFM mode of operation to meet low ripple voltage requirements at light load by changing the transconductance amplifier output compensation with detailed explanation and test results.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
		Telephony	www.ti.com/telephony
		Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265