

Where are we?

- ▶ Lots of Layout issues
 - ▶ Line of diffusion style
 - ▶ Power pitch
 - ▶ Bit-slice pitch
 - ▶ Routing strategies
 - ▶ Transistor sizing
 - ▶ Wire sizing

Layout - Line of Diffusion

- ▶ Very common layout method
 - ▶ Start with a "line of diffusion" for each type
 - ▶ Cross with poly to make transistors
 - ▶ This is the "type 2" NOR gate

Line of Diffusion in General

- ▶ Start with lines of diffusion for each transistor type

Line of Diffusion in General

- ▶ Cross with Poly to make transistors

Line of Diffusion in General

- ▶ Now break and connect diffusion
 - ▶ There's our NOR gate

Stick Diagrams

- ▶ You can plan things with paper and pencil using Stick Diagrams
 - ▶ You'll need colored pencils
 - ▶ Draw lines for layers instead of rectangles
 - ▶ Then you can translate to layout

Gate Layout

- ▶ Layout can be very time consuming
 - ▶ Design gates to fit together nicely
 - ▶ Build a library of standard cells
- ▶ Standard cell design methodology
 - ▶ V_{DD} and GND should abut (standard height)
 - ▶ Adjacent gates should satisfy design rules
 - ▶ nMOS at bottom and pMOS at top
 - ▶ All gates include well and substrate contacts

Example: Inverter

Example: NAND3

- ▶ Horizontal N-diffusion and p-diffusion strips
- ▶ Vertical polysilicon gates
- ▶ Metal1 V_{DD} rail at top
- ▶ Metal1 GND rail at bottom
- ▶ 32λ by 40λ

Stick Diagrams

- ▶ *Stick diagrams* help plan layout quickly
 - ▶ Need not be to scale
 - ▶ Draw with color pencils or dry-erase markers

Wiring Tracks

- ▶ A *wiring track* is the space required for a wire
 - ▶ 4λ width, 4λ spacing from neighbor = 8λ pitch
- ▶ Transistors also consume one wiring track

Well spacing

- ▶ Wells must surround transistors by 6λ
 - ▶ Implies 12λ between opposite transistor flavors
 - ▶ Leaves room for one wire track

Area Estimation

- ▶ Estimate area by counting wiring tracks
 - ▶ Multiply by 8 to express in λ

Example: O3AI

- ▶ Sketch a stick diagram for O3AI and estimate area
 - ▶ $Y = (A+B+C) \cdot D$

Example: O3AI

- ▶ Sketch a stick diagram for O3AI and estimate area
 - ▶ $Y = (A+B+C) \cdot D$

Example: O3AI

- ▶ Sketch a stick diagram for O3AI and estimate area
 - ▶ $Y = (A+B+C) \cdot D$

Euler Paths

- ▶ A graphical method for planning complex gate layout
 - ▶ Take the transistor netlist and draw it as a graph
 - ▶ Note that the pull-up and pull-down trees can be duals of each other
 - ▶ Find a path that traverses the graph with the same variable ordering for pull-up and pull-down graphs
 - ▶ This guides you to a line of diffusion layout

Simple example: NOR

- ▶ Euler path is a tour of all edges
- ▶ Find a path that has the same ordering for pull-up and pull-down, i.e. $A B$
 - ▶ $V_{dd} A 1 B Out$ $GND A Out B GND$

This Path Translates to Layout

- Find a path that has the same ordering for pull-up and pull-down, i.e. A B
- You can also include all the internal nodes
- Pull-up: Vdd A 1 B Out
- Pull-Down: GND A Out B GND
- Line of diffusion layout

Examples

- Switch to chalkboard for examples
- Also chalkboard examples of latches and feedback

Layout Example: Flip Flop

- Simple D-type edge triggered flip flop

Zoom in on Latch

- Need two copies of this for a full D flip flop

Stick Diagram of Latch

- First add the gates
- Note where outputs can be shared
- Ignore details of signal crossings for now...

Stick Diagram of Latch

- First add the gates
- Note where outputs can be shared
- Ignore details of signal crossings for now...

Stick Diagram of Latch

- First add the gates
 - Note where the signals are relative to the schematic

Stick Diagram of Latch

- First add the gates
 - Note where the signals are relative to the schematic
 - Note where additional connections are needed

Start With First Enabled Inv

- I'm using 5u power wires, 29u vertical pitch based on the C5x standard cell model
 - Probably overkill...
- Add DIF for N- and P-type transistors
 - Note 2x standard size because of serial connection

Add Next Enabled Inverter

- Add two more poly gates for second enabled inverter
 - Note that the two enabled inverters share an output (not connected yet)
 - Note that I've added vdd! and gnd! For DRC
 - I'll deal with C-Cb crossover later...

Aside: Multiple Contacts

- Metal resistance 0.05 ohm/sq
- Contact resistance 5 ohms/contact
- Active resistance 70 ohms/sq
- Gate resistance 50 ohms/sq
- Active resistance 7 ohms - contact to gate minimum distance

- Look at a model of transistor resistance

Contact Option #1

- Total equivalent resistance = 56.1 Ohms
 - Metal resistance = 0.05 O/square
 - Contact resistance = 5 O/contact
 - Active resistance = 70 O/square
 - Gate resistance = 50 O/square
 - Active resistance 70 - contact to gate

Contact Option #2

Case 2

- ▶ Total equivalent resistance = 105.1 Ohms

Contact Option #3

Case 3

- ▶ Total equivalent resistance = 24.7 Ohms
- ▶ So, put in as many contacts as will fit along side a wide gate...

Meanwhile, Add inverter

- ▶ Note that it's back to standard size
- ▶ Shares vdd/gnd connection with enabled inverter
- ▶ Minimum spacing for all transistors so far
 - ▶ Incremental DRC at EVERY step!

Finish Inverter (mostly)

- ▶ Make inverter output connections
 - ▶ Don't connect yet
 - ▶ I'm going to use M1 as a horizontal layer
 - ▶ Which means being careful about vertical use of M1

Make Feedback Connections

- ▶ Output of inverter (connected in M1 for now) goes to input of 2nd enabled inverter
- ▶ Output of enabled inverters goes to input of inverter
 - ▶ Note that outputs of enabled inverters goes through POLY

Deal With C/Cb Crossover

- ▶ Start by cutting the "select" gates of the enabled inverters

Connect the C Input

- ▶ Prepare for M1 crossover in C wire
 - ▶ C is N-type in first enabled inverter, P-type in second enabled inverter
 - ▶ Use M1PLY contacts
- ▶ PROBLEM! We need to squeeze a poly wire inbetween those contacts...
 - ▶ Use design rules to plan for space

Look at Gap

- ▶ You need to have enough space for minimum width poly to fit through gap

Start Making Room

- ▶ Push D-signal poly out of the way with minimum spacing to DIF
 - ▶ We'll move it back later
- ▶ Make sure to continue to DRC at every step!

- ▶ Jog the poly around and through the gap with minimum spacing to M1PLY contact on both sides

Fit Things Back Together

- ▶ Now put big D-poly jog back as close as you can

- ▶ Add M1PLY contacts for future connections
 - ▶ Need to get Cb, C, D signals into the latch in the future
 - ▶ Those will most likely be routed on some type of metal
 - ▶ So we need the M1 metal connection at the bottom

Plan For Clock Routing

- ▶ Break M1 output connection on inverter to leave room for horizontal M1 routing
- ▶ I'll eventually route C and Cb through the cell horizontally on M1

Bit Slice Plan

- ▶ Plan is to stitch these together to make a register
- ▶ Inputs on top in M2
- ▶ Outputs on bottom in M2
- ▶ Clock and Clock-bar routed horizontally in M1

Need Second Latch

- ▶ Basically a copy of the first latch
- ▶ But with reversed C and Cb connections
- ▶ Copy the first layout...

Expand from Latch to F/F

- ▶ Select and copy the first latch
- ▶ Now I need to reverse the C and Cb connections

C/Cb Routing Plan

- ▶ Remember my C/Cb routing plan
- ▶ Plan for where those wires can go

C/Cb Routing Plan

- ▶ Remember my C/Cb routing plan
- ▶ Plan for where those wires can go

Connect Clocks to 1st Latch

- ▶ Adjust contact positions for the first enabled inverter

Connect Clocks to 2nd Latch

- ▶ Now shift the contacts the other way for the second latch
- ▶ Makes the complementary C/Cb connection

Connect Clocks to 2nd Latch

- ▶ Now shift the contacts the other way for the second latch
- ▶ Makes the complementary C/Cb connection

Connect the Two Latches

- ▶ Q of first goes to D of second
- ▶ Don't really need both top and bottom connections, but it doesn't hurt
- ▶ Lower resistance paths

Note Extra Routing Channels

- ▶ Note that this vertical pitch, and this cell contents have left two additional M1 horizontal routing channels through the middle of the cell

Now Consider Output Inverters

- ▶ Two more inverters
- ▶ Make them 2x size for output drive

Output Inverters

- ▶ Add the DIF for the output inverters
- ▶ Remember I want to make them 2x size

Make Output Connections

- ▶ Add vdd, gnd and output contacts
- ▶ Add poly gates
- ▶ Make output connections in M2
- ▶ Connect to 2nd latch and to 2nd inverter

Now Squeeze Inverter

- ▶ Select regions of the layout and stretch to move it all to a new spot

Keep Squeezing

- ▶ Now squeeze power supply contacts

Squeezed Version

- ▶ Output inverters squeezed together
- ▶ Note that D, Q, And Qb are routed vertically in M2

Final D-Type Flip Flop

- ▶ Squeeze vertically since I don't need extra routing channels, and I don't need to match with standard cells
- ▶ Add long TUB and SUB contacts

Put Four of them Together

D3 D2 D1 D0 C
 Q3 Q2 Q1 Q0 Cb

- ▶ Add instances that abut
 - ▶ Or use the "array" feature of the instance dialog
- ▶ Note that C and Cb are routed in horizontal M1

Zoom in to Cell Boundary

- ▶ There's a little extra space
 - ▶ Caused by wanting each latch to DRC on its own
 - ▶ Could close this up by overlapping cells