Using Programmable Logic Devices

Introduction

This application note covers three areas:

- Where and *why* do I use Programmable Logic Devices (*PLD*s)?
- How do I use PLDs?
- Software and hardware *support* for Atmel PLDs.

Where Do I Use PLDs?

Any digital logic design can be done using PLDs. If you normally begin your design by:

- Using AND and OR functions
- Thinking of 7400 series components
- Using truth tables, or
- State diagrams

You are already on the path to using PLDs.

Designing a microprocessor-based system, with memory and I/O? How about all that "glue" logic you use to interface with the bus, provide chip selects, and any unusual signals required by special chips? Most of these functions are currently done with 7400 series TTL. *How about using a PLD instead*?

Designing a stand-alone PC board which uses a state machine to control multiple output signals? Using latches to synchronize signals? Using counters to divide down master clock frequencies? Converting parallel-to-serial and back again? All of these functions fit easily in modern PLDs. *Most anything found in your TTL Databook can be replaced with your own, PERSONALIZED, programmable logic device.*

PLD Applications

- Glue Logic
- State Machines
- Synchronization
- Decoders
- Counters
- Bus Interfaces
- Parallel-to-Serial
- Serial-to-Parallel
- Subsystems
- and Many Others

Why PLDs?

Maybe you have already heard all the wonderful reasons for using PLDs. Well, they're true! First, let's review some of the more important ones:

- Increased Integration. You can reduce the package count of your designs while simultaneously increasing the features offered by your product.
- Lower Power. CMOS and fewer packages combine to reduce power consumption.
- Improved Reliability. Lower power plus fewer interconnections and packages translate into greatly improved system reliability.
- Lower Cost. PLDs reduce inventory costs, too.
- Easier To Use! Yes, believe it or not, once you get past the initial learning period, PLDs are easier to use than discrete logic functions.
- Easier to Change. Oops! Need to make a change? You won't need "blue wire" when you use a PLD – all changes are internal,and can be done quickly. ECNs are a snap – and system reliability is maintained!





Erasable Programmable Logic Device

Application Note

Rev. 0485C-09/99



Let's Get Started!

Figure 1 describes the PLD design process. After having read the first part of this application note, you now have the perfect application for a PLD, right? So here you go!

How do you translate your idea into a working prototype? *First, you need a computer with an editor of some kind.* If you have a workstation with a schematic editor, you may input your design using familiar logic blocks. Otherwise, a line or full screen text editor, used in the non-document mode will do. An example of an ABEL[™] text file is on the next page.

Next, turn the **logic compiler** loose on your design. First it will *check for typographical errors* and any inconsistencies in your specification. Most compilers then attempt to *reduce your logic* using standard logic reduction theory. Then, a **simulator** will check the test vectors you input, comparing your logic description against the predicted responses. This is an excellent way to verify your design. Check with the appropriate software manuals for more information.

At the end of the compilation process, a *JEDEC* file is output. This file is a standard format accepted by most programming hardware. Next *download this file* to your chosen programmer.

At this point you are ready to "build" your **prototype**. Make sure the programmer has the correct information to program the device you have chosen (an Atmel PLD, of course), plug in your device, and go! Most programmers will even functionally test your prototype for you if you include test vectors in your JEDEC file.

Take your configured PLD, and *plug it into your system*. If you find any errors, just use your editor to make the necessary changes, and repeat the process. It's easy!

Example Design

The following design is a simple example using ABEL[™] to process the logic description file and an AT22V10 as the target device. The equations are on the next page, and are a direct reproduction of the actual ABEL input file.

Each of the three allowable input formats are shown. A truth table is used to describe a simple 2-to-4 decoder, as

is often used to decode chip selects in a microprocessor system. Next, the state machine format is used to describe a divide-by-4 counter. And finally, Boolean equations are used to describe some random logic.

Note the test vectors used to test the device. The "c" nomenclature means that this pin has a low-to-high-to-low series of transitions for this vector. Each time this happens, the counter should increment. Also note that the counter starts in the reset condition, which is both outputs "1" for an active low output.

Now you're ready to go - Have fun!





Note: 1. Examples of compilers are ABEL, CUPL[™], PLDesigner XL[™], nd LOG/iC. Each of these products contains modules which allow simulation of your design. They also minimize your logic equations, which gives you flexibility in describing your design.

Example ABEL Description File

```
module X3;
title 'Example using 22V10 - KHG 1/6/88';
X310 device 'P22V10';
Clk,A12,A13
                          pin1,2,3;
CE0,CE1,CE2,CE3
                          pin20,21,22,23;
Q1,Q2,CarOut
                          pin17,18,14;
CarEn,A,B,C,D
                          pin6,7,8,9,10;
Out1,Out2
                          pin15,16;
X,Z,c
                           = .X. , .Z. , .C.;
"Counter States
                           = ^b00;
State1
                                       State2
                                                = ^b01;
                           = ^b10;
State3
                                       State4
                                               = ^b11;
"The following truth table defines the 2 to 4 decoder, which decodes
" A13 and A12 into CE0, CE1, CE2, and CE3.
truth_table ([A13,A12] -> [CE0,CE1,CE2,CE3])
[0, 0] \rightarrow [0, 1, 1, 1];
[0,1] -> [1,0,1,1];
[1,0] -> [1,1,0,1];
[1,1] -> [1,1,1,0];
"The following state description defines the divide by 4 counter
state_diagram [Q2,Q1]
State State1: GOTO
                      State2;
State State2:
                GOTO
                       State3;
                GOTO
State State3:
                       State4;
                GOTO
                       State1;
State State4:
" The following equations are general in nature to illustrate Boolean input
" format. The CarOut equation uses state 4 above to produce a carry.
Equations
CarOut
                           = Q2 & Q1 & CarEn;
                                                      "& = AND
Out1
                           = A & B + C & D; "+ = OR, AND takes precedence
Out2
                           = A & C + B & D;
"The following are the appropriate test vectors
test_vectors
([Clk, CarEn, A13, A12, A, B, C, D] - >[CE0, CE1, CE2, CE3, Q2, Q1, CarOut, Out1, Out2]);
[0, 0, 0, 0, 0, 0, 0, 0] - > [0, 1, 1, 1, 1, 1, 0, 0, 0];
[ c, 0, 0, 1, 1, 1, 0, 0 ] - >[ 1, 0, 1, 1, 0, 0, 0, 1, 0 ];
[\ c,\ 0,\ 1,\ 0,\ 1,\ 0,\ 1,\ 0\ ]\ -\ > [\ 1,\ 1,\ 0,\ 1,\ 0,\ 1,\ 0,\ 0\ ,\ 1\ ];
[\ c,\ 0,\ 1,\ 1,\ 0,\ 0,\ 1,\ 1\ ]\ -\ > [\ 1,\ 1,\ 1,\ 0,\ 1,\ 0,\ 1,\ 0\ ,\ 1,\ 0\ ];
[\ c,\ 0,\ 0,\ 0,\ 0,\ 1,\ 0,\ 1\ ]\ -\ > [\ 0,\ 1,\ 1,\ 1,\ 1,\ 1,\ 0,\ 0,\ 1\ ];
[ 0, 1, 0, 1, 1, 1, 1, 1 ] - > [ 1, 0, 1, 1, 1, 1, 1, 1];
```

end X3;





Atmel Headquarters

Corporate Headquarters 2325 Orchard Parkway San Jose, CA 95131 TEL (408) 441-0311 FAX (408) 487-2600

Europe

Atmel U.K., Ltd. Coliseum Business Centre Riverside Way Camberley, Surrey GU15 3YL England TEL (44) 1276-686-677 FAX (44) 1276-686-697

Asia

Atmel Asia, Ltd. Room 1219 Chinachem Golden Plaza 77 Mody Road Tsimhatsui East Kowloon Hong Kong TEL (852) 2721-9778 FAX (852) 2722-1369

Japan

Atmel Japan K.K. 9F, Tonetsu Shinkawa Bldg. 1-24-8 Shinkawa Chuo-ku, Tokyo 104-0033 Japan TEL (81) 3-3523-3551 FAX (81) 3-3523-7581

Atmel Operations

Atmel Colorado Springs 1150 E. Cheyenne Mtn. Blvd. Colorado Springs, CO 80906 TEL (719) 576-3300 FAX (719) 540-1759

Atmel Rousset Zone Industrielle 13106 Rousset Cedex France TEL (33) 4-4253-6000 FAX (33) 4-4253-6001

Fax-on-Demand North America:

1-(800) 292-8635 International: 1-(408) 441-0732

e-mail literature@atmel.com

Web Site http://www.atmel.com

BBS 1-(408) 436-4309

© Atmel Corporation 1999.

Atmel Corporation makes no warranty for the use of its products, other than those expressly contained in the Company's standard warranty which is detailed in Atmel's Terms and Conditions located on the Company's web site. The Company assumes no responsibility for any errors which may appear in this document, reserves the right to change devices or specifications detailed herein at any time without notice, and does not make any commitment to update the information contained herein. No licenses to patents or other intellectual property of Atmel are granted by the Company in connection with the sale of Atmel products, expressly or by implication. Atmel's products are not authorized for use as critical components in life support devices or systems.

Marks bearing [®] and/or [™] are registered trademarks and trademarks of Atmel Corporation.

Terms and product names in this document may be trademarks of others.

