

Using Decoupling Capacitors in 3.3-V Systems

A power supply decoupling structure is like a tree, starting at the supply and ending at the individual Vcc pin. At each level, you should not allow a voltage drop (delta V) of more than 30 mV.

General Formula: $\Delta V = I \cdot t / C$

The following example shows how to calculate capacitor values in a typical application. These calculations ignore the series inductance in each capacitor, and make assumptions about power and frequency that may not fit every application.

There is a decoupling capacitor at every Vcc pin. A dc current of 200 mA per pin is a reasonable assumption, but this current might come as a 1-Amp spike with 20% duty cycle at perhaps 40 MHz:

$$C = 1 \text{ A} \cdot 5 \text{ ns} / 30 \text{ mV} = 150 \text{ nF} = 0.15 \mu\text{F}$$

This capacitor also must support the charging of load capacitors. Let's assume eight pins

with 50 pF each = 400 pF total:

$$C = 3 \text{ V} \cdot 0.4 \text{ nF} / 30 \text{ mV} = 40 \text{ nF} = 0.04 \mu\text{F}$$

This means that a 0.1 μF decoupling capacitor is marginal for supplying the internal dynamic current (1 A • 5 ns), but can easily supply eight full-swing outputs.

There is a larger capacitor, one per device, that evens out slower current changes. This capacitor might supply 5 Amps dc for a microsecond:

$$C = 5 \text{ A} \cdot 1 \mu\text{s} / 30 \text{ mV} = 150 \mu\text{F}$$

At the output of the switching supply is a capacitor that supplies 50 Amps to the whole board, and covers the 100 kHz period of the switching supply:

$$C = 50 \text{ A} \cdot 10 \mu\text{s} / 30 \text{ mV} = 15,000 \mu\text{F}$$

Vcc decoupling is important, and becomes more critical as chips get bigger, as clock frequencies and supply current increase, and as supply voltage decreases. ♦